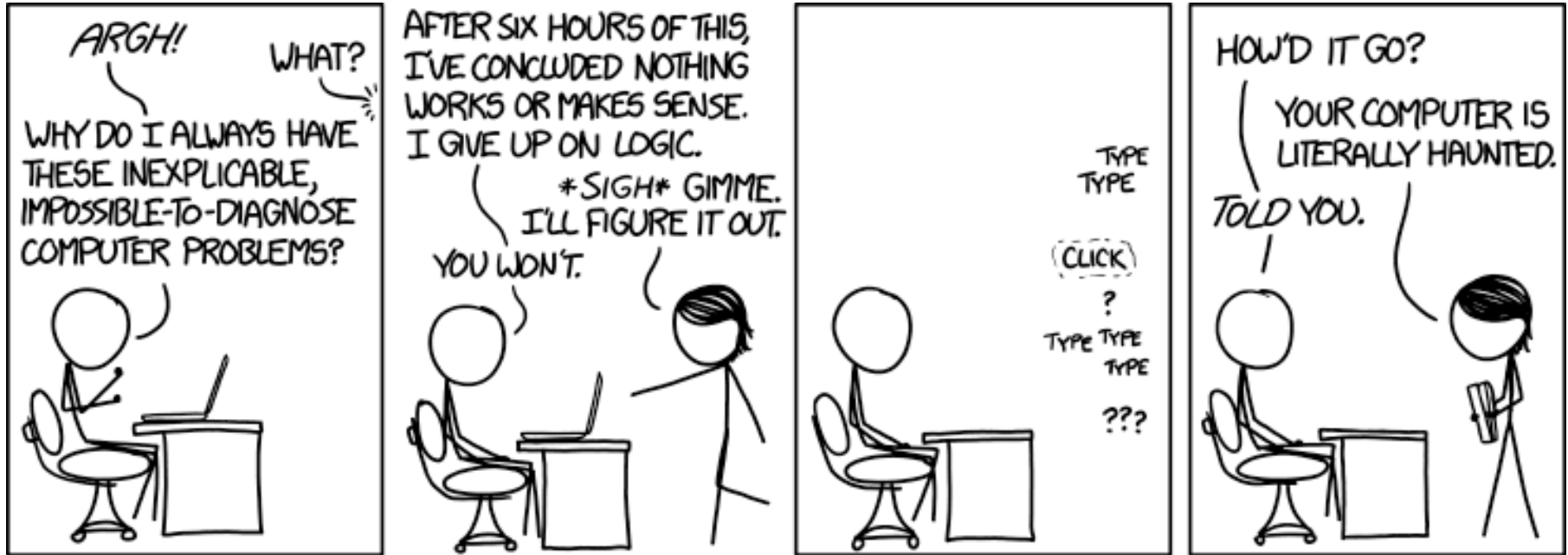


Three week "detour," featuring ...




... *the ghost in the machine*

OK Recursing?
OKer than before?

Hw#4: binary + Python

CS ||| Today

Circuit design, part 1

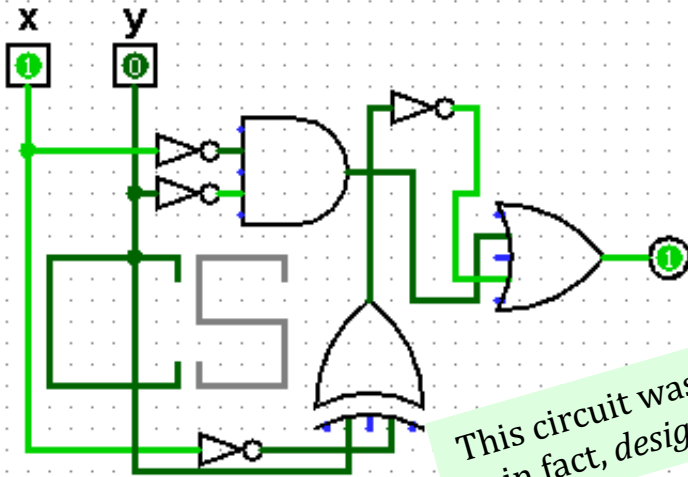

This circuit was NOT,
in fact, designed!



Minterm Expansion Principle

That's minterm, NOT midterm



A circuit for *any function* can be built from ...



... *just* these three logic gates!

Last week's solutions

*too compressed,
admittedly!*

```
def blsort(L):
    """ returns a sorted version of L
        (L has only 1's and 0's)
    """
    return count(0,L)*[0] + count (1,L)*[1]

def decipher (S):
    """ input: string that has been shifted
        output: English rotation of S
    """
    L = [ encipher(S,n) for n in range(26) ]
    LoL = [ [wordProb(x),x] for x in L ]
    bestpr = max(LoL)
    return bestpr[1]

def gensort(L):
    """ returns a sorted version of the list L
    """
    if len(L) == 0: return L
    else:
        m = min(L)
        R=remOne(m,L)
        return [m] + gensort(R)

def jscore(S,T):
    """ returns the jotto score of S vs. T
    """
    if S == '' or T == '': return 0
    elif S[0] in T:
        return 1 + jscore(S[1:],remOne(S[0],T))
    else: return jscore(S[1:],T)
```

```
def exact_change(t,L):
    """ returns whether t can be made by summing el's in L
    """
    if t==0: return True
    elif t<0 or L==[]: return False
    else:
        useit=exact_change(t-L[0],L[1:])
        loseit=exact_change(t,L[1:])
        return useit or loseit

def LCS (S,T):
    """ returns the longest common subseq of S and T
    """
    if S == '' or T=='': return ''
    elif S[0]==T[0]: return S[0]+LCS(S[1:],T[1:])
    else:
        result1 = LCS(S[1:], T)
        result2 = LCS(S, T[1:])
        if len(result1) < len(result2): return result2
        else: return result1

def make_change(t,L):
    """ returns how t can be made by summing el's from L
        or False, if it's not possible...
    """
    if t==0: return []
    elif t<0 or L==[]: return False
    else:
        useit=make_change(t-L[0],L[1:])
        loseit=make_change(t,L[1:])
        if useit == False: return loseit
        useit = L[0:1] + useit
        return useit
```

too recursive?

Creativity with Caesar...

```
def decipher( S ) :  
    """ TESIHYDW - je tusyfxuh  
        jxyi tesijhydw, zki j hkd  
        tusyfxuh ed yj.          """  
    ... code here ...
```

Creativity with Caesar...


```
def decipher( S ) :  
    """ DOCSTRING - to decipher  
        this docstring, just run  
        decipher on it.      """  
    ... code here ...
```

my *favorite* not-fully-working decipher...



Creativity with Caesar...
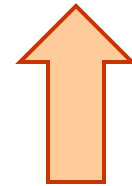
```
def decipher( S ) :  
    """ This works sometimes  
    """  
    return encipher( S, 3 )
```



and the docstring
is 100% correct!



This
week

def

Circuits!

... sometimes

```
return encipher( S, 3 )
```



Designing physical devices
that work *all the time!*

This
week

def

Circuits!

is sometimes

```
return encipher( S, 3 )
```


A FILM FROM DANIEL'S
**EVERYTHING
EVERYWHERE
ALL AT ONCE**



The big picture...

In a computer, each bit is represented as a voltage (**1** is +5v and **0** is 0v)

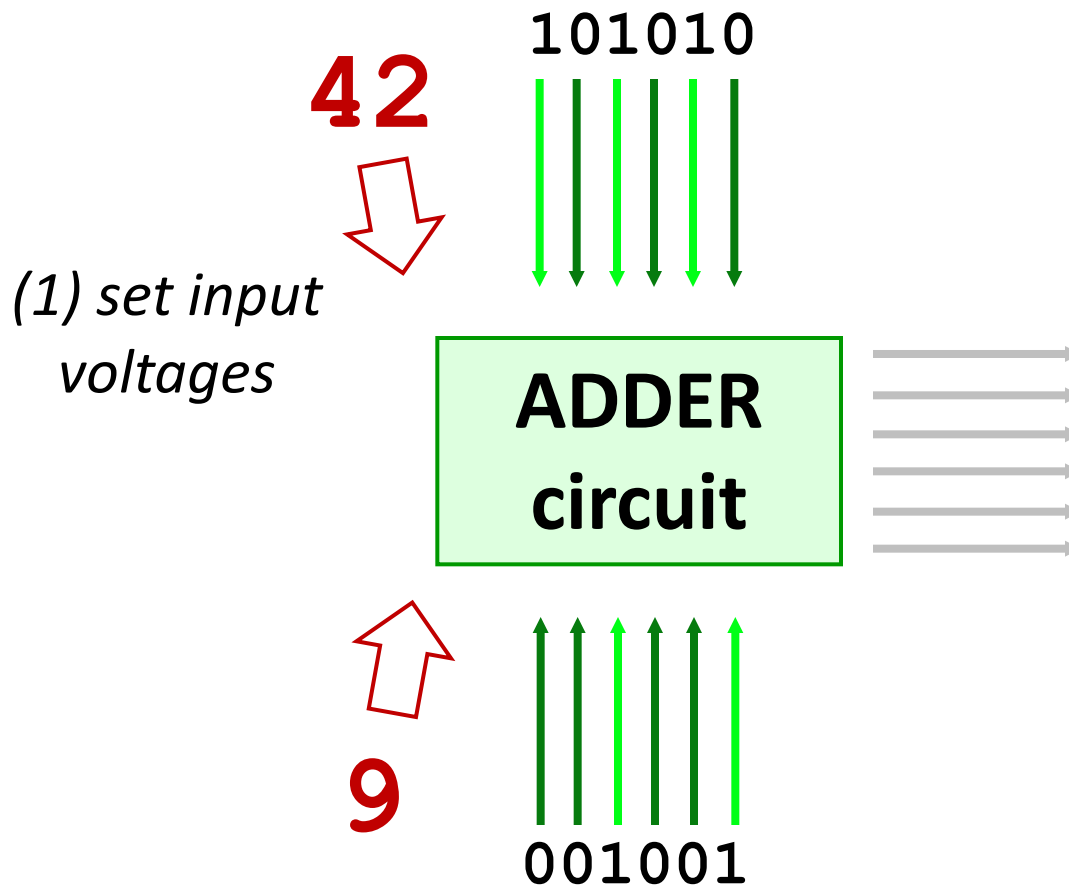Computation is simply the **deliberate combination** of those voltages!




What's in that green box?



The big picture...

In a computer, each bit is represented as a voltage (**1** is +5v and **0** is 0v)

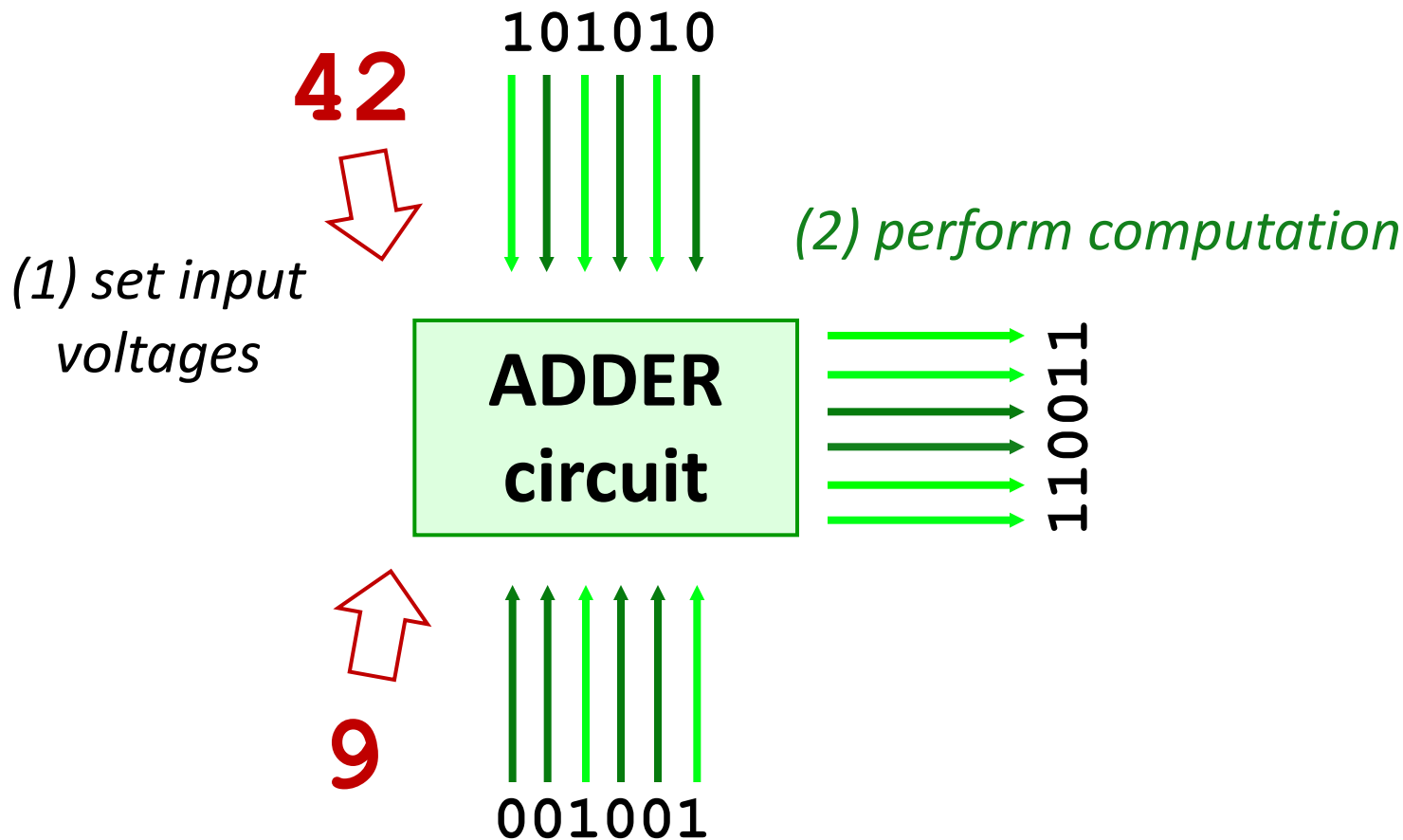Computation is simply the **deliberate combination** of those voltages!




What's in that green box?



The big picture...

In a computer, each bit is represented as a voltage (**1** is +5v and **0** is 0v)

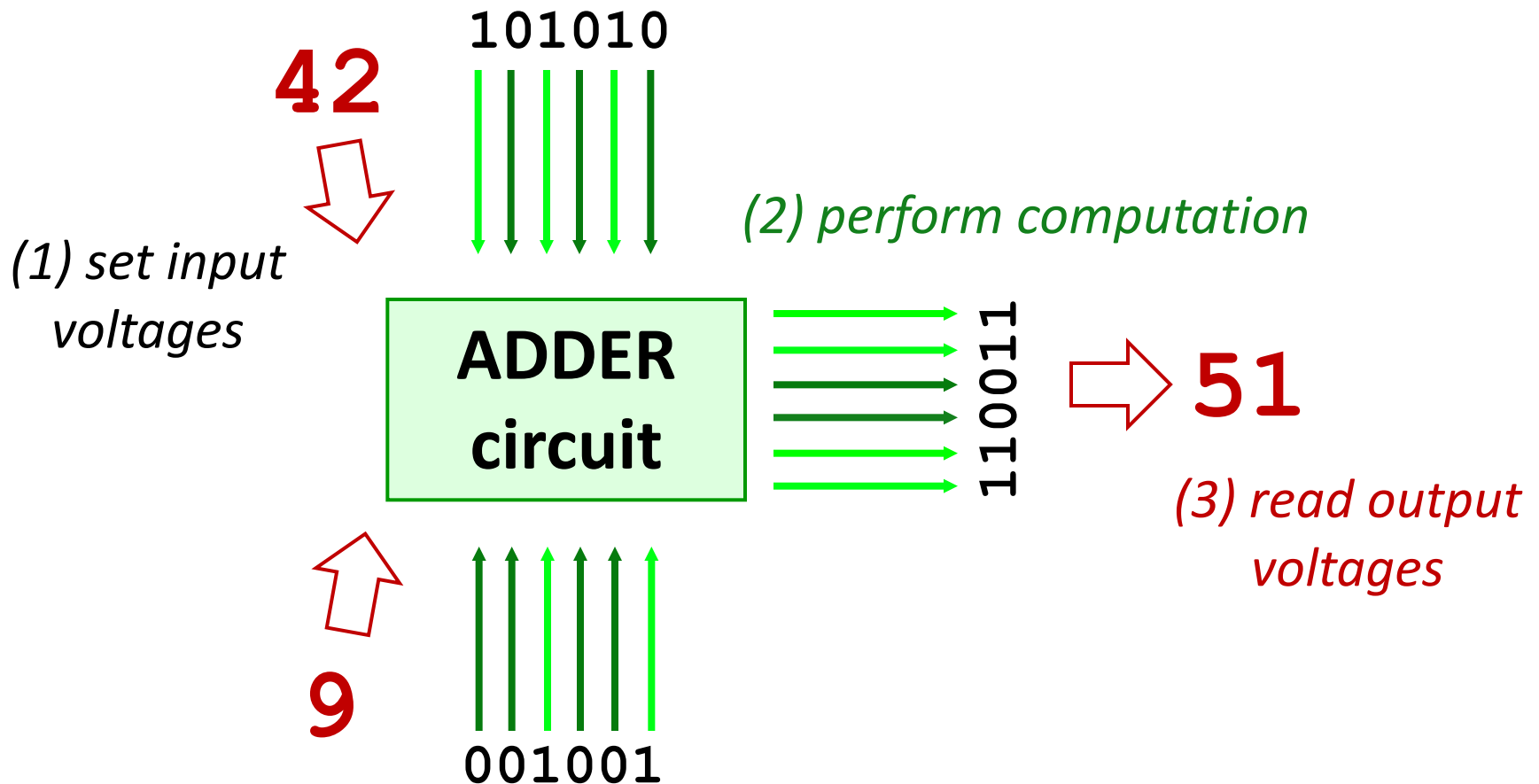Computation is simply the **deliberate combination** of those voltages!



What's in that green box?




Richard Feynman: "Computation is just a physics experiment that always works!"

All computations...

... are *functions of bits*

binary inputs A and B

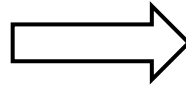

output, A+B

A	B		add
00	00	→	000
00	01	→	001
00	10	→	010
00	11	→	011
01	00	→	001
01	01	→	010
01	10	→	011
01	11	→	100
10	00	→	010
10	01	→	011
10	10	→	100
10	11	→	101
11	00	→	011
11	01	→	101
11	10	→	101
11	11	→	110

addB

bitwise
addition
function

four bits in...


...three bits out

You built this in Python
last week as **addB**
purely syntactically

This week, you'll
build the **addB**
function in
Circuitverse

Motivation: A function we want...

"three-bit"
adder

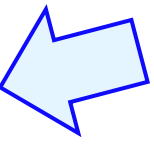

3 bits of input

$$\begin{array}{r} 1 \\ 0 \\ + 1 \\ \hline 10 \end{array}$$

2 bits of output

All 5 of these bits
have *names*... !

What! Why do these bits
get individual names?!



Motivation: A function we want...

"three-bit"
adder

3 bits of input

c
1

These three inputs can
change however we like ...

y
0

x
1

+

carry bit
10
sum bit

All 5 of these bits
have *names*... !

*Because each is an
individual wire!*

What! Why do these bits
get individual names?!



2 bits of output

*... but these two output bits will
have to change to be correct.*

Truth table

3 bits of input

$$\begin{array}{r} c \\ 1 \\ y \\ 0 \\ x \\ 1 \\ + \\ \hline \end{array}$$

carry bit 10 sum bit

Which output
bit is this
truth table ?!?

IN			OUT
x	y	c	circuit output
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Truth table

3 bits of input

$$\begin{array}{r} 1 \\ 0 \\ 1 \\ + \\ \hline 10 \end{array}$$

"sum" bit

carry bit


sum bit

Which output bit is this truth table ?!?

IN			"sum" bit
x	y	c	circuit output
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

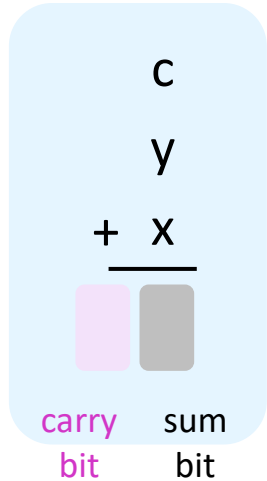Part 1: Represent your function as *bits*...

Any function can be represented using only bits...



IN			OUT
x	y	c	circuit output
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

This one is
named the
sum function

*That's some
function, all right!*



three bits in...

...one bit out

Truth table

3 bits of input

"carry" bit

$$\begin{array}{r} \mathbf{c} \\ \mathbf{x} \\ + \mathbf{y} \\ \hline \end{array}$$


carry bit ? ? sum bit

What truth table for the "carry" bit?

IN			OUT	
x	y	c	circuit output	
0	0	0	}	
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

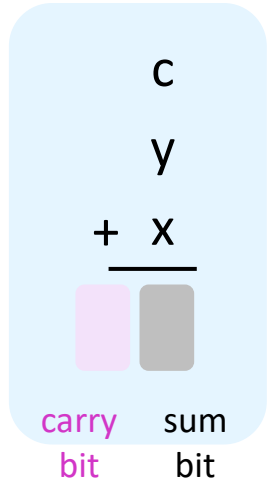Part 1: Represent your function as *bits*...

Any function can be represented using only bits...



IN			OUT
x	y	c	circuit output
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

This one is named the **carry** function

three bits in...

...one bit out

I'm feeling carried away, in fact!



Part 1: Represent your func as *bits*...

For
any
func!

Any function can be represented using only bits...

Use a
truth
table

IN			OUT
x	y	c	circuit output
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

another f'n!

fun!



three bits in...

...one bit out

Our building blocks: *logic gates*

AND



OR



NOT




These circuits are *physical* functions of bits...

not just theoretical models

... and *all* mathematical functions can be built from them!

Our building blocks: *logic gates*

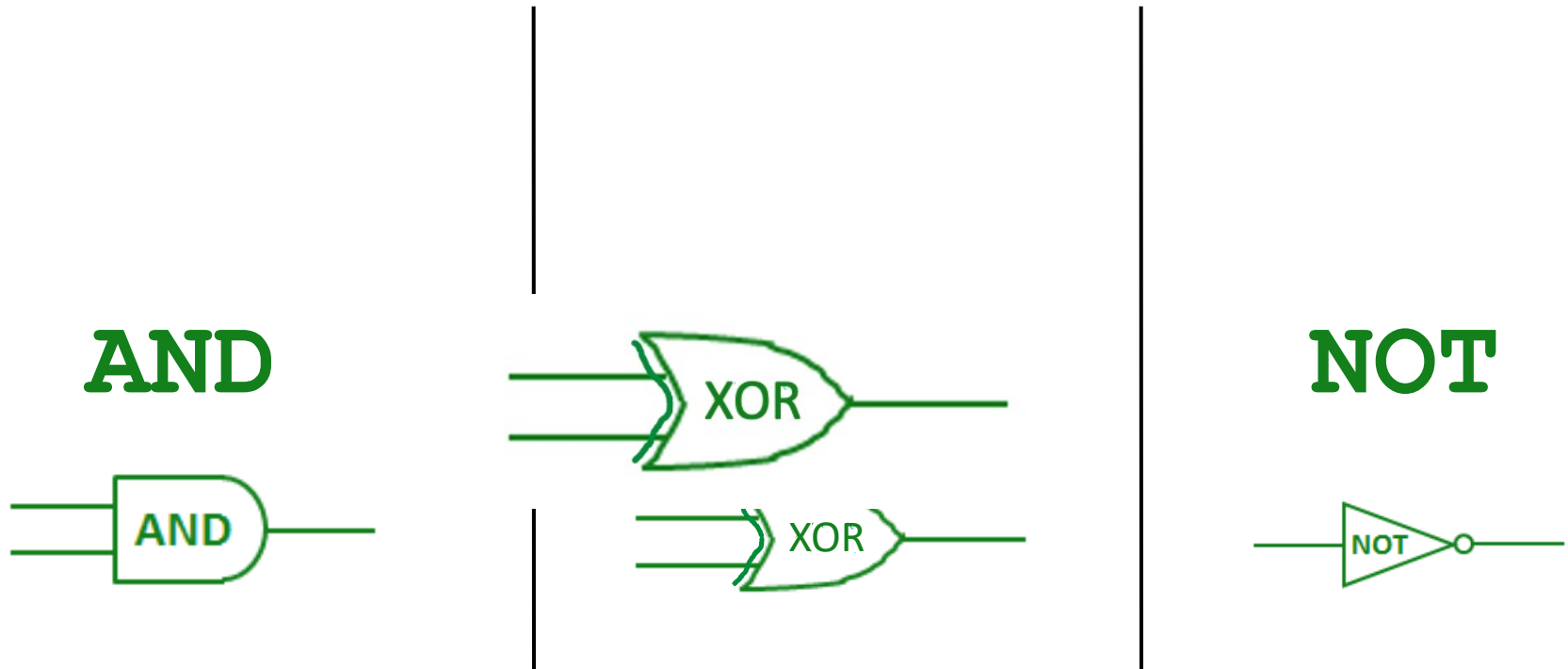

These circuits are *physical* functions of bits...

not just theoretical models

... and *all* mathematical functions can be built from them!

Our building blocks: *logic gates*

AND outputs 1 only
if **ALL** inputs are 1

AND



OR outputs 1 if
ANY input is 1

OR



NOT reverses
its input

NOT



These circuits are *physical* functions of bits...

not just theoretical models



... and *all* mathematical functions can be built from them!

AND

drill sergeant
metaphor?

Strict! Everything input must be
True to output a True

inputs

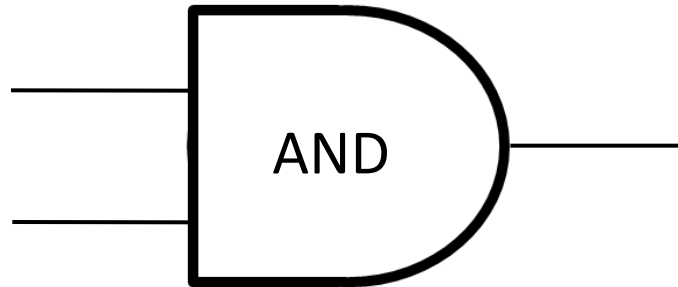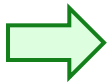



output

AND outputs 1 when **ALL** inputs are 1
otherwise it outputs 0

AND

Strict! Everything input must be True to output a True

inputs

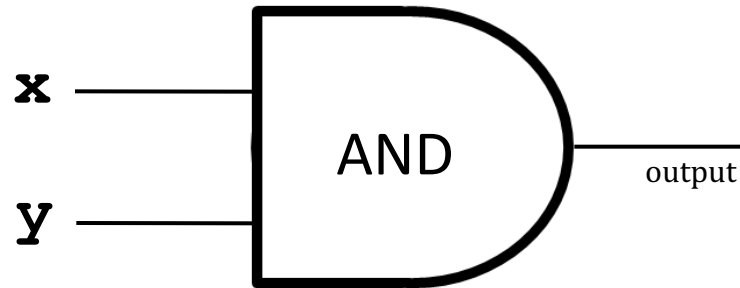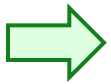

output

AND's
function:




input		output
x	y	AND (x, y)
0	0	0
0	1	0
1	0	0
1	1	1

"Truth table"

AND

Strict! Everything input must be True to output a True

inputs

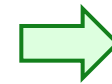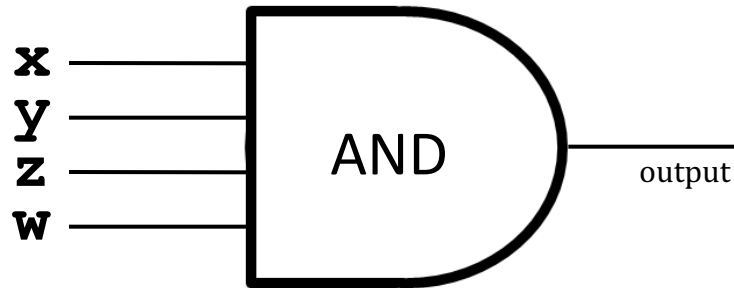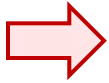

output

AND's
function:


input				output
x	y	z	w	AND (xyzw)
0	0	0	0	
0	0	0	1	
...12 more rows not shown...				
1	1	1	0	
1	1	1	1	

How many of the
16 rows here will
output a 1?

AND

Strict! Everything input must be True to output a True


inputs →

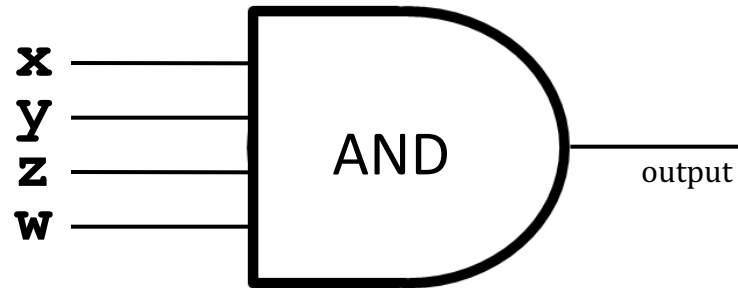

→ output

AND's
function:

input				output
x	y	z	w	AND (xyzw)
0	0	0	0	0
0	0	0	1	0
...12 more rows not shown...				0
1	1	1	0	0
1	1	1	1	1

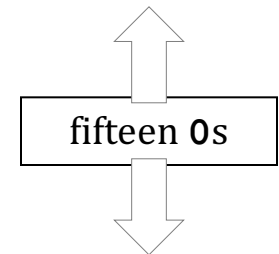




one 1

OR

camp counselor
metaphor?

easy-going: if anything is
OK, everything's OK

inputs

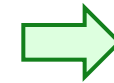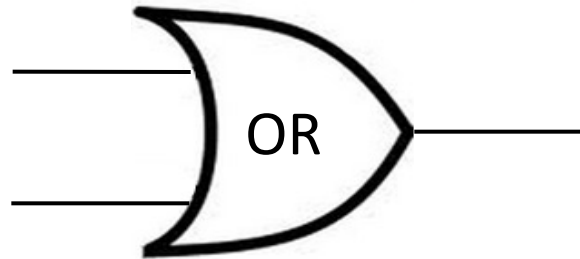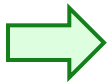

output


OR outputs 1 when **ANY** input is 1

It outputs 0 only if all inputs are 0.

OR

easy-going: if anything is True, the output is True

inputs 

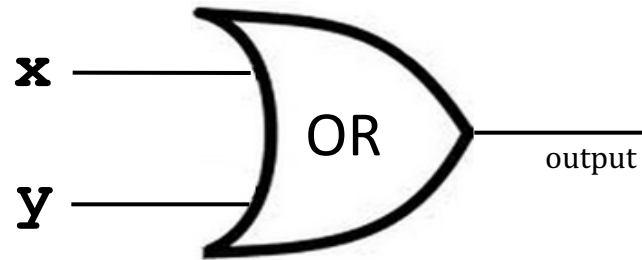

 output


OR's
function:

input		output
x	y	OR (x, y)
0	0	0
0	1	1
1	0	1
1	1	1

OR

easy-going: if anything is
OK, everything's OK

inputs

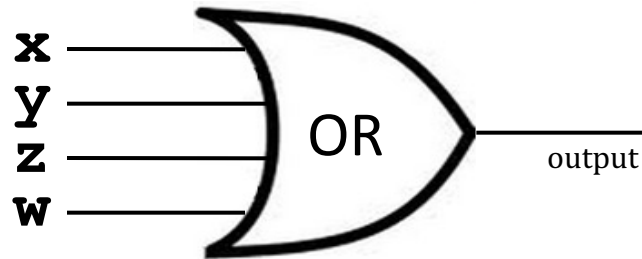

output

OR's
function:

input			
x	y	z	w
0	0	0	0
0	0	0	1
...12 more rows not shown...			
1	1	1	0
1	1	1	1



output
OR (xyzw)

How many of the
16 rows here will
output a 1?

OR

easy-going: if anything is
OK, everything's OK

inputs

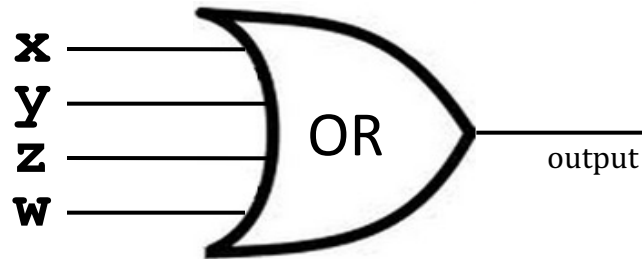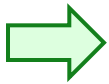

output


OR's
function:

input				output
x	y	z	w	OR (xyzw)
0	0	0	0	0
0	0	0	1	1
...12 more rows not shown...				1
1	1	1	0	1
1	1	1	1	1

one 0




fifteen 1s

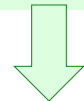

NOT

inputs →

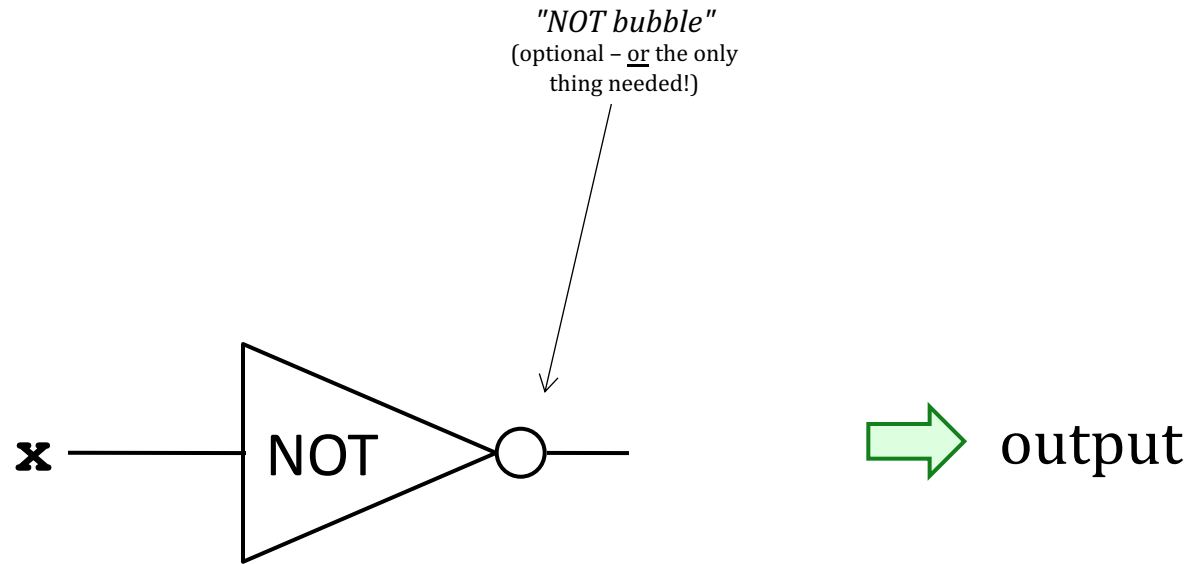

NOT's
function:

input	output
x	NOT (x)
0	1
1	0

one 1

one 0

Our building blocks: *logic gates*

input		output
x	y	AND (x, y)
0	0	0
0	1	0
1	0	0
1	1	1

AND outputs 1 only
if **ALL** inputs are 1


AND



input		output
x	y	OR (x, y)
0	0	0
0	1	1
1	0	1
1	1	1

OR outputs 1 if
ANY input is 1

OR

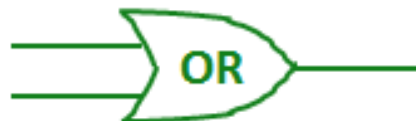

input	output
x	NOT (x)
0	1
1	0

NOT reverses
its input

NOT



Our building blocks: *logic gates*

input		output
x	y	AND (x, y)
0	0	0
0	1	0
1	0	0
1	1	1

AND outputs 1 only
if **ALL** inputs are 1


AND



input		output
x	y	XOR (x, y)
0	0	0
0	1	1
1	0	1
1	1	0

OR outputs 1 if
ANY input is 1

OR

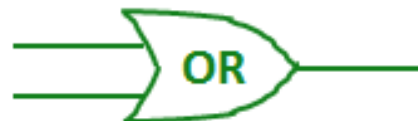

input	output
x	NOT (x)
0	1
1	0

NOT reverses
its input

NOT



Our building blocks: *logic gates*

input		output
x	y	AND (x, y)
0	0	0
0	1	0
1	0	0
1	1	1

AND outputs 1 only
if **ALL** inputs are 1


AND **ALL**



input		output
x	y	OR (x, y)
0	0	0
0	1	1
1	0	1
1	1	1

OR outputs 1 if
ANY input is 1

OR **ANY**

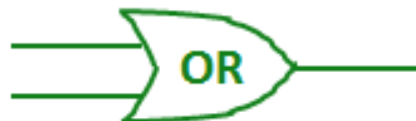

input	output
x	NOT (x)
0	1
1	0

NOT reverses
its input

NOT



Claim !?

We need only these three building blocks to compute anything at all

I need proof!



AND outputs 1 iff **ALL** its inputs are 1

ALL
must be 1



OR outputs 1 iff **ANY** input is 1

ANY
can be 1



NOT reverses its input

From gates to *circuits*...

What inputs make this circuit output 1?

CircuitVerse Project Circuit Tools Help hw5startercircuits

XOR fulladder ripplecarry prime optprime mult exrails ex

CIRCUIT ELEMENTS

Eight 3-bit inputs

Decoders & Plexer
Sequential Elements
Memory Elements
Test Bench
Misc

PROJECT PROPERTIES

Project : hw5startercircuits
Circuit : ex
Clock Time : 500
Clock Enabled : ☒
Lite Mode : ☐

Delete Edit

000
001
010
011
100
101
110
111

This is an example circuit, showing the interaction of AND, OR, and NOT

output

inputs			output of our circuit
x	y	c	
0	0	0	?
0	0	1	?
0	1	0	?
0	1	1	?
1	0	0	?
1	0	1	?
1	1	0	?
1	1	1	?

Row A
Row B
Row C
Row D
Row E
Row F
Row G
Row H

Too small to read...

What inputs make this circuit output 0?

From gates to *circuits*...

What inputs make this circuit output 1?

CircuitVerse Project Circuit Tools Help hw5startercircuits

XOR fulladder ripplecarry prime optprime mult exrails ex

CIRCUIT ELEMENTS

Eight 3-bit inputs

Decoders & Ples
Sequential Elem
Memory Element
Test Bench
Misc

PROJECT PRO
Project : hw5star
Circuit : ex
Clock Time : 500
Clock Enabled :
Lite Mode :
Delete
Edit

000
001
010
011
100
101
110
111

This is an example circuit, showing the interaction of AND, OR, and NOT

x y c

output

inputs


x	y	c
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

circuit output

Each output is 0 or 1

What inputs make this circuit output 0?

CircuitVerse!

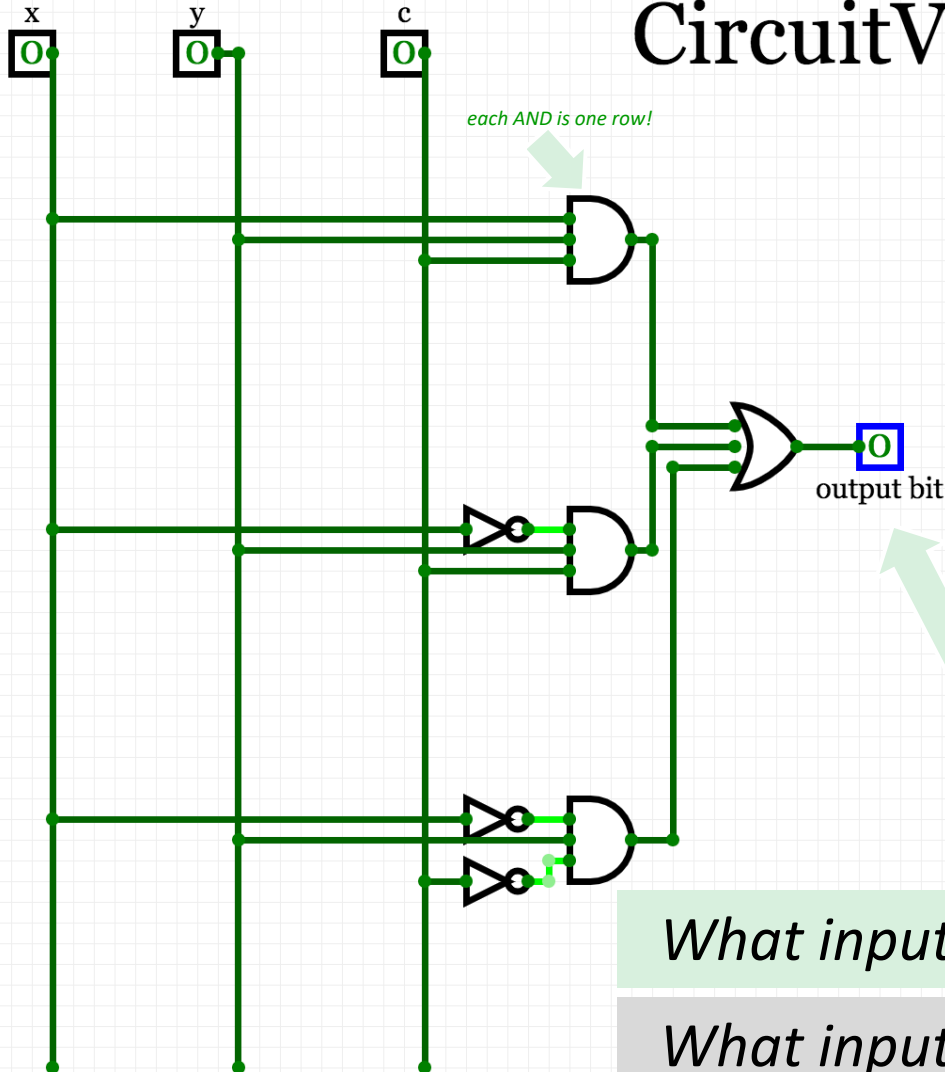

inputs				
x	y	c	output(x,y,c)	
0	0	0	?	Row A
0	0	1	?	Row B
0	1	0	?	Row C
0	1	1	?	Row D
1	0	0	?	Row E
1	0	1	?	Row F
1	1	0	?	Row G
1	1	1	?	Row H


What inputs make this circuit output 1?

What inputs make this circuit output 0?

Rails

There is **NO** difference between these two circuits!


How?

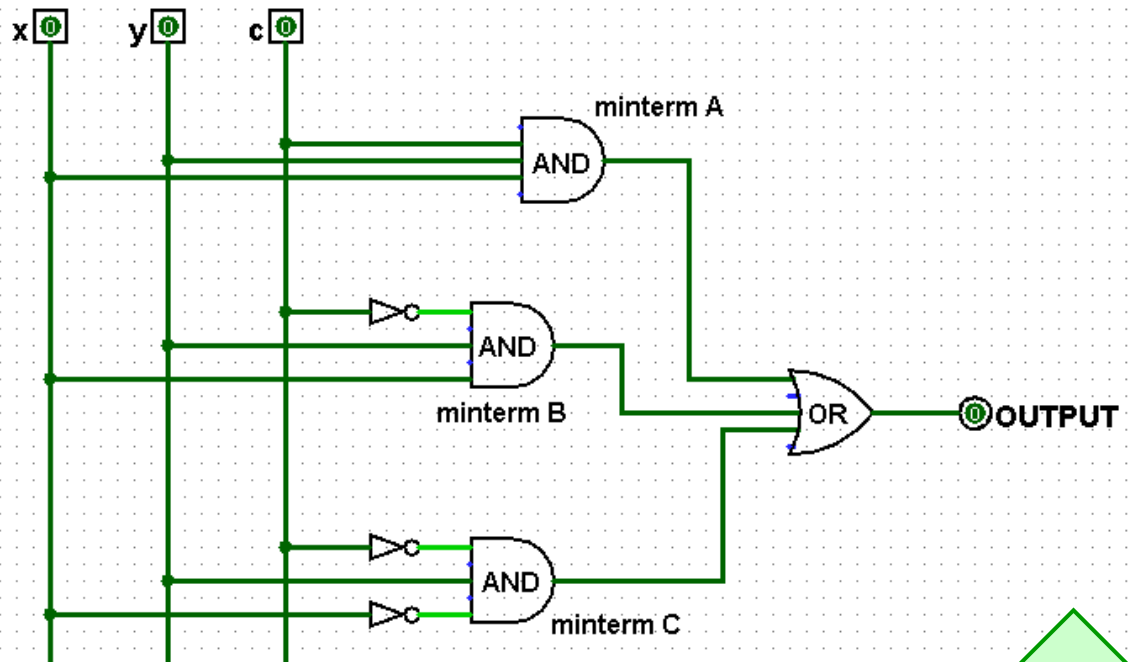

Any *disadvantages* of this "**rails**" approach?

Any *advantages*?

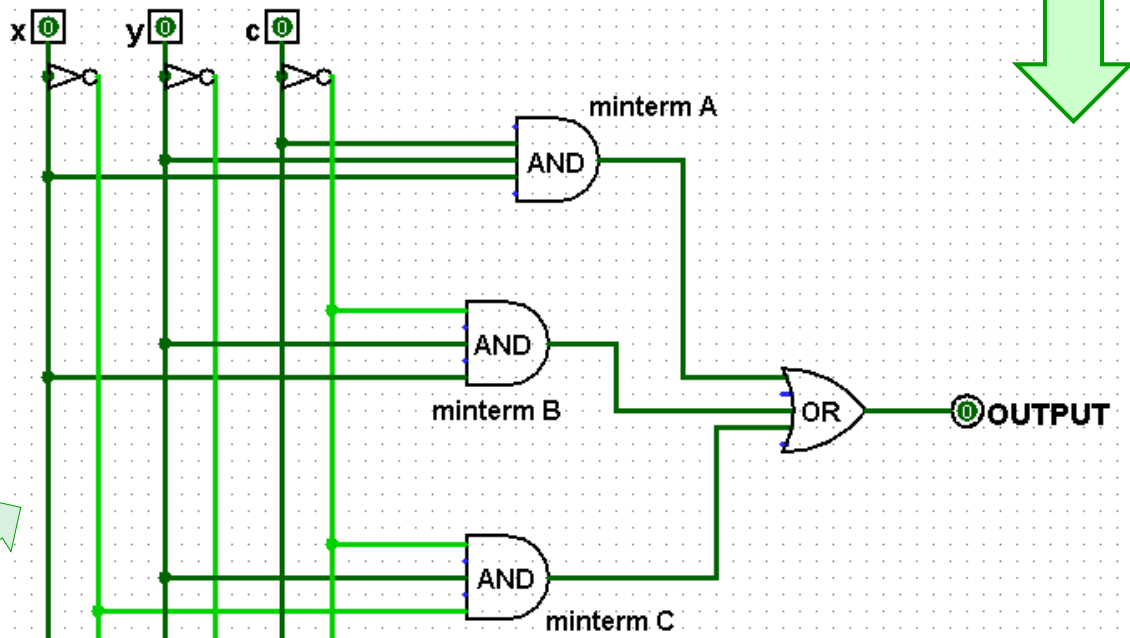using rails for **not x**, **not y**, **not c**




Try it!

Names: _____

Fill in the function values for this circuit (the truth table)

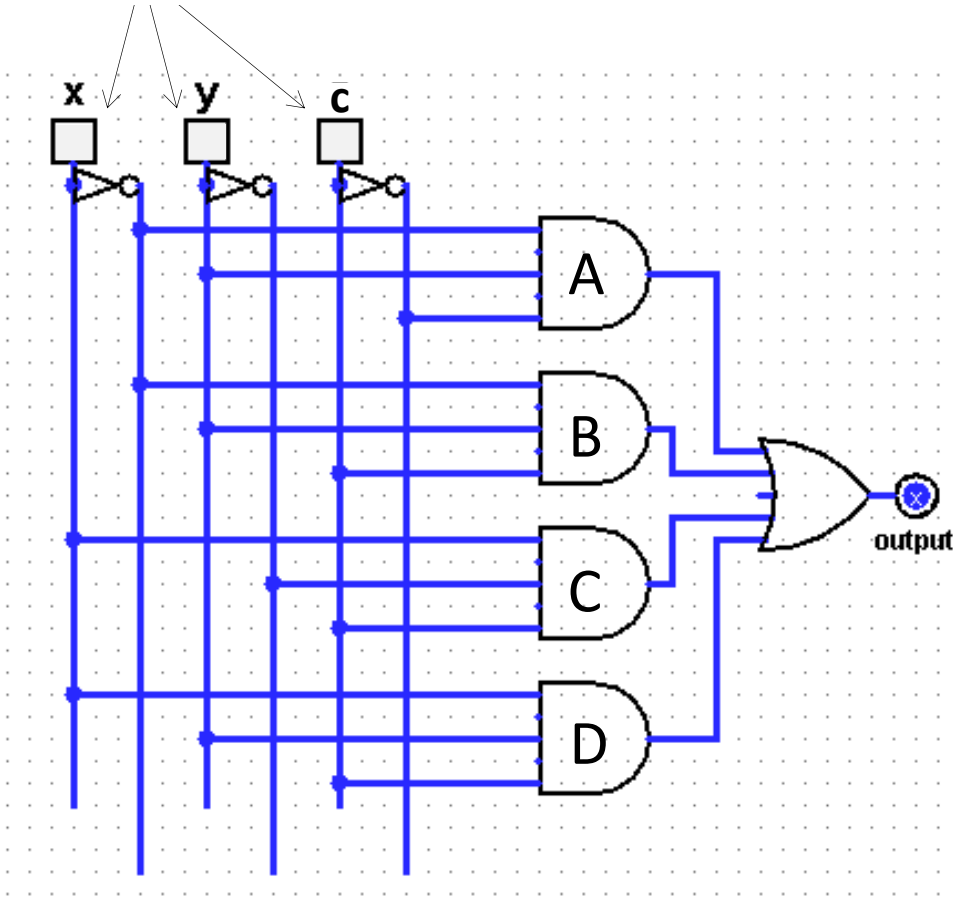Each input x, y, and z can **independently** be 0 or 1, for *eight* total possible inputs:



inputs			circuit output	Gate?
x	y	c		
0	0	0		
0	0	1		
0	1	0	1	A
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

Each output is 0 or 1

together

(1) This circuit uses 8 logic gates – *how many of each?* AND ____ OR ____ NOT ____

(2) Follow upstream from A. What x,y,c bits make A output 1 ? (and why is that all we need to know for A?)


(3) For **each** possible input, write the circuit output in the truth table above.

(ec) Could this circuit use **fewer** logic gates? *If so, how?!* *If not, how do you know?!*

This circuit is prime!



Real! logic gates...

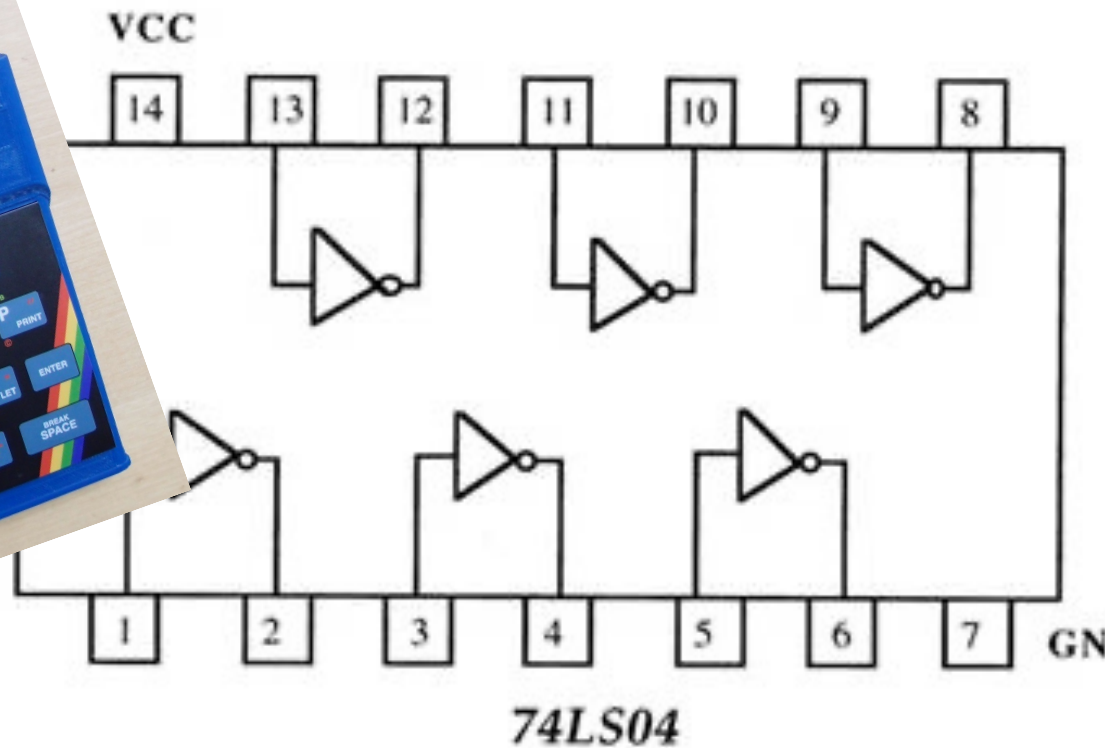


74LS04 NOT gate

Try it!

Try this on the other page first...

Fill in the function values for this circuit (the truth table)

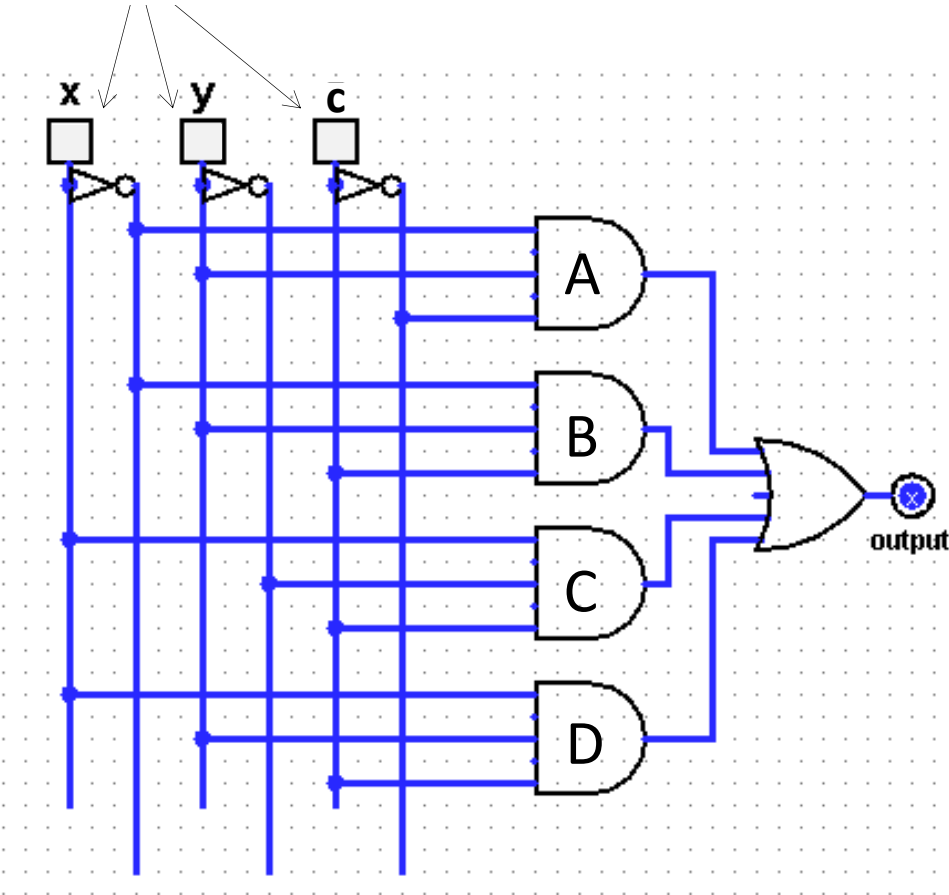Each input x, y, and z can **independently** be 0 or 1, for *eight* total possible inputs:



inputs			circuit output	Gate?
x	y	c		
0	0	0	0	
0	0	1	0	
0	1	0	1	A
0	1	1	1	B
1	0	0	0	
1	0	1	1	C
1	1	0	0	
1	1	1	1	D

Each output is 0 or 1

together

- (1) This circuit uses 8 logic gates – *how many of each?* AND 4 OR 1 NOT 3
- (2) Follow upstream from A. What x,y,c bits make A output 1? 010 Why is that all we need to know for A?)
- (3) For **each** possible input, write the circuit output in the truth table above.

two can be combined!

Could this circuit use ***fewer*** logic gates?

If so, how?!

If not, how do you know?!

see above!


This circuit is prime!



The claim...



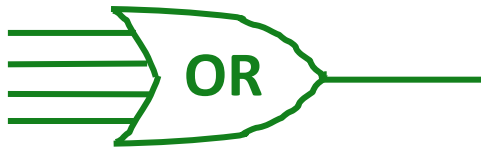AND outputs 1 only if
ALL its inputs are 1



OR outputs 1 if
ANY input is 1



NOT reverses its input

We need only these three building blocks
to compute *anything at all*


I need
proof!



The proof... !



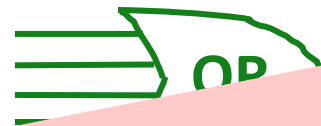AND outputs 1 only if
ALL its inputs are 1



We prove this **constructively** using
the **minterm expansion principle**.



NOT reverses its input

We need only these three building blocks
to compute ***anything at all***

I need
proof!



A constructive proof...

i Specify a **truth table** defining **any** function you want

input		output
x	y	$f(x, y)$
0	0	0
0	1	1
1	0	1
1	1	0

ii For each input row whose output needs to be 1, build an **AND** circuit that outputs 1 only for that specific input!

iii OR them all together


Hey! This is a 3-i'ed proof!



A constructive proof...

i Specify a **truth table** defining **any** function you want

input		output
x	y	$f(x, y)$
0	0	0
0	1	1
1	0	1
1	1	0

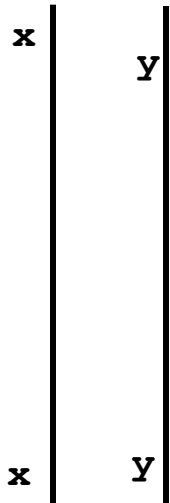


The ZERO rows ALREADY work –
with no connections at all !

ii For each input row whose output needs to be 1, build an **AND** circuit that outputs 1 only for that specific input!

iii OR them all together

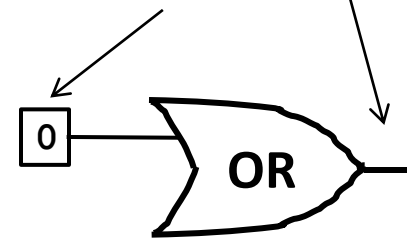We ensure this **OR**
outputs zero by
default.




A constructive proof...

i Specify a **truth table** defining **any** function you want

ii For each input row whose output needs to be 1, build an **AND** circuit that outputs 1 only for that specific input!

input		output
x	y	$f(x, y)$
0	0	0
0	1	1
1	0	1
1	1	0

iii OR them all together

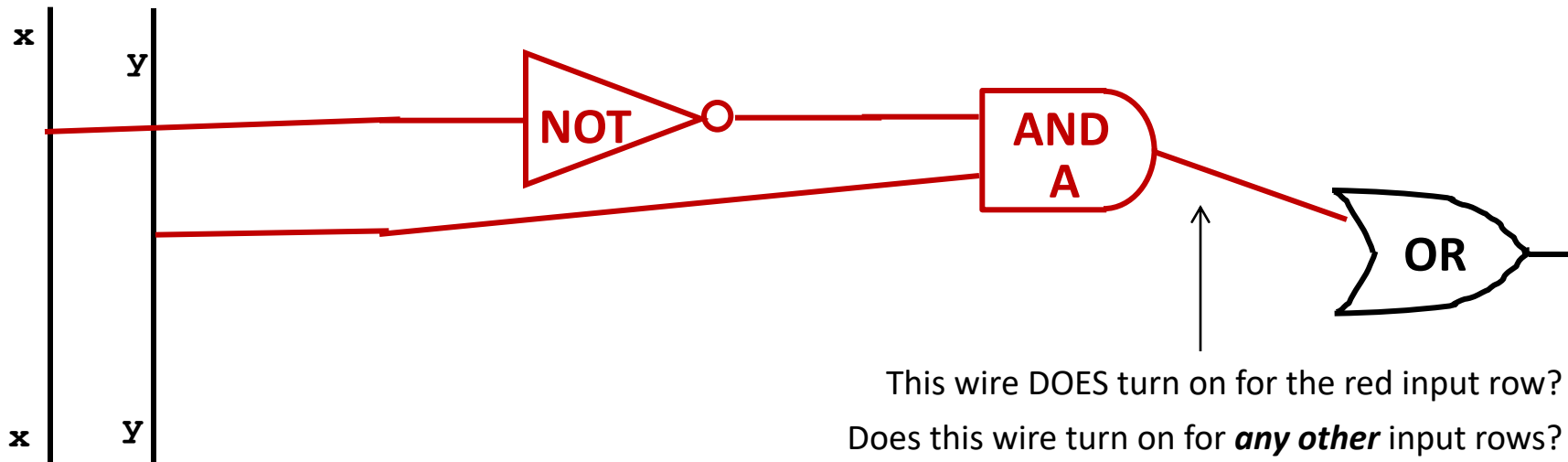


A constructive proof...

i Specify a **truth table** defining **any** function you want

ii For each input row whose output needs to be 1, build an **AND** circuit that outputs 1 only for that specific input!

input		output
x	y	$f(x, y)$
0	0	0
A 0	1	1
B 1	0	1
1	1	0

iii OR them all together

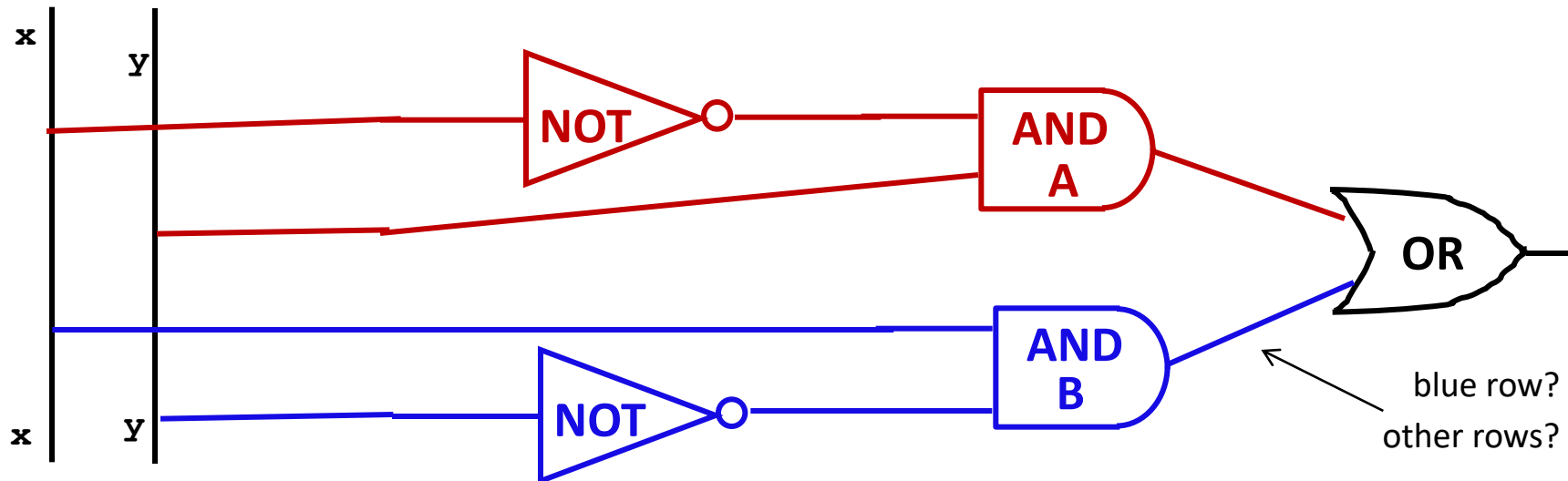


A constructive proof...

(i) **MINTERM expansion principle**

For each input row whose output needs to be 1, build an **AND** circuit that outputs 1 *for that specific input!*

This is a *constructive* proof that AND, OR, NOT suffice to build **any** function of bits!

all together

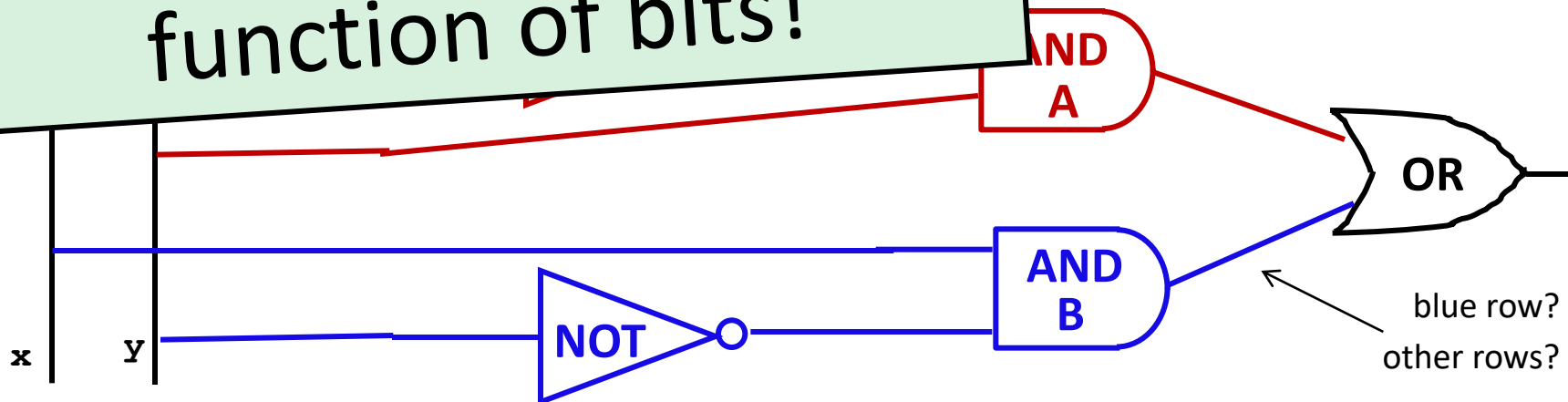


A constructive proof...

and ALL functions are just functions of bits !


expansion principle

This is a *constructive* proof that AND, OR, NOT suffice to build **any** function of bits!

all together

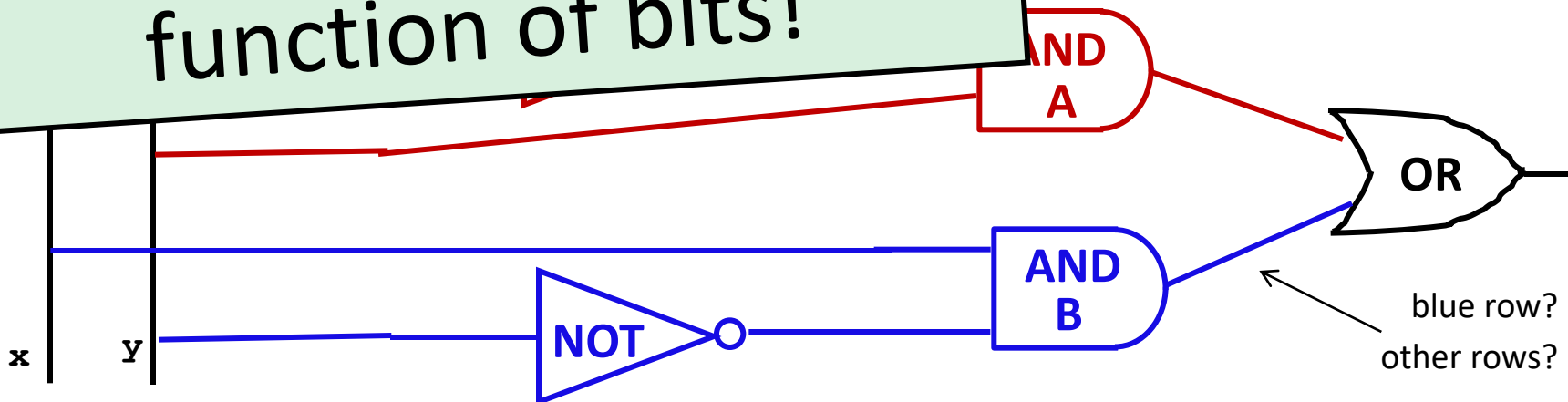

Minterm Expansion Principle

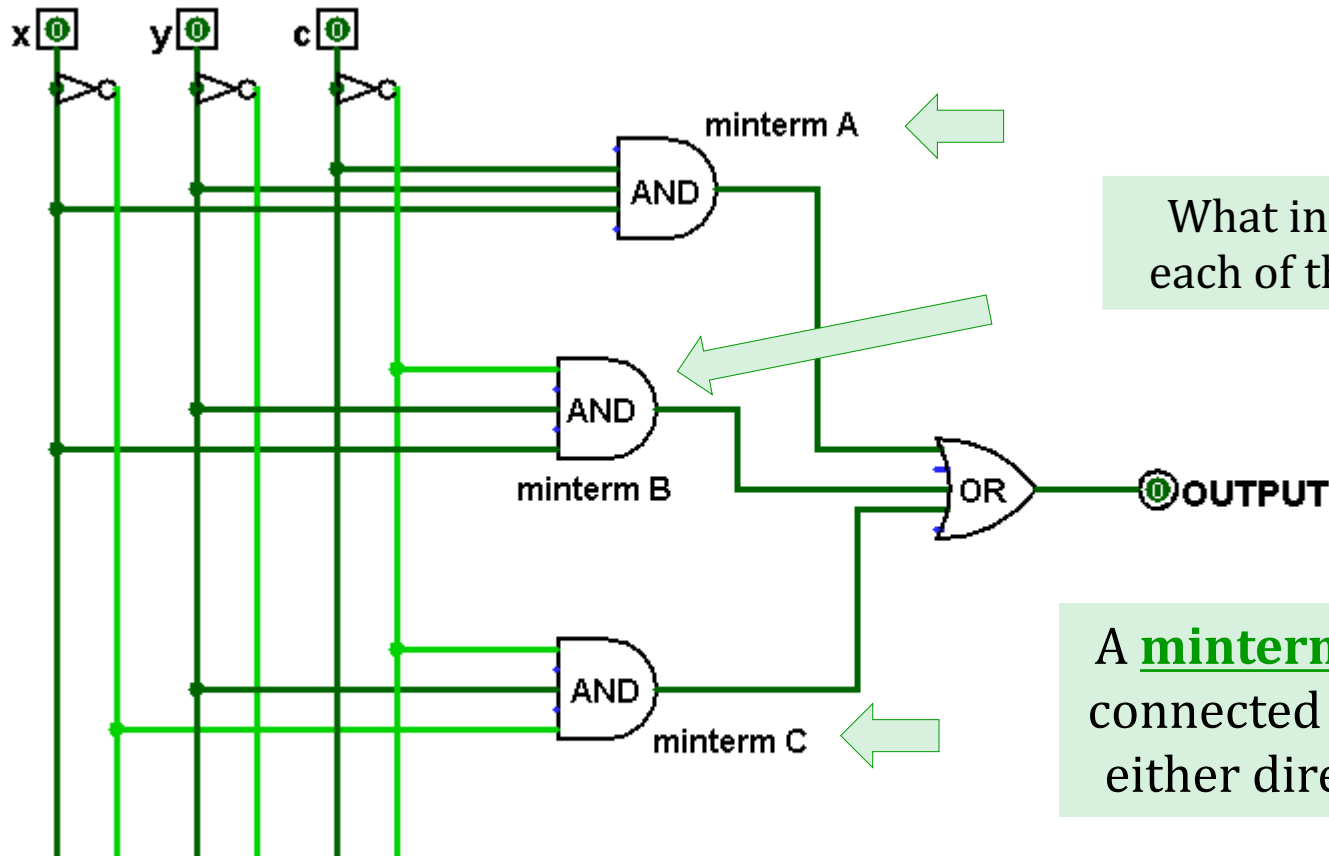

What input "activates"
each of these minterms?


we did this before!

A **minterm** is an **AND** gate
connected to *all* input bits -
either directly or inverted

For each **1** in the truth
table, use one AND gate,
called a **minterm**.

Each minterm selects *one* input:

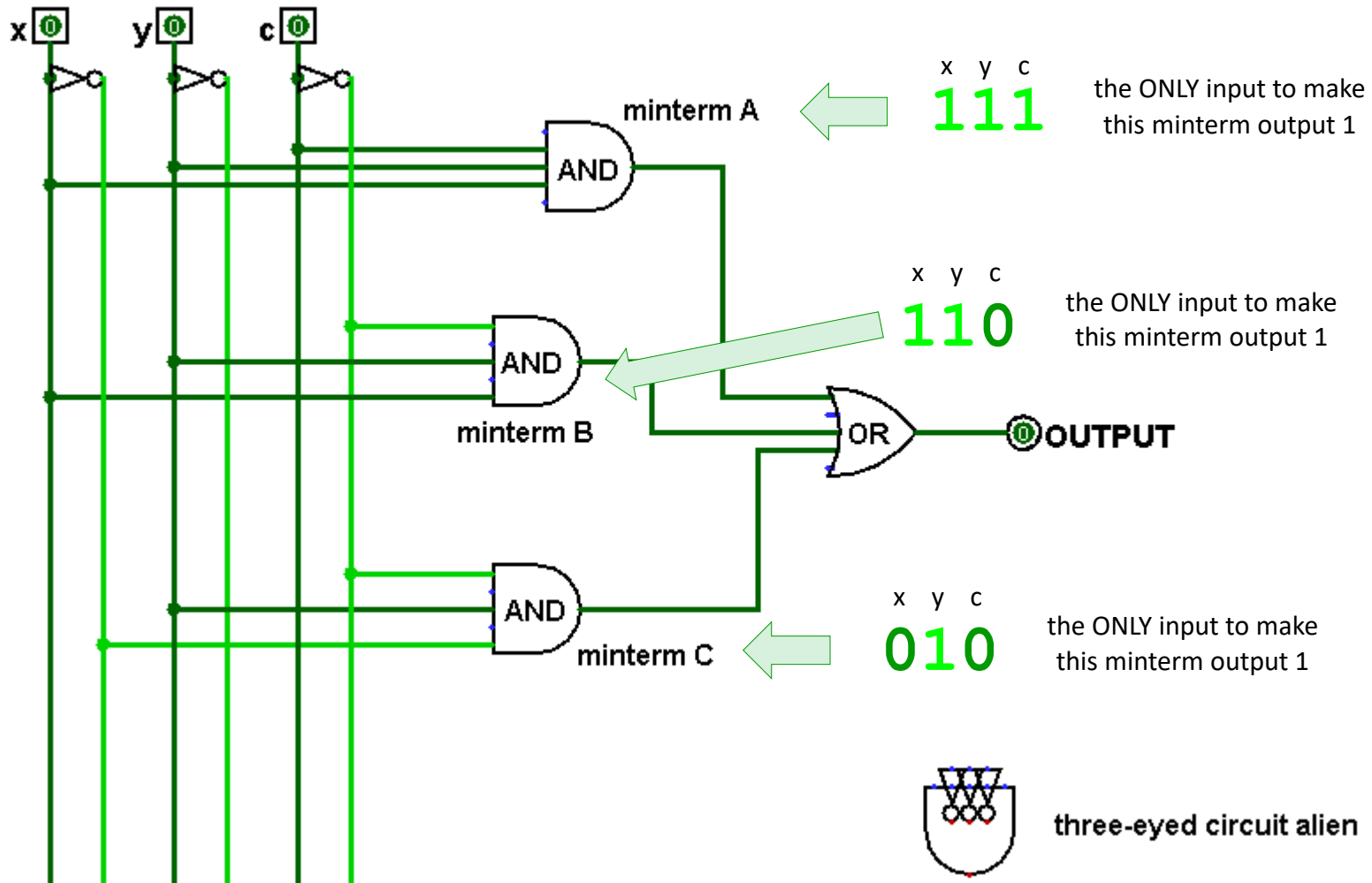
a *minterm* is an AND gate that "*selects*" a single input row



Minterm Expansion Principle

Looks a little
wiry to me!



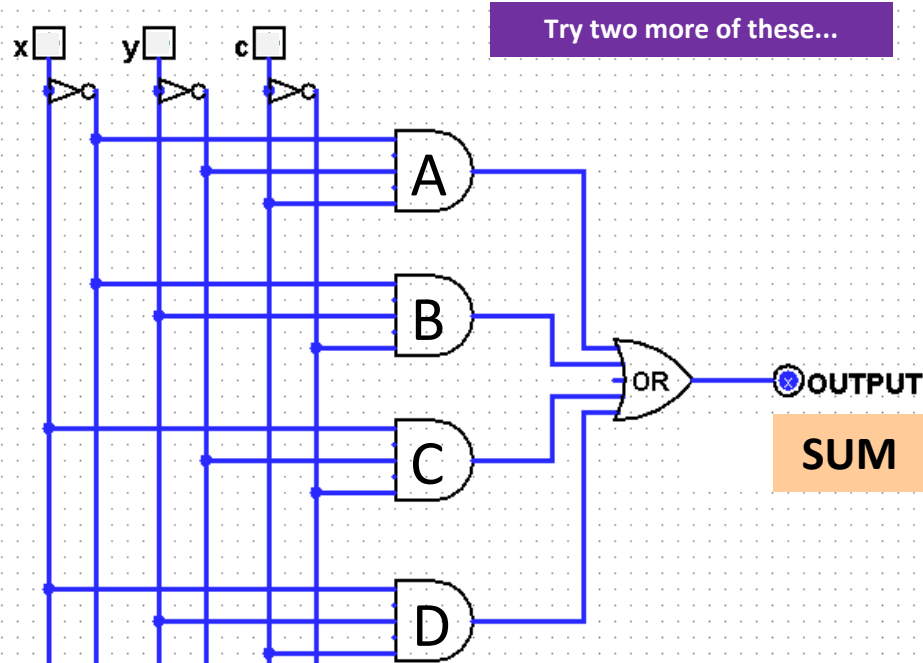

Try two more of these...


input			output
x	y	c	
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Take 2...

(1) Fill in all 8 rows of the function values (truth table) for this circuit...

Hint: Determine the input that turns each AND gate – each *minterm* -- to **True**

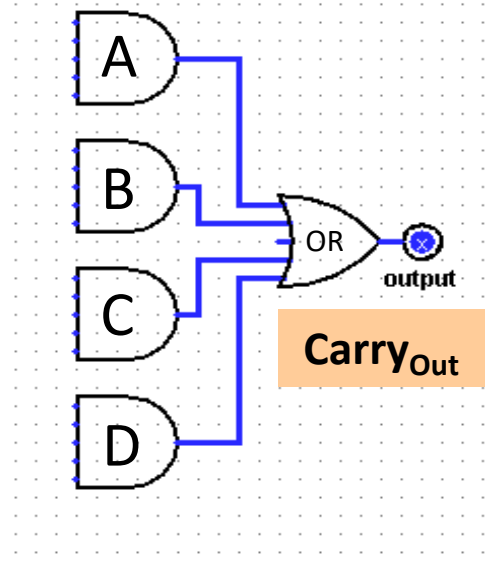(2) Draw the upstream wires that will implement this function as a circuit.




input			output
x	y	c	
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	A 1
1	0	0	0
1	0	1	B 1
1	1	0	C 1
1	1	1	D 1

(Extra #1) Any gates you can optimize away here?

(Extra #2) How could you replace the OR with only ANDs and NOTs?
ORs aren't needed!

(Extra #3) How do the two circuits on this page implement **addition of any two binary #s!?**
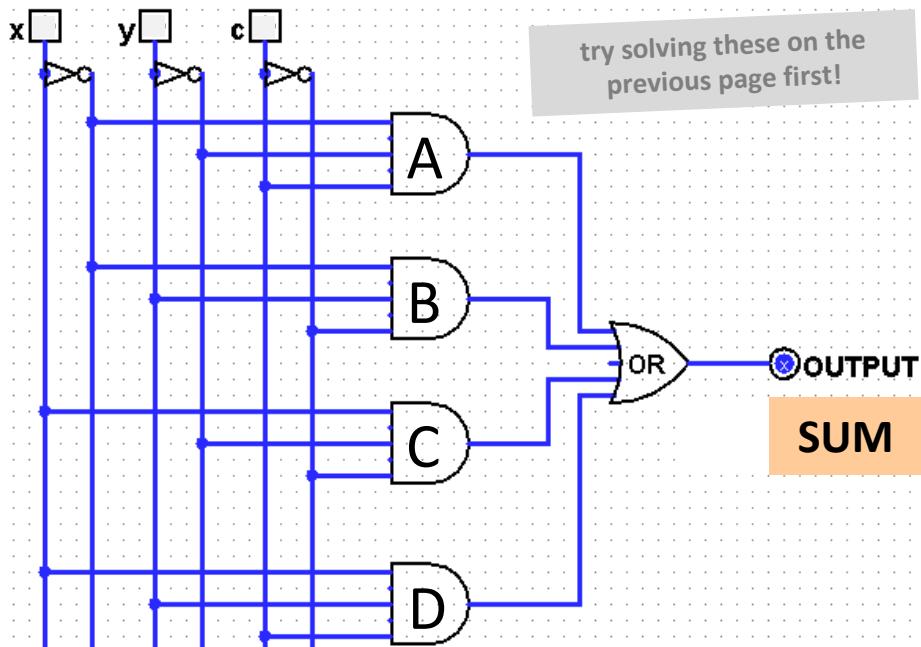
$$\begin{array}{r}
 111 \\
 1011 \quad x \\
 + 1111 \quad y \\
 \hline
 11010
 \end{array}$$




input			output	
x	y	c		
0	0	0		0
0	0	1	A	1
0	1	0	B	1
0	1	1		0
1	0	0	C	1
1	0	1		0
1	1	0		0
1	1	1	D	1

Take 2...

(1) Fill in all 8 rows of the function values (truth table) for this circuit...

Hint: Determine the input that turns each AND gate – each *minterm* -- to **True**

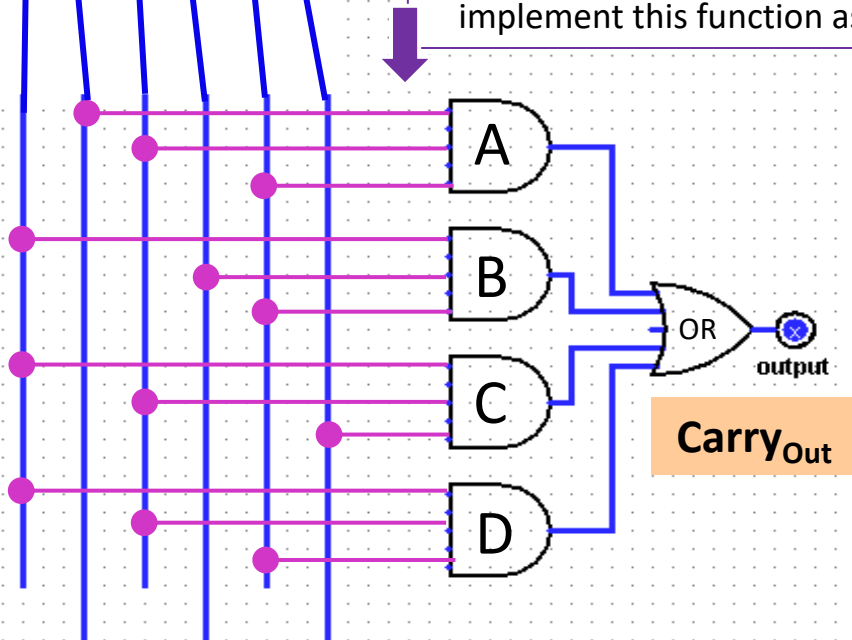(2) Draw the upstream wires that will implement this function as a circuit.



input			output	
x	y	c		
0	0	0		0
0	0	1		0
0	1	0		0
0	1	1	A	1
1	0	0		0
1	0	1	B	1
1	1	0	C	1
1	1	1	D	1

(Extra #1) Any gates you can optimize away here?

(Extra #2) How could you replace the OR with only ANDs and NOTs?
ORs aren't needed!

(Extra #3) How do the two circuits on this page implement **addition of any two binary #s!?**

```


  1 1 1
 1011 x
+ 1111 y
-----
11010

```

input		output
x	y	OR (x, y)
0	0	0
0	1	1
1	0	1
1	1	1

OR else ?!

Can you get rid of ORs by using only NOTs and ANDs?

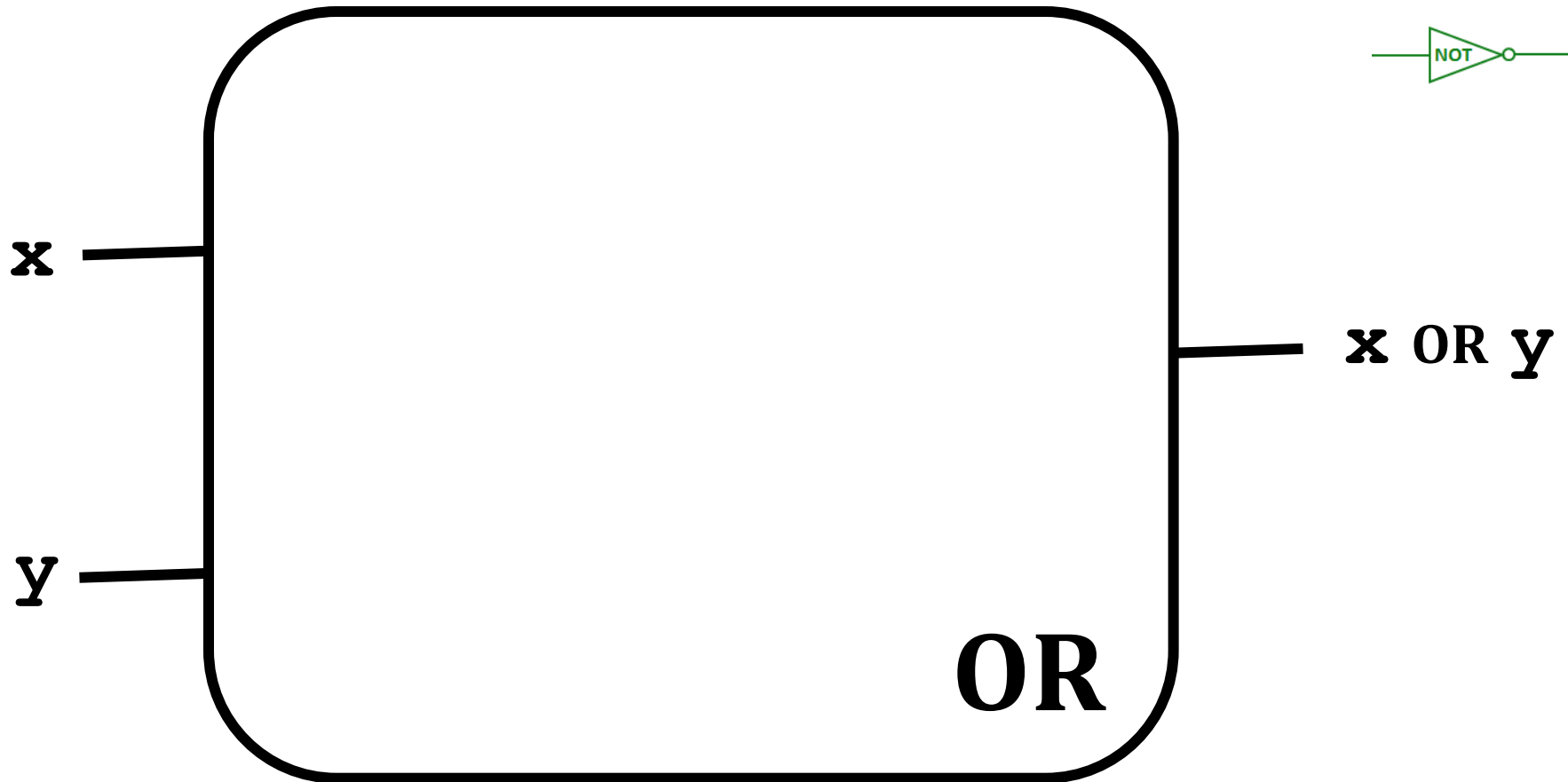

Lab5: *adders!*

A **full adder** sums three input bits to create a 2-bit **binary** output

x	y	c _{in}	carry _{out}	sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

3 bits of input
(considered individually)

2 bits of output
(considered a binary #)



these columns
look familiar!

Full Adder (FA)

the full adder

