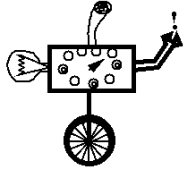


CS 60




Logic Synthesis

November 9, 2001

Synthesizing Switching Functions

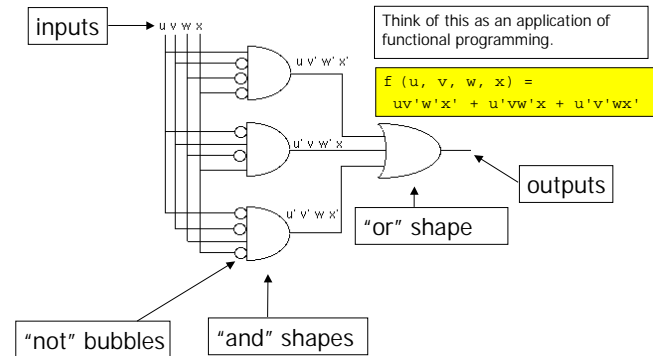A "logic circuit" is composed of switching functions



SOP and Minterm forms

$$f(u, v, w, x) = u'v'w'x' + u'vw'x + u'v'wx'$$

- This is called a **SOP** (sum-of-products) form. In this case, a "product" means product of variables or complemented variables.
- It is also a **minterm** form. A minterm is a product that uses *all* of the variables.
- Not every SOP is a minterm form.

Truth Table

$$f(u, v, w, x) = u'v'w'x' + u'vw'x + u'v'wx'$$

u	v	w	x	f
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

Note the Connection

$$f(u, v, w, x) =$$

$$u v' w' x'$$

$$+ u' v w' x$$

$$+ u' v' w x'$$

u	v	w	x	f
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

The "1" rows of the truth table correspond exactly to the minterms!

Shorthands

$$f(u, v, w, x) =$$

$$u v' w' x'$$

$$+ u' v w' x$$

$$+ u' v' w x'$$

Show only the "1" rows (be careful)

u	v	w	x	f
0	0	1	0	1
0	1	0	1	1
1	0	0	0	1

Represent whole table by a set of "minterm numbers":

{2, 5, 8}

Represent whole table by a single numeral: 0010010010000000

Ways to Specify Boolean Functions

- Logic circuit
- Functional expression
 - SOP form
 - Minterm expansion
- Truth table
- Compressed truth table
- Index number
- Karnaugh map

Counting Functions

- The following are all equal:
 - The number of boolean functions of n variables.
 - The number of ways to assign 0 or 1 to the 2^n rows of the truth table.
 - The number of subsets of $\{0, 1, 2, \dots, 2^n - 1\}$

Example

- Verbal description:

Implement a "mod 3 adder using logic gates"

- A definition of mod3 addition:

$$f(a, b) = (a+b)\%3$$

where $a, b \in \{0, 1, 2\}$

Tabulate definition of function

$(x+y)\%3$	0	1	2
0	0	1	2
1	1	2	0
2	2	0	1

Encode sets into bits

- Set to be encoded: $\{0, 1, 2\}$
- Chosen encoding (among many):

$0 \rightarrow 00$
 $1 \rightarrow 01$
 $2 \rightarrow 10$

Transcribe the Function to the Encoded Values

Function	Encoding			
$(x+y)\%3$	0	1	2	
0	0	1	2	$0 \rightarrow 00$
1	1	2	0	$1 \rightarrow 01$
2	2	0	1	$2 \rightarrow 10$

↓

Encoded Function	uv		
	00	01	10
00	00	01	10
01	01	10	00
10	10	00	01

Here first argument becomes uv, second becomes xy.

Split the Encoded Function into individual switching functions

Encoded Function		uv		
		00	01	10
	00	0 0	0 1	1 0
xy	01	0 1	1 0	0 0
	10	1 0	0 0	0 1

Call this f_1 .

		uv		
		00	01	10
	00	0	0	1
xy	01	0	1	0
	10	1	0	0

left bit

		uv		
		00	01	10
	00	0	1	0
xy	01	1	0	0
	10	0	0	1

right bit

Call this f_2 .

The resulting switching functions generally will only be *partially* specified.

		uv		
		00	01	10
	00	0	0	1
xy	01	0	1	0
	10	1	0	0

u	v	w	x	f_1	f_2
0	0	0	0	0	0
0	0	0	1	0	1
0	0	1	0	1	0
0	0	1	1	?	?
0	1	0	0	0	1
0	1	0	1	1	0
0	1	1	0	?	?
0	1	1	1	?	?
1	0	0	0	1	0
1	0	0	1	0	0
1	0	1	0	0	1
1	0	1	1	?	?
1	1	0	0	?	?
1	1	0	1	?	?
1	1	1	0	?	?
1	1	1	1	?	?

		uv		
		00	01	10
	00	0	1	0
xy	01	1	0	0
	10	0	0	1

As the unspecified values will never occur, we can give the function either value 0 or 1.

For the time being, let's just make them all 0.

Now we can "read off" an expression for each function.


$$f_1(u, v, w, x) = u'v'wx + u'vw'x' + uv'wx'$$

u	v	w	x	f_1	f_2
0	0	0	0	0	0
0	0	0	1	0	1
0	0	1	0	1	0
0	0	1	1	?	?
0	1	0	0	0	1
0	1	0	1	1	0
0	1	1	0	0	0
0	1	1	1	?	?
1	0	0	0	1	0
1	0	0	1	0	0
1	0	1	0	0	1
1	0	1	1	?	?
1	1	0	0	?	?
1	1	0	1	?	?
1	1	1	0	?	?
1	1	1	1	?	?

Exercise: "read off" the expression for f_2 .


u	v	w	x	f_1	f_2
0	0	0	0	0	0
0	0	0	1	0	1
0	0	1	0	1	0
0	0	1	1	?	?
0	1	0	0	0	1
0	1	0	1	1	0
0	1	1	0	0	0
0	1	1	1	?	?
1	0	0	0	1	0
1	0	0	1	0	0
1	0	1	0	0	1
1	0	1	1	?	?
1	1	0	0	?	?
1	1	0	1	?	?
1	1	1	0	?	?
1	1	1	1	?	?

Realize each function by gates

 

Check by Simulating Circuit

 (Try all combinations; one combination is shown)



Rex Implementation

```

encode(0) => [0, 0];
encode(1) => [0, 1];
encode(2) => [1, 0];

decode([0, 0]) => 0;
decode([0, 1]) => 1;
decode([1, 0]) => 2;
decode([x, y]) => "error, should not occur";

add3(i, j) = (i+j)%3;

addByCircuit(i, j) = decode(circuit(encode(i), encode(j)));

circuit([u, v], [w, x]) =>
[
  !u && !v && w && !x
  || !u && v && !w && x
  || u && !v && !w && !x,

  !u && !v && !w && x
  || !u && v && !w && !x
  || u && !v && w && !x];

```

Testing Code

```

test(addByCircuit(0, 0), add3(0, 0));
test(addByCircuit(0, 1), add3(0, 1));
test(addByCircuit(0, 2), add3(0, 2));

test(addByCircuit(1, 0), add3(1, 0));
test(addByCircuit(1, 1), add3(1, 1));
test(addByCircuit(1, 2), add3(1, 2));

test(addByCircuit(2, 0), add3(2, 0));
test(addByCircuit(2, 1), add3(2, 1));
test(addByCircuit(2, 2), add3(2, 2));

```