

State Machines In Hardware


December 3, 2001

State Machines in Hardware


- A hardware implementation of a state machine needs two major parts
 - Finite memory (to remember which state we're currently in)
 - Logic to determine what the next state should be, given the current state and the next input.
- We can encode an arbitrary set of states just as we encode any set, in terms of some number of bits.
- We implement the next-state function using *combinational* logic gates: given an encoded version of the current state and the input, produce the encoding of the next state.

Next-State Sequential Logic for a Finite-State Machine

 
Combinational logic for the next-state function (gates)




Example: A Multiples-of-3 Machine

 

 Suppose we encode the state set using 2 bits, thus:



Transition Table

 

The next state is summarized by the following table:


next state	input	
current state	0	1
00	00	01
01	10	00
10	01	10

But we already know how to implement such a table in logic!


Karnaugh Maps

next vw	input (x)	
current state (vw)	0	1
00	00	01
01	10	00
10	01	10


next v:

 

next w:

 


Logic Diagram

 


Representing a Discrete Sequence in Continuous Time

- From our viewpoint, time appears to be a continuous variable.
- For a digital sequence, we want discrete values $[x_0, x_1, x_2, x_3, \dots]$, not a continuous function $x(t)$.
- The typical way to handle this is to use a *clock*.
- The continuous sequence is "sampled" at regularly-spaced times, when the clock "ticks".


Sampling a Signal

 

Sampling a Signal

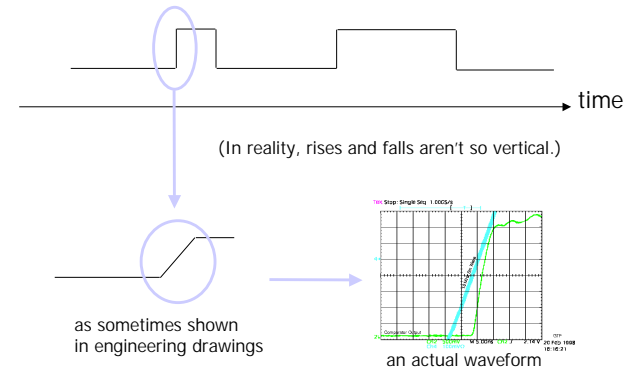

Sampling a Signal

 


Clock Rate

- The clock is analogous to the conductor of a symphony orchestra: it keeps all of the players in synch.
- The rate at which the clock ticks is the quoted rate of the processor, e.g. 500 MHz (500,000,000 ticks per second).
- It is possible to design systems that don't have clocks ("asynchronous systems") but these are rare.

The Basic Unit of Memory is the Flip-Flop


- A flip-flop remembers **one bit**, either a 0 or 1.
- The presence of a synchronizing clock is assumed.
- The bit is held from one clock-tick to the next.
- Each time the clock ticks, whatever value (0 or 1) exists at the flip-flop's input is **remembered**; the old value is lost.

Flip-Flop Behavior

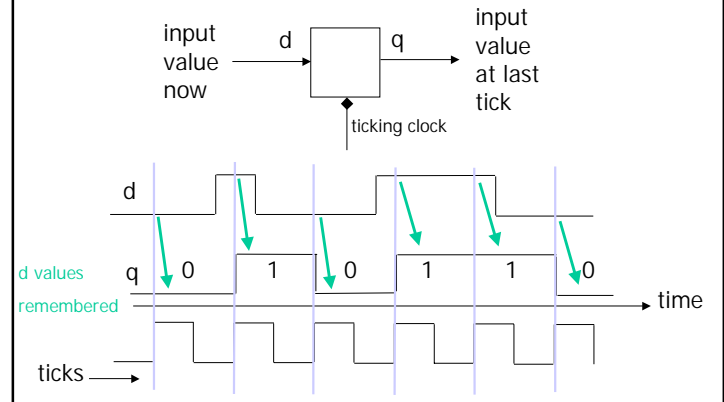


Inside a Flip-Flop

 
- A flip-flop can be constructed from ordinary gates (which have some associated switching *delay*) and feed-back connections.
- A first approximation, called a **clocked latch**, is:



Clocked Latch Behavior

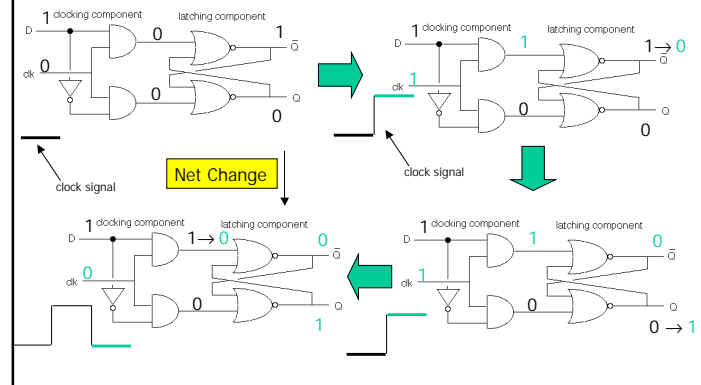


Edge-Triggered Flip-Flop

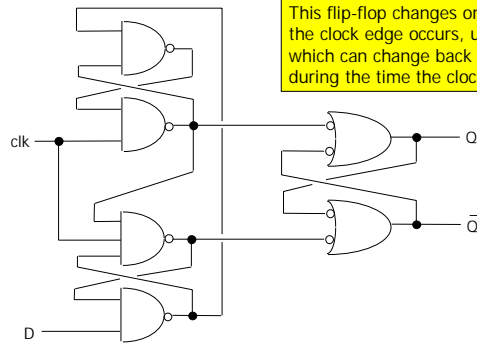

This flip-flop changes only when the clock edge occurs, unlike the latch, which can change back and forth during the time the clock is 1.

Analysis is left to the reader.

Logic Diagram in Context

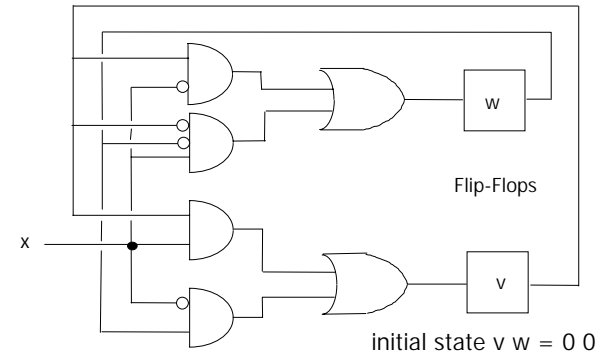


initial state $v\ w = 0\ 0$

Output Considerations

- We need to drive the output from the encoded state.
- The output is coded, just like the state and input.
- Let's say that the output is z which has value 1 for accepting, 0 for rejecting.
- Since the only accepting state is 00, the output function is

$$z = v'w'$$

Final Circuit, with Output

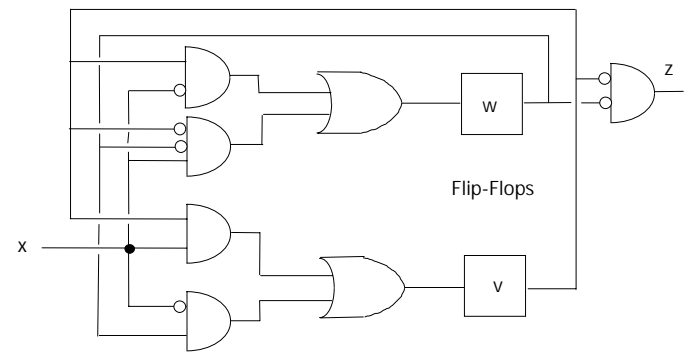

initial state $v\ w = 0\ 0$

Physical Computers

(as distinguished from
"virtual" computers, such as
Turing machines)

Computer Components


- Finite-state machines
- Combinational logic
- Buses

Register


- A register is a finite-state machine that remembers values as bit vectors.
- A register may perform other functions as well:
 - Clearing
 - Incrementing, decrementing
 - Shifting

Simplest register

Remembers one bit = Flip-Flop

 


Two-Bit Register

 


Inputs to a Register

 
- Data (e.g. value to be remembered)
- "Strobe": function to be performed
- Simplest register has no strobe inputs



Register with Strobe Input

 


Register with Two Strobe Inputs

 

1-bit register with load & clear

 
- {clear, load} is 1-hot (never both 1 simultaneously)



Strobe Possibilities


- load
- clear
- increment
- decrement
- complement
- left-shift
- right-shift

Register Transfer

 

Equivalent Java: `A = B;`


Selective Register Transfer

 


See also:
Boole/Shannon
Expansion

Equivalent Java: `A = P ? B : C;`

4-way selection

 

Selection Using a Bus

 


For this to make sense, we need another register output value separate from 0,1.

Implementing Bus Connection

- We can't simply use AND-gates; the output of an AND will *always* be 0 or 1.
- Connecting together wires with 0 and 1 simultaneously would be fatal.
- For the bus, use a third possible output value:
 - "high impedance", "high Z", or
 - NC (no connection)


3-State Buffer

 

output = control ? data : NC;


No Connection


Selection using Bus

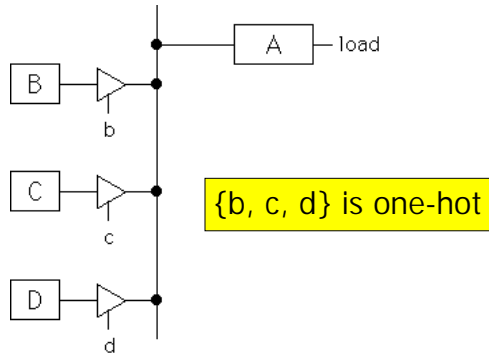

Bus vs. Multiplexor

- The bus-type connection allows selection from a large number of inputs without requiring a multiplexor tree or other complex logic.

Computing using Combinational Functions

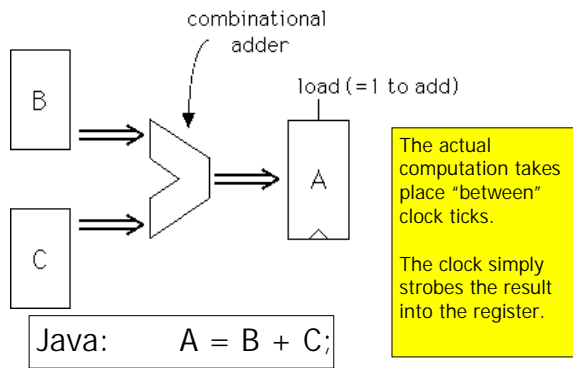

Next class:

ISC Processor Structure

