

Logic Simplification

Logic Expression Simplification

- Often it is possible to simplify function expressions from, say, their minterm form.
- This may be done by using various identities, as we know. But more systematic methods will be shown.

Simplification Example

3-argument
majority
function

v	w	x	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

minterm form: $\text{majority}(v, w, x) =$

Notice Certain "Adjacencies"

3-argument
majority function

v	w	x	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

These rows are "adjacent":
their variable combinations
differ in only 1 bit

$$\left. \begin{array}{l} v'wx \\ vw'x \\ vwx \end{array} \right\} = wx$$

$$\text{simplified majority}(v, w, x) = \boxed{wx} + vw'x + vwx'$$

$$\text{unsimplified majority}(v, w, x) = v'wx + vw'x + vwx' + \boxed{vwx}$$

Any other Adjacencies?

(ok to use a row more than once)

v	w	x	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Adjacencies can Overlap

3-argument
majority function

v	w	x	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$\text{simplified majority}(v, w, x) = wx + \boxed{vx} + vwx'$$

$$\text{unsimplified majority}(v, w, x) = v'wx + \boxed{vw'x} + vwx' + \boxed{vwx}$$

Any More Adjacencies?

3-argument
majority function

v	w	x	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$\text{simplified majority}(v, w, x) = wx + \overline{vx} + vw\overline{x}$$

$$\text{unsimplified majority}(v, w, x) = v'wx + \overline{vw'x} + vw\overline{x} + \overline{vwx}$$

Any More Adjacencies?

3-argument
majority function


v	w	x	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$\text{simplified majority}(v, w, x) = wx + vx + \overline{vw}$$

$$\text{unsimplified majority}(v, w, x) = v'wx + vw'x + \overline{vw\overline{x}} + \overline{vwx}$$


unsimplified majority
 
$$\text{majority}(v, w, x) = v'wx + vw'x + vw\overline{x} + vwx$$



simplified majority
 
$$\text{majority}(v, w, x) = wx + vx + vw$$



Simplified/Unsimplified Comparison for Majority

- Draw the diagrams
- Unsimplified:
 - 4 and-gates, 3 inputs each, some with negation,
 - 1 4-input or-gate
- Simplified:
 - 3 and-gates, 2 inputs each, none with negation,
 - 1 3-input or-gate

Implications for Simplified Functions

- If communicated by human, easier to understand, transfer
- If implemented as hardware, fewer gates, wires
- If implemented as software, fewer tests, execution steps

Visualizing Adjacencies


- Hypercube representation of truth table
- Karnaugh map representation

Hypercubes (connected vertices = adjacent)

1-dimension =
1 logical variable




2-dimensions =
2 logical variables

 

Hypercubes


3-dimensions =
3 logical variables

 


Sub-cubes

- An n -dimensional hypercube, for $n > 0$, has embedded in it a set of m -dimensional hypercubes, for each $m < n$.
- These are called the *sub-cubes* of the original hypercube.

Sub-cubes

 


Which sets are subcubes?

 

"Plotting" Functions on Hypercubes

$$\text{majority}(v, w, x) = v'wx + vw'x + vwx' + vwx$$


each minterm is a vertex

 

Simplified Functions on Hypercubes

$$\text{majority}(v, w, x) = wx + vx + vw$$

each term is a sub-cube

 

Sub-Cube Dimensions

- The **dimension of a sub-cube** is
 - n minus (number of variables in the corresponding product term)
- where n is the total number of variables.
- Examples: 3 variables total:
 - dimension 0: 3 variables
 - dimension 1: 2 variables
 - dimension 2: 1 variables
 - dimension 3: 0 variables (= constant 1)
- "More is less" (Greater dimension, fewer variables)


SOP Circuits (sum-of-products)

- An SOP will always correspond to
 - a set of **sub-cubes**
 - Collectively the vertices in the sub-cubes cover the "on" vertices.
 - The vertices in the sub-cubes don't cover any "off" vertices.
- Such a set is called a **cover** for the function.
- Each cover corresponds to a different gate implementation.

Simplified Covers


- In a fully-simplified SOP, each sub-cube will be **maximal**, in that it is not contained within another sub-cube.
- If instead it were properly contained in another sub-cube, then it could be **replaced** with that sub-cube.
- The replacement would have **fewer** variables, i.e. be simpler.

Maximality

 


This set of 2 sub-cubes covers the function.

Maximality

 

However the red sub-cube is not maximal.
 It should be extended to the blue sub-cube as shown for greater simplification.
 The resulting cover is simpler, even though one vertex is covered twice.


More-is-Less Principle

 

Making the sub-cubes as **large** as possible, makes the resulting product term as **small** as possible.


Einstein's Principle:

 Explanations should be made as simple as possible, but no simpler.




Including x by itself will not work!


Non-Uniqueness of Simplest Cover






 


Non-Uniqueness of Simplest Cover

 


4-D Hypercube

 


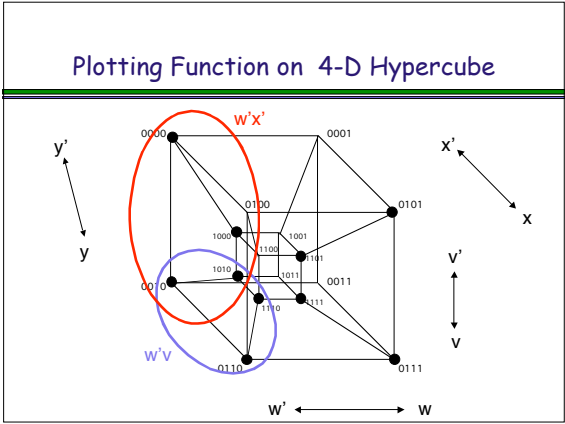   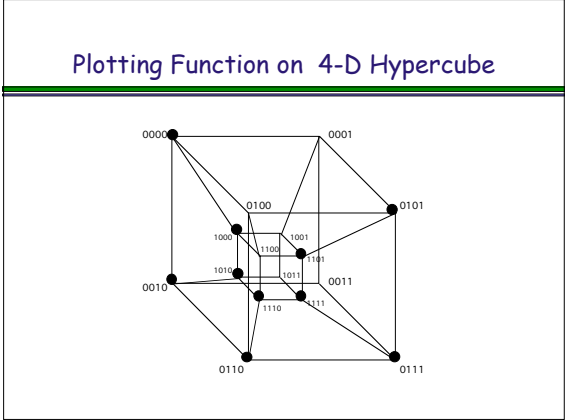 


Plotting Function on 4-D Hypercube

 


Plotting Function on 4-D Hypercube

 

Plotting Function on 4-D Hypercube

 

Plotting Function on 4-D Hypercube

 


Hypercube Function-Plotting Applet

An applet conceived by R. Keller and implemented by Ian Weiner, HMC '01 as a CS60 project.

<http://www.cs.hmc.edu/~keller/javaExamples/hypercube>

Check out dimensions > 4.

Gray Code on a Hypercube

 


Path touches every node without retracing any arc (Hamiltonian path).

Other CS uses of Hypercubes



- Distributed parallel computer topologies
- High-speed sorting

Non-CS uses of Hypercubes

 

Rotating hypercube from <http://casa.colorado.edu/~ajsh/sr/hypercube1.html>

  Hypercubes occur wherever independent attributes are found: e.g. genetics, "complexity"




Left: A 6-dimensional hypercube representing a genetic sequence space. From Manfred Eigen, *Steps toward life*, Oxford U. Press, 1992, p. 94.


Above: Hypercube representation of fitness landscape of mutants. From Stuart A. Kauffman, *The origins of order*, Oxford U. Press, 1993, p. 42.

More Hypercube Projections

5-D

 

15-D

 

From: <http://www.cs.reading.ac.uk/archive/hypercubes/>

Non-CS uses of Hypercubes: chemistry



Welcome to Hypercube, Inc.

What's Hot at Hypercube:

HyperNEWS

www.hypercom

Laboratory Exercises Using Hyperchem

Download: [Hyperchem Standard Online](#)

Latest News - December 1998. [Pocket HyperChem for Windows 95](#)

Order HyperChem for Windows CE and handheld PCs in your language!

Hypercube Game

"Sudden Death in the 4th Dimension":

<http://kbs.cs.tu-berlin.de/~jutta/swd/hyper-game.html>

2 players,

Start:



Move:



four reachable positions from each point.

Win = all of your pieces in sequence or star



(Grey wins.)



(Grey wins.)



(Black wins.)


Rubick's Hypercube

<http://www.rose-hulman.edu/~berglunb/Rubik/index.html>


Karnaugh Maps

- Invented by Maurice Karnaugh, 1953, at Bell Labs
- A way to **visualize** hypercubes of up to 4 (and stretching to 5 or 6) dimensions
- Approach by "flattening" a hypercube
- A structured form of Venn Diagram


"3-D" Karnaugh Map

 


Covering on a Karnaugh Map

 


Covering on a Karnaugh Map

 

Try this one

 


Answer

 


Using a Karnaugh Map to Prove Equalities

Prove that $x(v+w) = xv + xw$

 


Using a Karnaugh Map to Prove Equalities


Prove that $x(v+w) = xv + xw$

 


4-D Karnaugh Map

 


Implied connections on 4-D Karnaugh Map

 


Minterm Numbering on 4-D Karnaugh Map

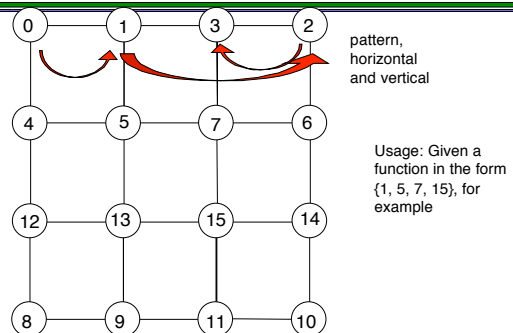

Assorted Sub-Cubes on 4-D Karnaugh Maps

 

Try this one

 

Exercises, etc.

- Project: Translate the hypercube game into a Karnaugh-map game.
- Exercise: Why is a Gray code sometimes called a "snake-in-the-box" code?

Simplification with "Don't Care" Combinations


- For certain problems, certain combinations (truth-table rows) never arise in actual operation.
- These are called "don't care" combinations.
- Because their input combinations never occur, the function value can be either 0 or 1. This means we can *elect* which value to use at our discretion.
- Usually we elect whichever value achieves the best simplification of the result.

Example: mod 3 adder


		uv					uv		
		00	01	10			00	01	10
xy	00	0	0	1	xy	00	0	1	0
	01	0	1	0		01	1	0	0
	10	1	0	0		10	0	0	1

Only 9 of 16 combinations actually occur, leaving 7 don't care ones. The don't cares are the same for both functions.


Plot Function on a K-Map

 


Plot Function on a K-Map

 


Do the other half.

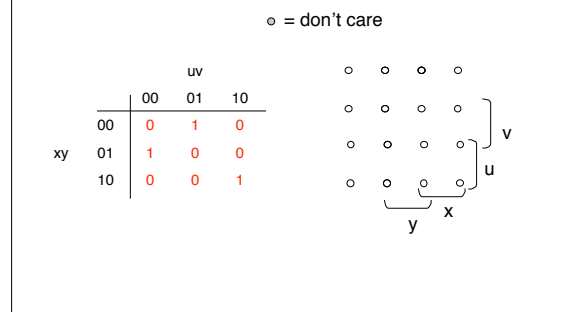

The other half.

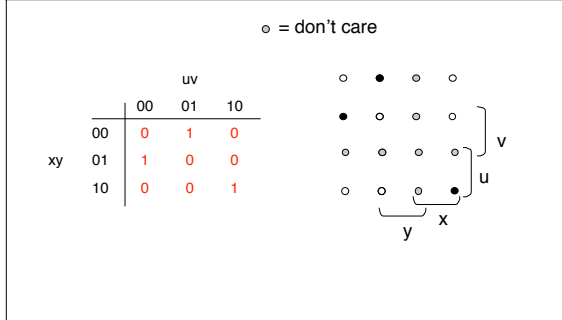

The other half.

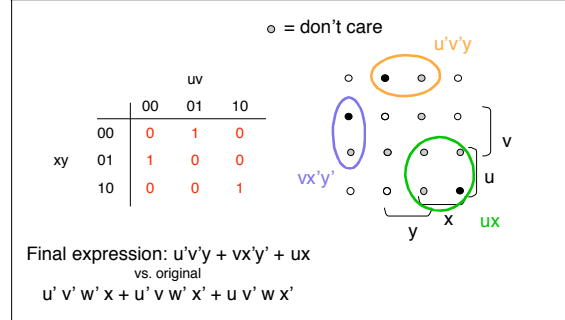

Implementation using NAND gates

- In some families of logic, **and**- and **or**-gates might not be available.
- Instead the only gate is **nand** (negated **and**).
- The question of sufficiency arises.

Sufficiency

- We know that functions **and**, **or**, and **not** are **sufficient** to realize any logic function.
- Two proofs:
 - minterm expansion: a sum of minterms, and each minterm uses **and** and **not** only
 - Boole-Shannon expansion (applied recursively)

Sufficiency

- To show that a given set of gate types is sufficient, it is enough to show that **and**, **or**, and **not** can be realized with those gate types.
- Actually it is sufficient to show just **and** and **not** can be realized, since **or** can be realized as:
 $a + b = (a' b)'$
 by DeMorgan's law. So if **and** and **not** are realizable, so is **or**.


nand alone is sufficient

- $a' = \text{nand}(a, a)$
- $\text{and}(a, b) = \text{nand}(a, b)'$
- $\text{or}(a, b) = \text{nand}(a', b')$
 $= \text{nand}(\text{nand}(a, a), \text{nand}(b, b))$


Exercises

- nor** alone is sufficient.
- Is **xor** alone sufficient?


Bubble Logic

 

SOP form using nand's only

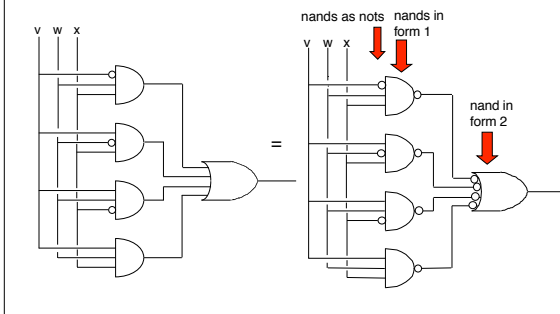


Logic Rebus

 


Common Logic Packages

- mod-2 adder
- mod-2 adder with carry-in
- 4-bit adder
- decoder (binary to one-hot)
- encoder (one-hot to binary)
- (MUX) multiplexor
- (DMUX) demultiplexor

mod-2 adder with carry-out

 


mod-2 adder with carry-in/out

 

$$\text{sum}(x, y, c) = x \oplus y \oplus c$$


$$\text{carry}(x, y, c) = xy + xc + yc = \text{majority}(x, y, c)$$

4-bit ripple-carry adder

 


Note: There are other ways to implement this.

4-bit decoder

 


4-bit encoder

 


	x_0	x_1	x_2	x_3	y_1	y_0
unlisted combinations are assumed not to occur	1	0	0	0	0	0
	0	1	0	0	0	1
	0	0	1	0	1	0
	0	0	0	1	1	1

multiplexor

 

demultiplexor

 

Exercises

- How would you build a decoder out of a demultiplexor?
- How would you build a 16-way multiplexor out of 4-way multiplexors?
- How would you build a 16-way demultiplexor out of 4-way demultiplexors?
- How would you use a decoder to build a decoder ring?