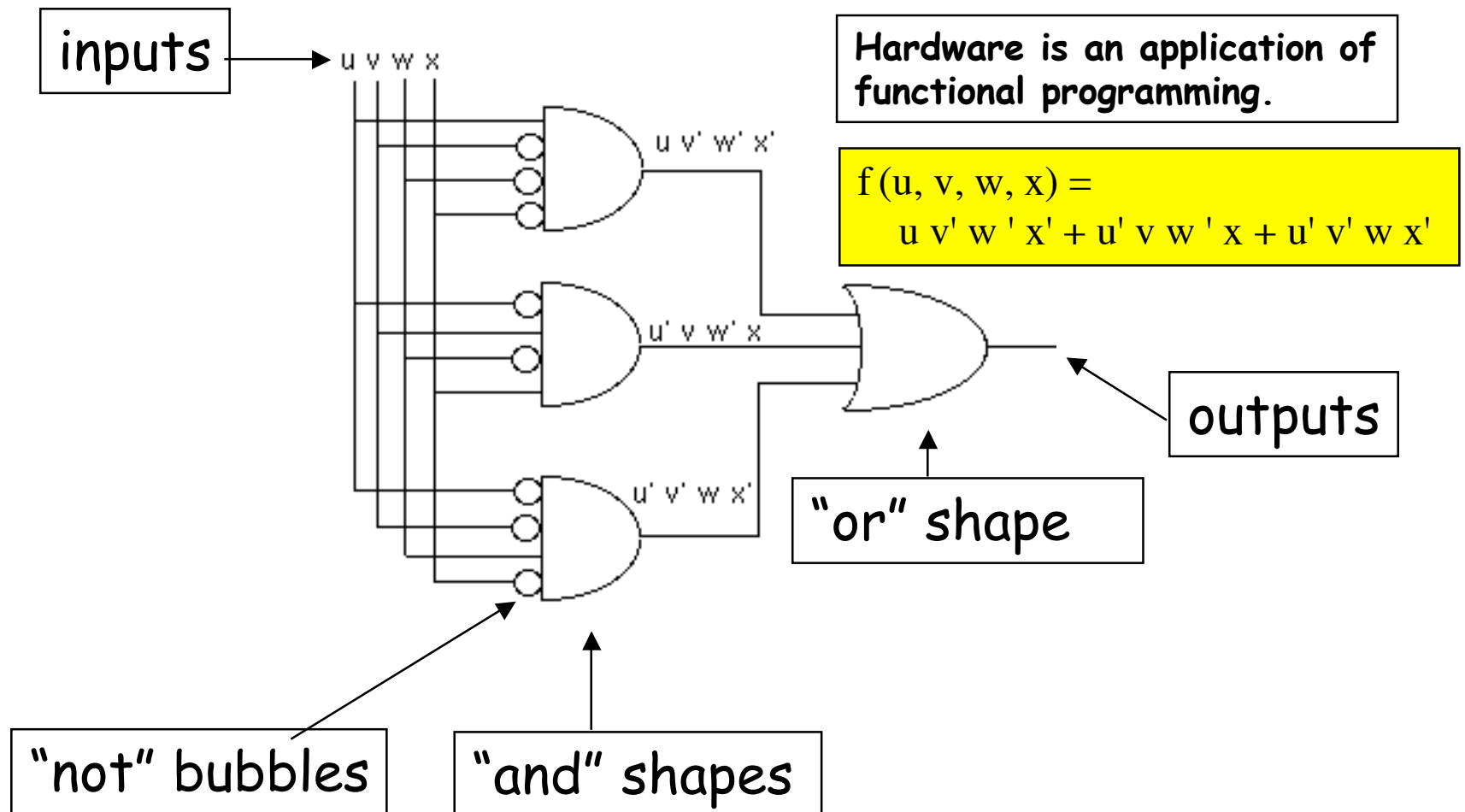





# Logic Circuit Synthesis

# Synthesizing Switching Functions


A "logic circuit" is composed of switching functions



# "and" gates

 


Engineering:  
 $x y$

 


Engineering:  
 $v w x y$

# "or" gates

 


Engineering:  
 $x + y$

 


Engineering:  
 $v + w + x + y$


# "not" Gates

 

$x'$

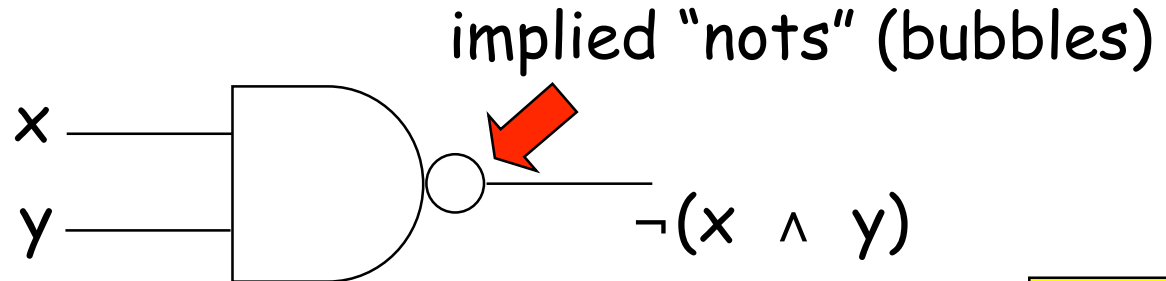

$(x y)'$

 

$x' + y'$

# Gates are Symbolic

---


---

- Gates are not just electronic; they can be
  - Mechanical
  - Hydraulic ("fluid logic")
  - Biological
  - Sub-atomic
  - Quantum-mechanical



# Mechanical Gates

"inverter"

 


# Mechanical Gates

---

---


"and" gate, using DeMorgan's law

 

"Nanotechnology"

# Fluid Gates

## "or" gate

 


# Biological Gates

---

---

input


output

 


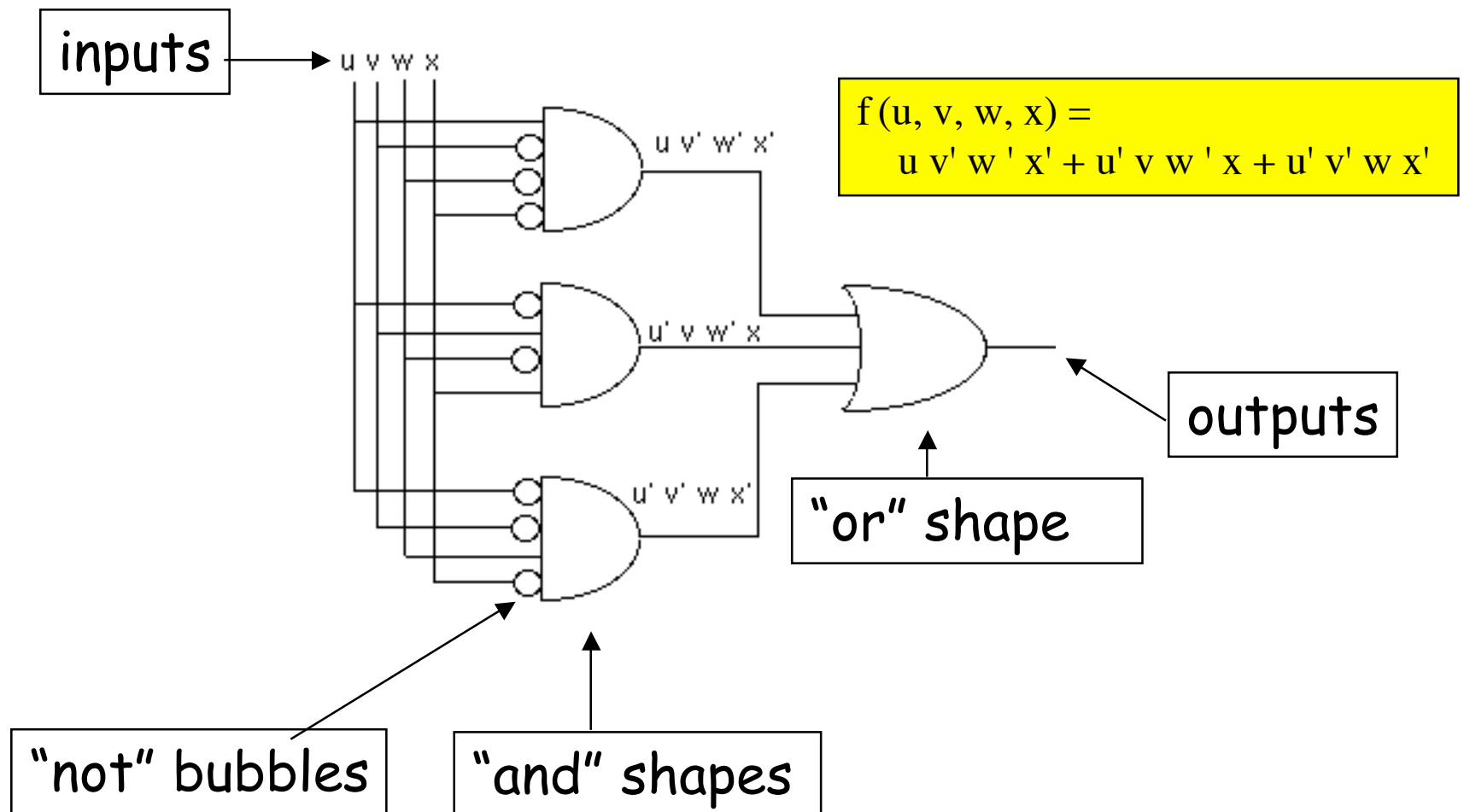
# Synthesizing Switching Functions

A "logic circuit" is composed of switching functions



## Ways to Specify Switching Functions

---

---

- Logic circuit
- Functional expression
  - SOP (sum-of-products) form
    - Minterm form
    - Other forms
- Truth table

# Note the Connection

## Truth table

u	v	w	x	f
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

$$f(u, v, w, x) =$$
$$u v' w' x'$$
$$+ u' v w' x$$
$$+ u' v' w x'$$

*Read off* each primed variable as 0, each unprimed as 1.

# Definition of "minterm"

---

---

- In the context of an n-variable switching function, a minterm is a function that is a conjunction ("and") of each variable or its complement (but not both).
- Minterm Examples (4 variables: u, v, w, x):  
 $uv'w'x$   
 $u'vw'x$
- Non-Minterm Examples (4 variables):  
 $uv$   
 $x$   
 $uvw$   
 $u'uvw$

# Note the Connection

$$f(u, v, w, x) =$$
$$u v' w' x'$$
$$+ u' v w' x$$
$$+ u' v' w x'$$

u	v	w	x	f
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

The "1" rows of the truth table correspond exactly to the minterms.

# Shorthands

$$\begin{aligned} f(u, v, w, x) = & \\ & u v' w' x' \\ & + u' v w' x \\ & + u' v' w x' \end{aligned}$$

Show only the "1" rows  
(be careful)

u	v	w	x	f
0	0	1	0	1
0	1	0	1	1
1	0	0	0	1

Represent whole table by a  
set of "minterm numbers":

$$\{2, 5, 8\}$$

Represent whole table by a single  
numeral:  $0010010010000000 = 9344_{10}$

# These are Equal

---

---

- The number of switching functions of  $n$  variables.
- The number of ways to assign 0 or 1 to the  $2^n$  combinations of  $n$  variables.
- The number of subsets of  $\{0, 1, 2, \dots, 2^n - 1\}$
- $2^{2^n}$

# Number of Switching Functions

---

---

- $2^{2^n}$
  - $n = 1: 2^2 = 4$
  - $n = 2: 2^4 = 16$
  - $n = 3: 2^8 = 256$
  - $n = 4: 2^{16} = 65,536$
  - $n = 5: 2^{32} = 4,294,967,296$
  - $n = 6: 2^{64} = 18,446,744,073,709,551,616$
- Each level **squares** the previous, since
- $2^{2^{n+1}} = 2^{2 \cdot 2^n} = 2^{2^n + 2^n} = (2^{2^n})^2$
- Also remember that  $2^{10} = 1024$  approx. 1000  
 $2^{20} =$  approx. 1,000,000 etc.


# The 16 switching functions of 2 variables

args		Function number															
b	c	0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1

constant 0								xor										constant 1
	and		$\neg$ implies					or		nor								nand
			$\neg$ implies reversed								iff		implies reversed		implies			
		projection		projection								$\neg$ projection		$\neg$ projection				
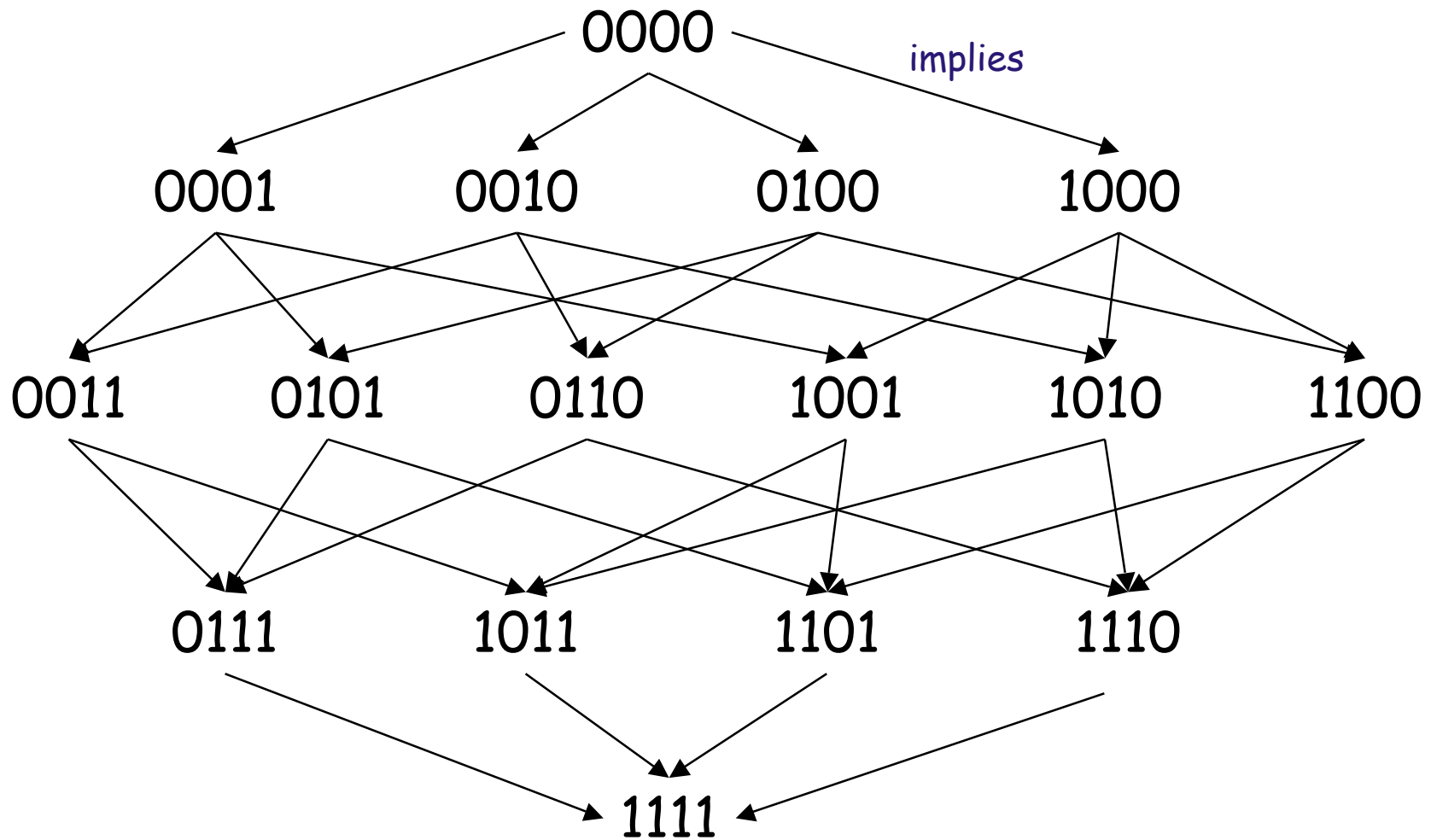
# Implication Lattice of 2-variable functions



# Logic Synthesis: Abstraction to Implementation

---

---

- **From:** Verbal problem description
- **To:** Implementation as a network of basic switching functions

# Logic Synthesis: Stages

---

---

- 1 **Provide** verbal problem description.
- 2 **Tabulate** description as function on finite sets.
- 3 **Encode** finite sets into bits.
- 4 **Transcribe** the encoded tables.
- 5 **Split** into individual switching functions.
- 6 **Realize** as a network of basic gates.

# Example

---

---

- Provide verbal description: Implement a "mod 3 adder using logic gates"
- A definition of mod3 addition:

$$f(a, b) = (a+b)\%3;$$

where  $a, b \in \{0, 1, 2\}$

# Tabulate definition of function

---

---

form-2 table:

$(x+y)\%3$	0	1	2
0	0	1	2
1	1	2	0
2	2	0	1

# Encode sets into bits

---

---

- Set to be encoded:  $\{0, 1, 2\}$
- Chosen encoding (among many possible):
  - $0 \rightarrow 00$
  - $1 \rightarrow 01$
  - $2 \rightarrow 10$

# Transcribe the Function to the Encoded Values

Function	Encoding			
$(x+y)\%3$	0	1	2	
0	0	1	2	→
1	1	2	0	
2	2	0	1	


0 → 00  
 1 → 01  
 2 → 10



Encoded Function		uv		
		00	01	10
	00	00	01	10
wx	01	01	10	00
	10	10	00	01

Here first argument becomes uv,  
 second becomes wx.
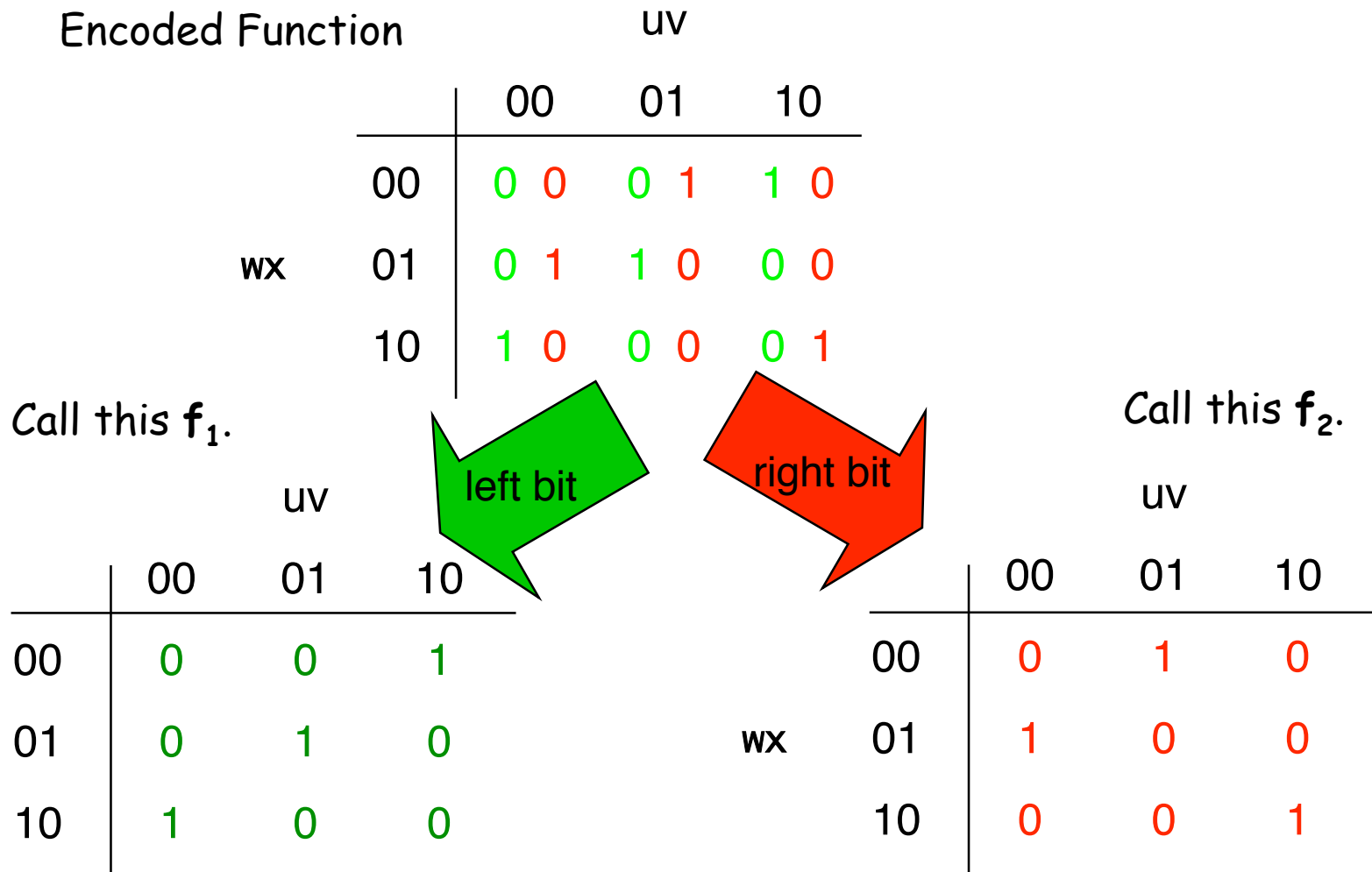
# Split the Encoded Function into individual switching functions



The resulting switching functions generally will only be *partially* specified; some combinations don't occur.

		uv		
		00	01	10
wx	$f_1$	0	0	1
	00	0	0	1
	01	0	1	0
	10	1	0	0

		uv		
		00	01	10
wx	$f_2$	0	1	0
	00	0	1	0
	01	1	0	0
	10	0	0	1

u	v	w	x	$f_1$	$f_2$	
0	0	0	0	0	0	
0	0	0	1	0	1	
0	0	1	0	1	0	
0	0	1	1	?	?	←
0	1	0	0	0	1	
0	1	0	1	1	0	
0	1	1	0	0	0	
0	1	1	1	?	?	←
1	0	0	0	1	0	
1	0	0	1	0	0	
1	0	1	0	0	1	
1	0	1	1	?	?	←
1	1	0	0	?	?	←
1	1	0	1	?	?	←
1	1	1	0	?	?	←
1	1	1	1	?	?	←

As the unspecified values will never occur, we can give the function either value 0 or 1.

For the time being, let's just make them all 0.

Now we can "read off" an expression for each function.

$$\begin{aligned}
 f_1(u, v, w, x) = & \\
 & u' v' w x' \\
 & + u' v w' x \\
 & + u v' w' x'
 \end{aligned}$$

u	v	w	x	f <sub>1</sub>	f <sub>2</sub>
0	0	0	0	0	0
0	0	0	1	0	1
0	0	1	0	1	0
0	0	1	1	?	?
0	1	0	0	0	1
0	1	0	1	1	0
0	1	1	0	0	0
0	1	1	1	?	?
1	0	0	0	1	0
1	0	0	1	0	0
1	0	1	0	0	1
1	0	1	1	?	?
1	1	0	0	?	?
1	1	0	1	?	?
1	1	1	0	?	?
1	1	1	1	?	?

Exercise: "read off" the expression for  $f_2$ .

u	v	w	x	$f_1$	$f_2$
0	0	0	0	0	0
0	0	0	1	0	1
0	0	1	0	1	0
0	0	1	1	?	?
0	1	0	0	0	1
0	1	0	1	1	0
0	1	1	0	0	0
0	1	1	1	?	?
1	0	0	0	0	0
1	0	0	1	0	0
1	0	1	0	1	1
1	0	1	1	?	?
1	1	0	0	?	?
1	1	0	1	?	?
1	1	1	0	?	?
1	1	1	1	?	?


Exercise: "read off" the expression for  $f_2$ .

$$\begin{aligned}
 f_2(u, v, w, x) = & \\
 & u' v' w' x \\
 & + u' v w' x' \\
 & + u v' w x'
 \end{aligned}$$

u	v	w	x	$f_1$	$f_2$
0	0	0	0	0	0
0	0	0	1	0	1
0	0	1	0	1	0
0	0	1	1	?	?
0	1	0	0	0	1
0	1	0	1	1	0
0	1	1	0	0	0
0	1	1	1	?	?
1	0	0	0	0	0
1	0	0	1	0	0
1	0	1	0	1	1
1	0	1	1	?	?
1	1	0	0	?	?
1	1	0	1	?	?
1	1	1	0	?	?
1	1	1	1	?	?


# Realize each function by gates

Mod 3  
adder

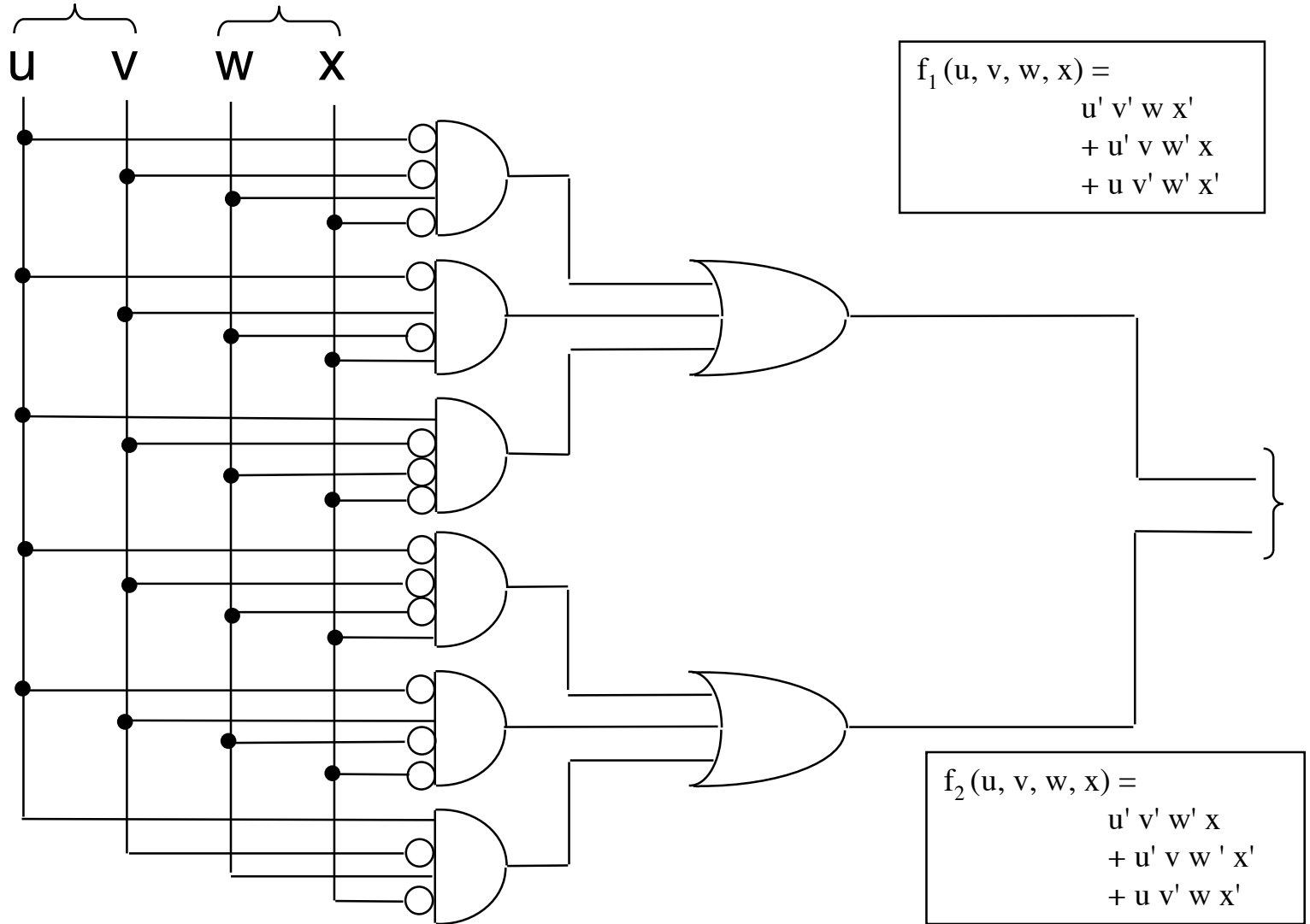
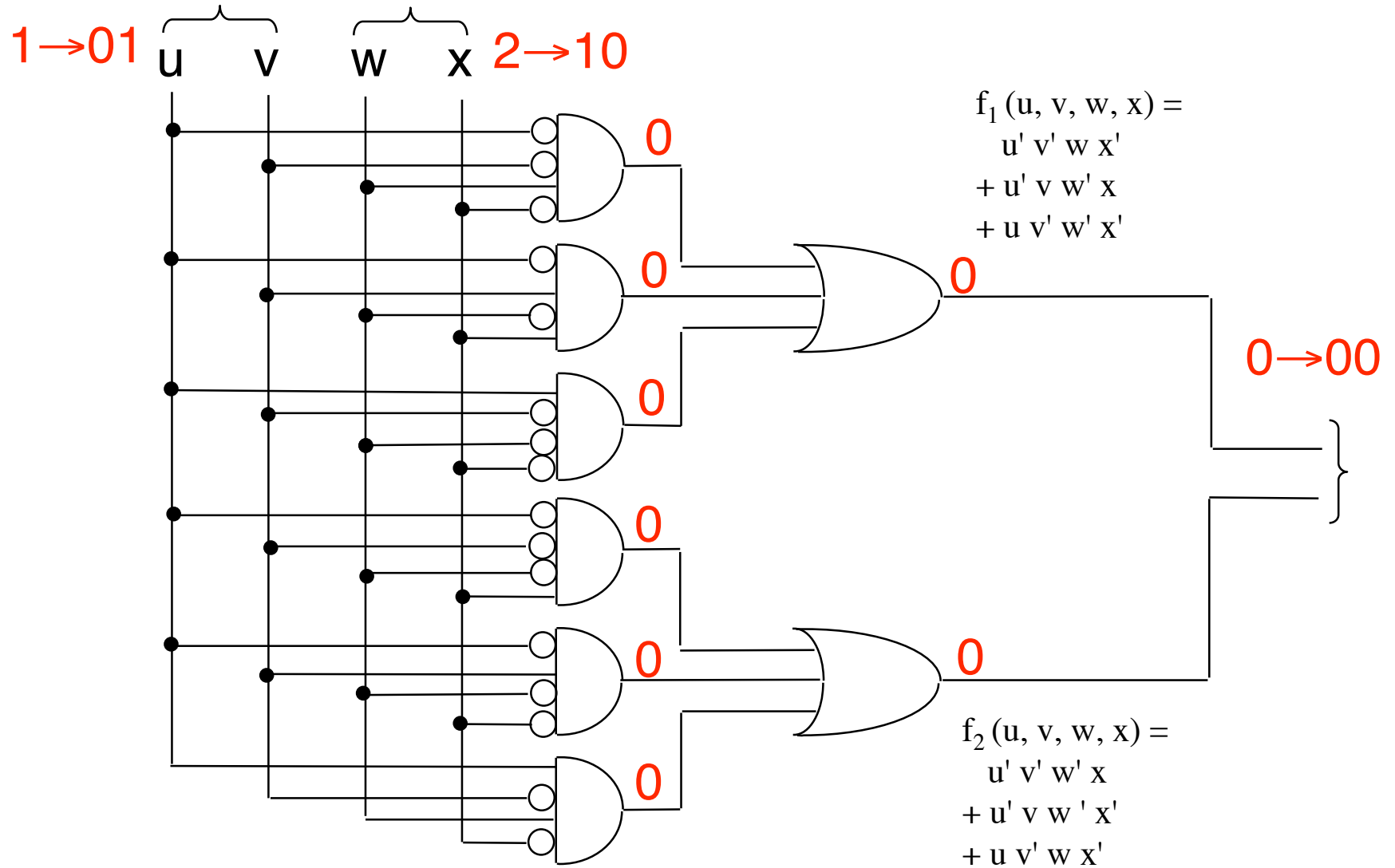
# Check by "Reverse Engineering"

(Try all combinations; one combination is shown)



# Rex Program for Checking all Combinations



```
encode(0) => [0, 0];  
encode(1) => [0, 1];  
encode(2) => [1, 0];
```

```
decode([0, 0]) => 0;  
decode([0, 1]) => 1;  
decode([1, 0]) => 2;  
decode([x, y]) => "error, should not occur";
```

```
add3(i, j) = (i+j)%3;
```

```
addByCircuit(i, j) = decode(circuit(encode(i), encode(j)));
```

```
circuit([u, v], [w, x]) =>  
  [ !u && !v && w && !x  
    || !u && v && !w && x  
    || u && !v && !w && !x,  
  
    !u && !v && !w && x  
    || !u && v && !w && !x  
    || u && !v && w && !x  
  ];
```

  

## Scheme Program for Checking all Combinations


**; The test encoder/decoder**

```
(define (encode d)
  (case d
    ('0 '(#f #f))
    ('1 '(#f #t))
    ('2 '(#t #f))
    (else (error "undefined encode" d))))

(define (decode e)
  (cond
    ((equal? e '(#f #f)) 0)
    ((equal? e '(#f #t)) 1)
    ((equal? e '(#t #f)) 2)
    (else ((error "undefined decode" e)))))

(define (add3 i j)
  (modulo (+ i j) 3))

 (define (addByCircuit i j)
  (decode (circuit (encode i) (encode j))))
```



**; The circuit simulation**

```
(define (circuit y z)
  (let ((u (first y))
        (v (second y))
        (w (first z))
        (x (second z)))
    (list
     (or
      (and (not u) (not v) w (not x))
      (and (not u) v (not w) x)
      (and u (not v) (not w) (not x)))
     (or
      (and (not u) (not v) (not w) x)
      (and (not u) v (not w) (not x))
      (and u (not v) w (not x))))))
```

# Testing Every Combination

---

---

```
(test (addByCircuit 0 0) 0)
```

```
(test (addByCircuit 0 1) 1)
```

```
(test (addByCircuit 0 2) 2)
```

```
(test (addByCircuit 1 0) 1)
```

```
(test (addByCircuit 1 1) 2)
```

```
(test (addByCircuit 1 2) 0)
```

```
(test (addByCircuit 2 0) 2)
```

```
(test (addByCircuit 2 1) 0)
```

```
(test (addByCircuit 2 2) 1)
```

```
Test 1: (addByCircuit 0 0) succeeds with result: 0
Test 2: (addByCircuit 0 1) succeeds with result: 1
Test 3: (addByCircuit 0 2) succeeds with result: 2
Test 4: (addByCircuit 1 0) succeeds with result: 1
Test 5: (addByCircuit 1 1) succeeds with result: 2
Test 6: (addByCircuit 1 2) succeeds with result: 0
Test 7: (addByCircuit 2 0) succeeds with result: 2
Test 8: (addByCircuit 2 1) succeeds with result: 0
Test 9: (addByCircuit 2 2) succeeds with result: 1
```

## Logic Simplification

---

---

- Consider the Boole/Shannon Expansion:  
$$f(x, y) = x f(1, y) + x' f(0, y)$$
- where  $y$  represents a bunch of variables.
- Without simplification, repeated expansion can be unwieldy.
- The following slides show ways to simplify.

## Some Logic Simplifications

---


---

$$f(x, y) = x G(y) + x' H(y)$$

- If  $G$  is the 0 function, then  $f(x, y) = x'H(y)$ .
- If  $H$  is the 0 function, then  $f(x, y) = xG(y)$ .
- If  $G = H$  (as functions), then  $f(x, y) = G(y)$ .
- If  $G$  is the 1 function, then  $f(x, y) = x + H(y)$  [no  $x$  on right].
- If  $H$  is the 1 function, then  $f(x, y) = x' + G(y)$  [no  $x$  on right].

# Bubble Logic

nand

 


DeMorgan:

$$\text{nand}(a, b) =$$



$$\text{and}(a, b)' =$$

$$\text{or}(a', b')$$

or

 


nand, another way

  

$$(a')' = a$$

# SOP form using nand's only

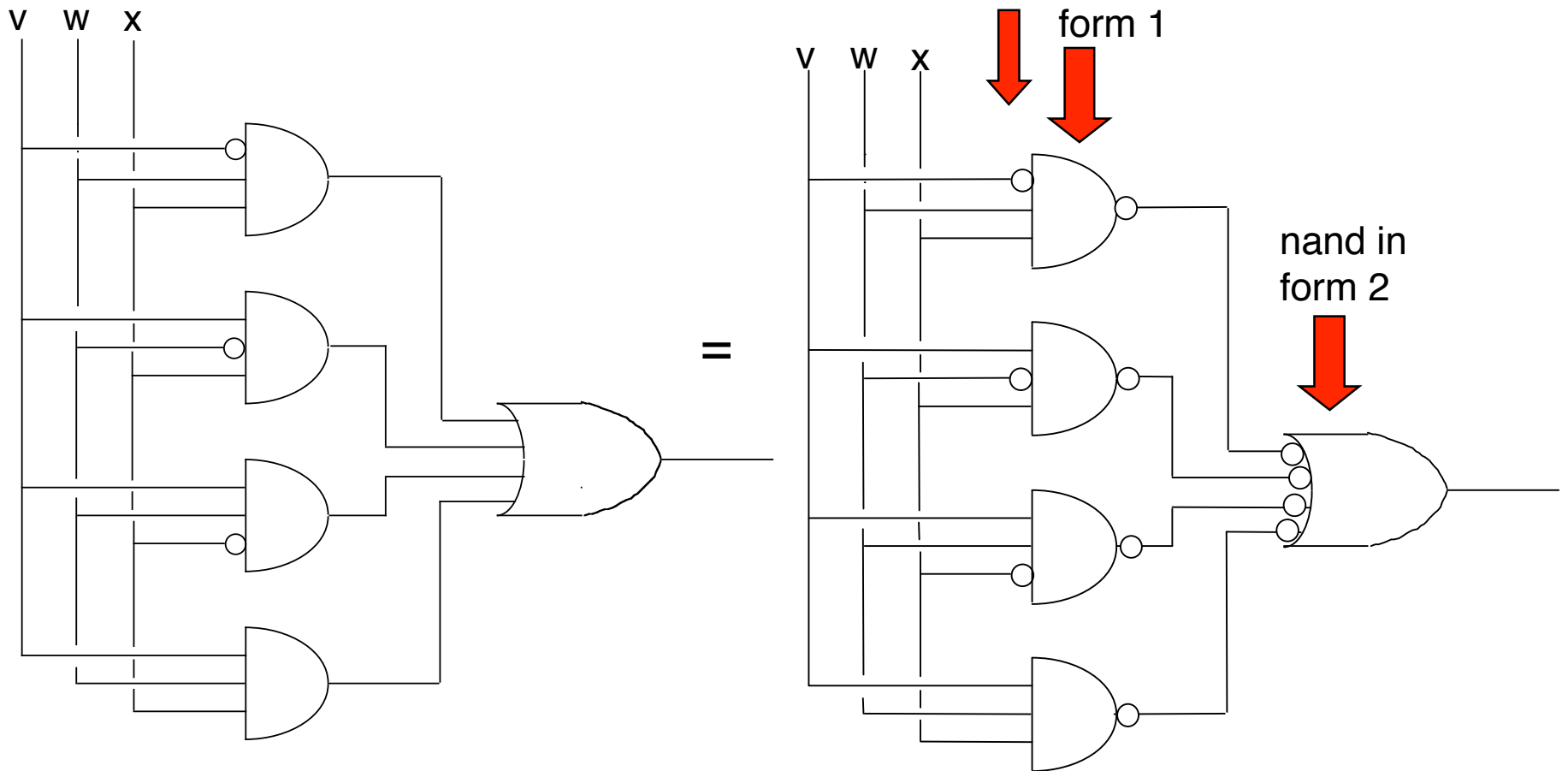

# Common Logic Packages

---


---

- mod-2 adder
- mod-2 adder with carry-in
- 4-bit adder
- decoder (binary to one-hot)
- encoder (one-hot to binary)
- (MUX) multiplexer
- (DMUX) demultiplexer

# mod-2 adder with carry-out

---

---

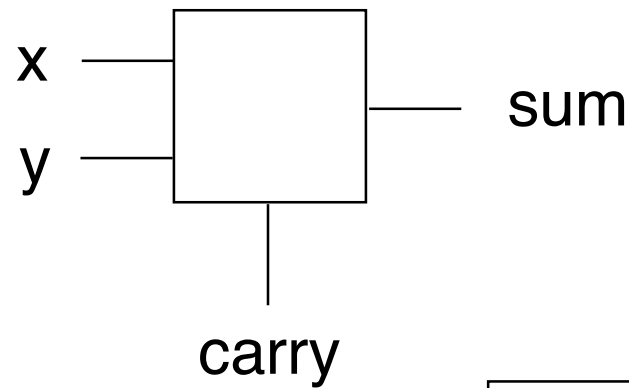

exclusive or


$$\text{sum}(x, y) = x \oplus y = xy' + x'y$$

$$\text{carry}(x, y) = x y$$

# mod-2 adder with carry-in/out

---


---

 

$$\text{sum}(x, y, c) = x \oplus y \oplus c$$

$$\text{carry}(x, y, c) = x y + x c + y c = \text{majority}(x, y, c)$$

# 4-bit ripple-carry adder

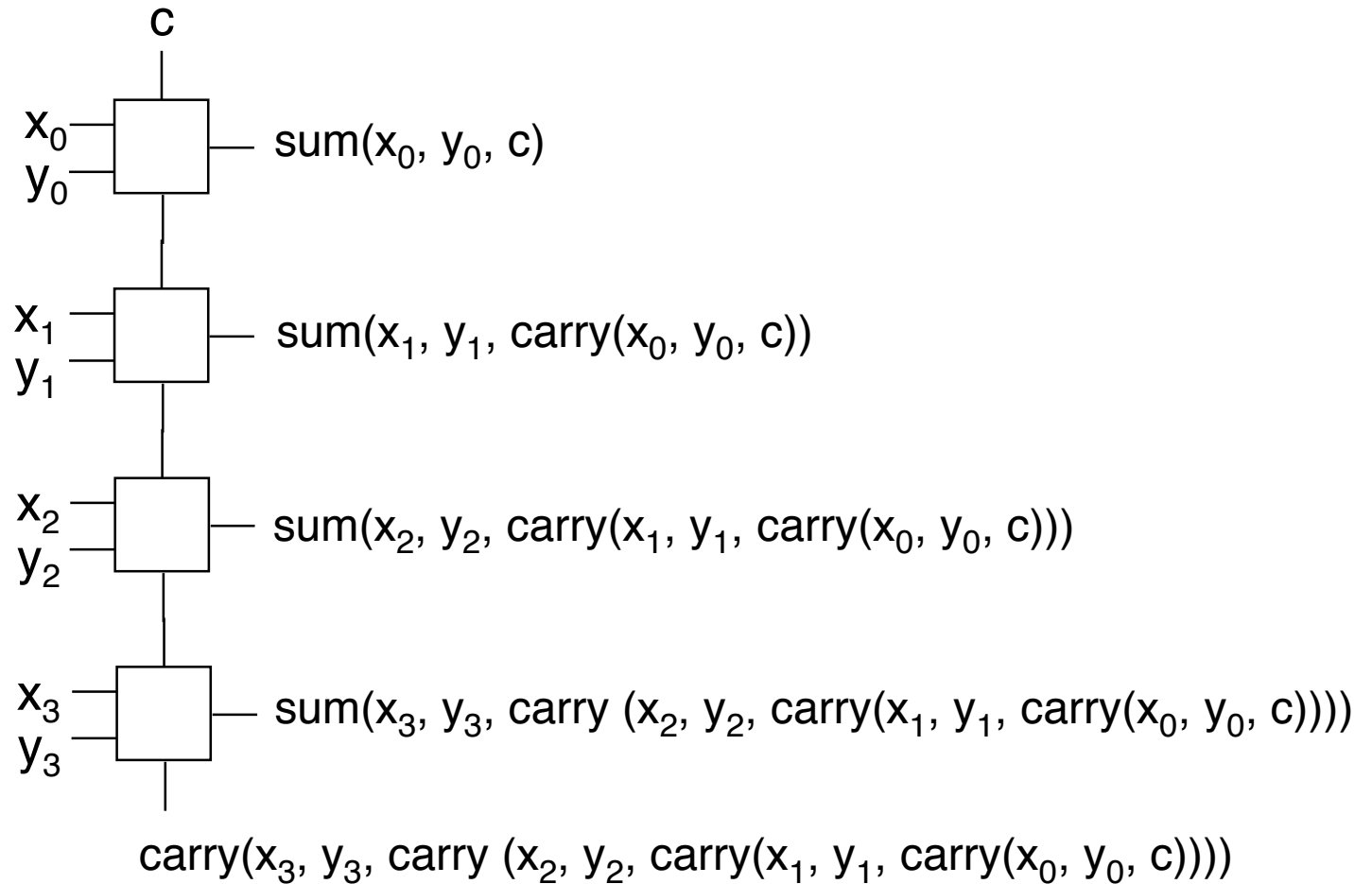


Note: There are other ways to implement this.


# 4-bit decoder

---

---

 


# 4-bit encoder

 

unlisted combinations are assumed not to occur

$x_0$	$x_1$	$x_2$	$x_3$	$y_1$	$y_0$
1	0	0	0	0	0
0	1	0	0	0	1
0	0	1	0	1	0
0	0	0	1	1	1


# multiplexer

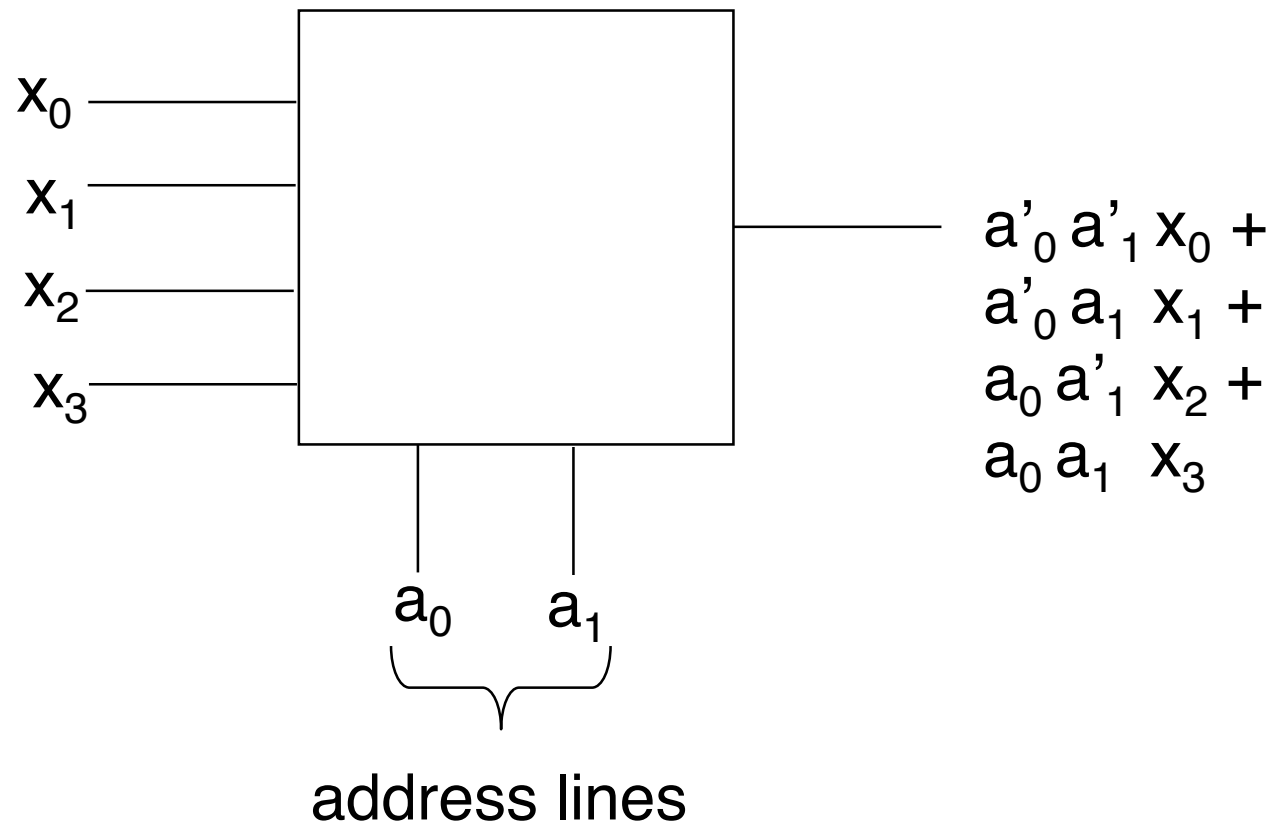

# demultiplexer

---

---

 

# Exercises

---

---

- How would you build a decoder out of a demultiplexor?
- How would you build a 16-way multiplexor out of 4-way multiplexors?
- How would you build a 16-way demultiplexor out of 4-way demultiplexors?

# Logic Rebuses

