

---

---

# Finite-State Machines as Hardware

# Implementing Finite-State Machines using Logic+Memory

---

---

- When we implemented logic functions, we used only gates and no memory; those are called *combinational* logic circuits.
- To implement a finite-state machine, some kind of *memory* is generally necessary to remember the previous state. These are called *sequential* logic circuits.

# Representing a Discrete Sequence in Continuous Time

---


---

- From our viewpoint, time appears to be a continuous variable.
- For a digital sequence, we want discrete values  $[x_0, x_1, x_2, x_3, \dots]$ , not a continuous function  $x(t)$ .
- The typical way to handle this is to use a *clock*.
- The continuous sequence is "sampled" at regularly-spaced times, when the clock "ticks".


# Sampling a Signal

---


---

 


# Sampling a Signal

 

 (In reality, rises and falls aren't so vertical.)




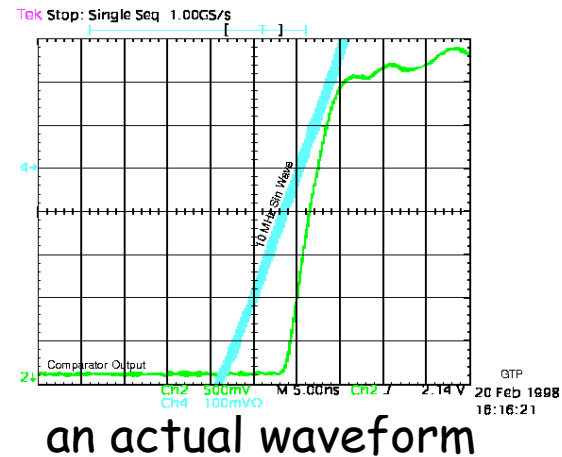as sometimes shown  
in engineering drawings



an actual waveform

# Sampling a Signal

 

# Clock Rate

---

---

- The clock is analogous to the conductor of a symphony orchestra: it keeps all of the players in synch.
- The rate at which the clock ticks is the quoted rate of the processor, e.g. 500 MHz (500,000,000 ticks per second).
- It is possible to design systems that don't have clocks ("asynchronous systems") but these are rare.



# The Basic Unit of Memory is the Flip-Flop

---

---


- A flip-flop remembers **one bit**, either a 0 or 1.
- The presence of a synchronizing clock is assumed.
- The bit is held from one clock-tick to the next.
- Each time the clock ticks, whatever value (0 or 1) exists at the flip-flop's input is **remembered**; the old value is lost.

# Flip-Flop Behavior

 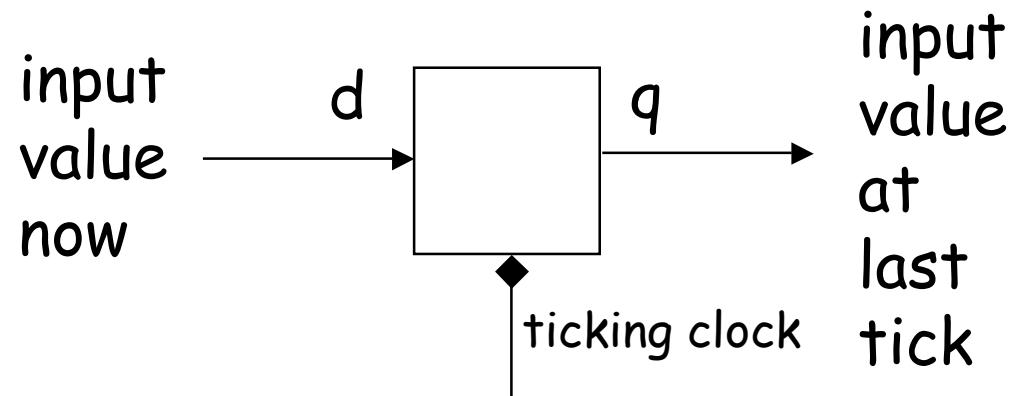

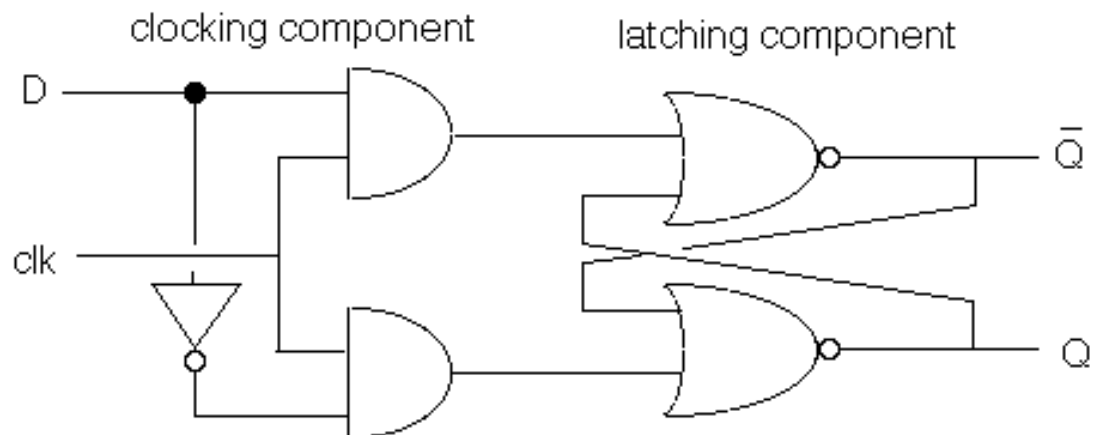
# Inside a Flip-Flop


- A flip-flop can be constructed from ordinary gates (which have some associated switching *delay*) and feed-back connections.
- A first approximation, called a *clocked latch*, is:



# Clocked Latch Behavior

 

# Edge-Triggered Flip-Flop

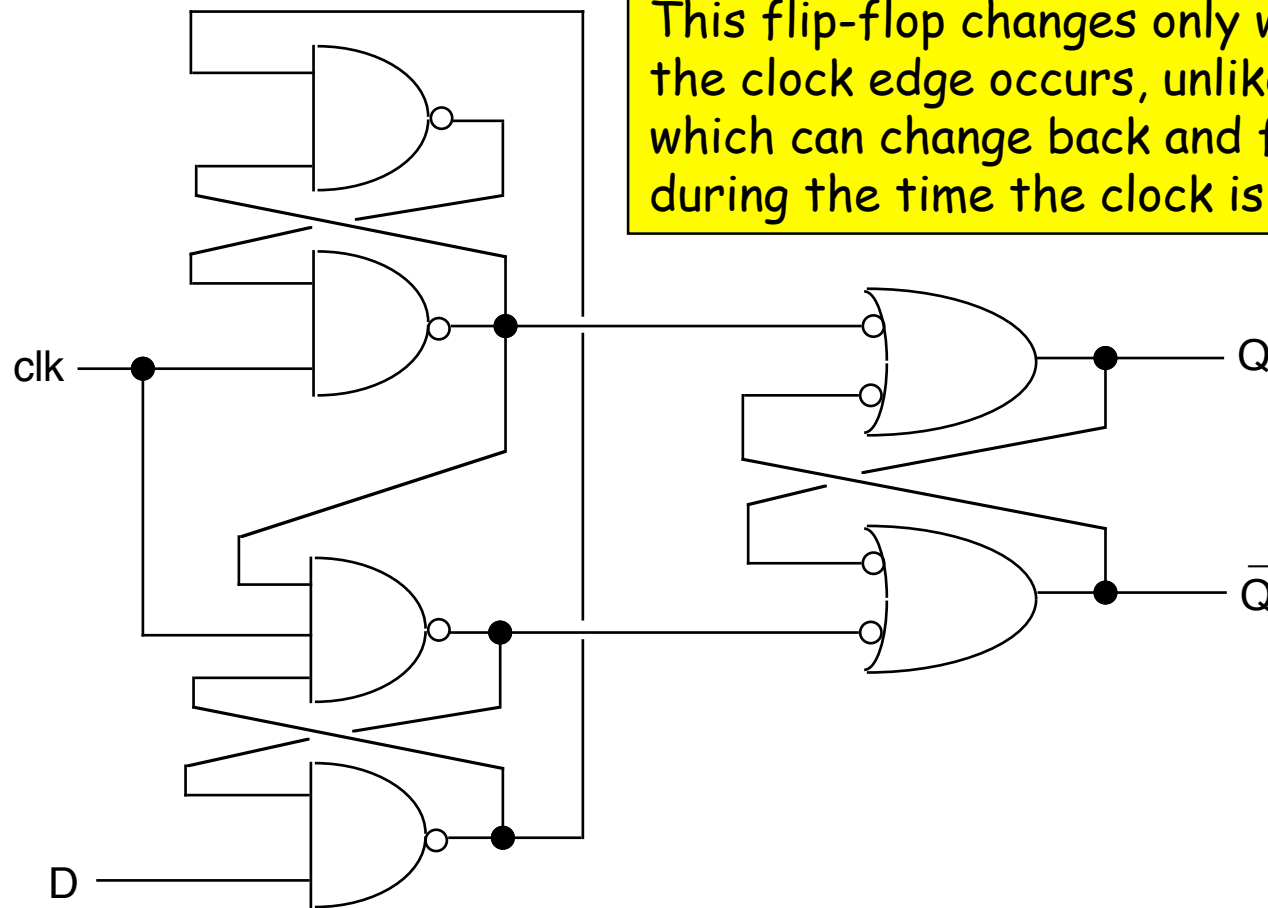

This flip-flop changes only when the clock edge occurs, unlike the latch, which can change back and forth during the time the clock is 1.

Analysis is left to the reader.

# Encoding An Arbitrary State Set for a Finite-State Machine

---


---

- We can encode an arbitrary **state set** just as we encode any set, in terms of some number of bits.
- When the encoding has been chosen, we need **one flip-flop per bit**.
- We implement the next-state function using *combinational* logic: given an encoded version of the current state, produce the encoding of the next state.

# Next-State Sequential Logic for a Finite-State Machine

Combinational logic for the next-state function (gates)

Bits encoding the input

 


Bits encoding the current state


# Example: Implement a multiples-of-3 machine

---


---

 

 Suppose we encode the state set using 2 bits, thus:


 
# Example: Implement a multiples-of-3 machine



The next state is summarized by the following table:


next state current state	input	
	0	1
00	00	01
01	10	00
10	01	10

But we already know how to implement such a table in logic!


# Logic for Multiple-of-3

next vw	input (x)	
current state (vw)	0	1
00	00	01
01	10	00
10	01	10

next v:

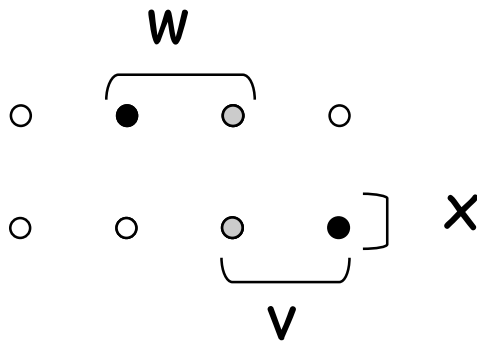

next w:

 


What are the simplified logic functions?

# Logic for Multiple-of-3


next vw current state (vw)	input (x)	
	0	1
00	00	01
01	10	00
10	01	10

next v:

 

$$\text{next } v = wx' + vx$$

next w:

 


$$\text{next } w = vx' + v'w'x$$


# Logic Diagram

$$\text{next } v = wx' + vx$$

$$\text{next } w = vx' + v'w'x$$

 

# Logic Diagram in Context

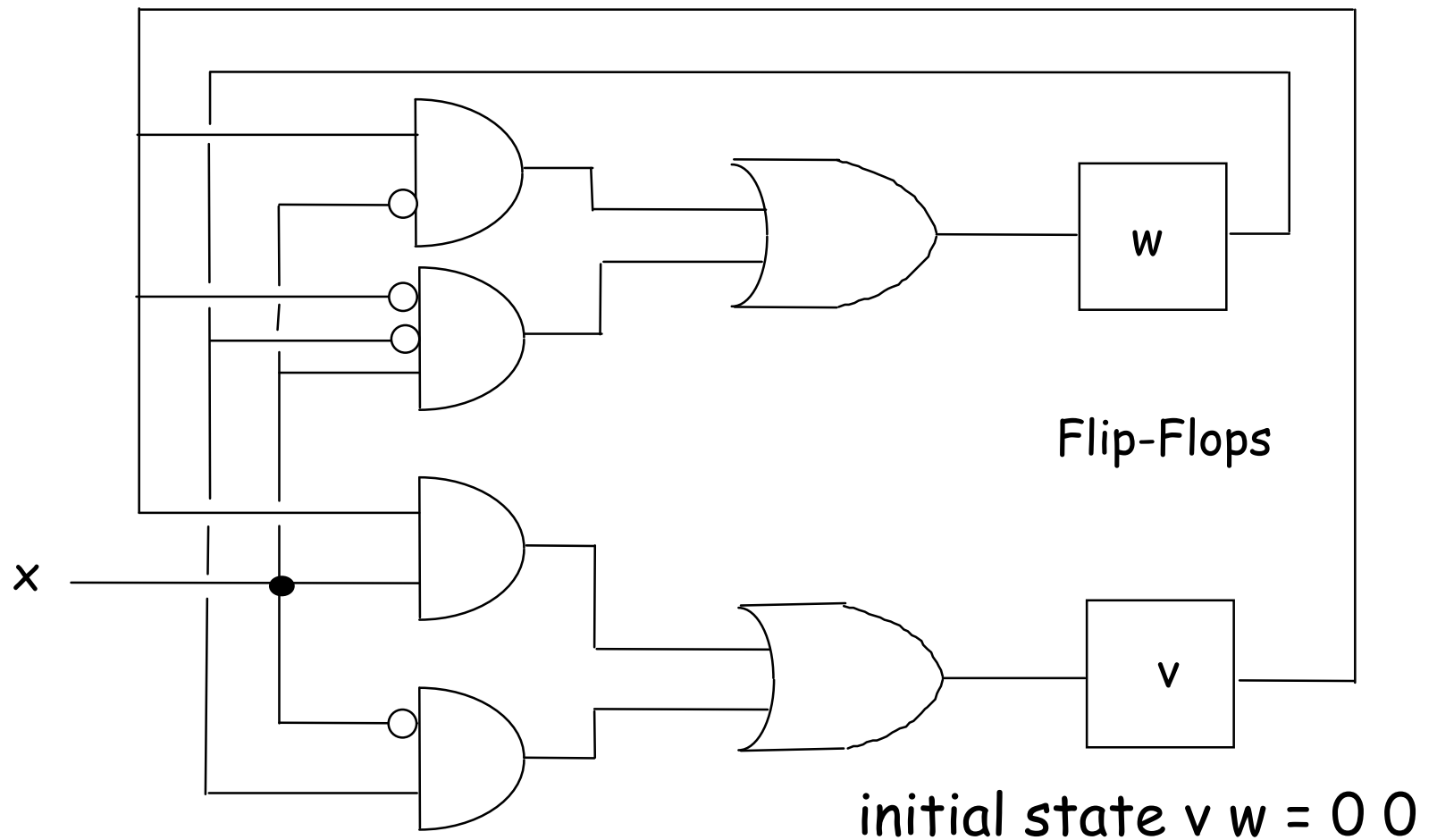

# Output Considerations


---

---

- We need to drive the output from the encoded state.
- The output is coded, just like the state and input.
- Let's say that the output is  $z$  which has value 1 for accepting, 0 for rejecting.
- Since the only accepting state is 00, the output function is

$$z = v'w'$$

# Final Circuit, with Output

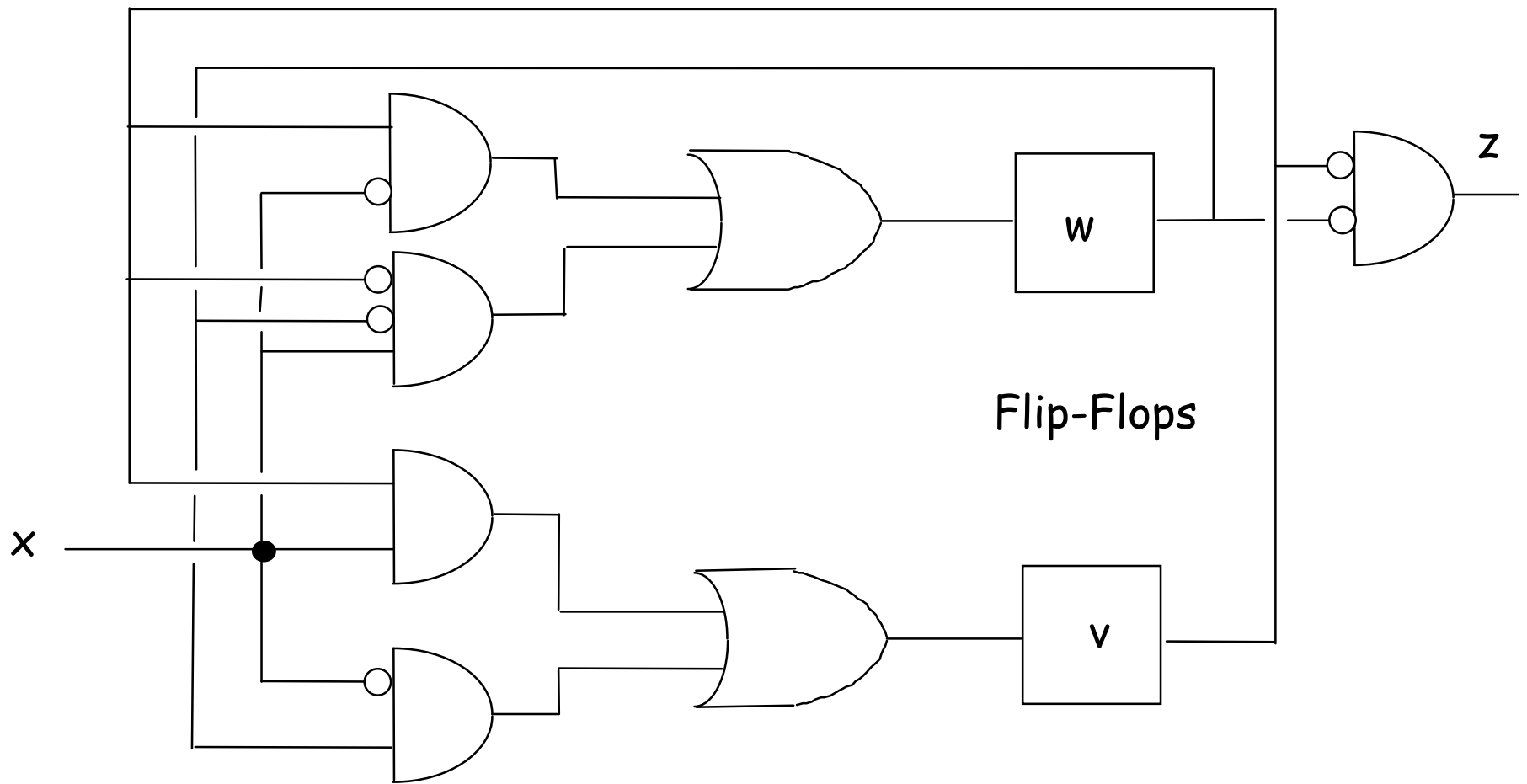

initial state  $v w = 0 0$

# Reverse Engineering

---

---

- We can check our result by “reverse engineering”, that is construct the state diagram from the logic itself.
- From the drawing, we have:
  - next  $v = vx + wx'$
  - next  $w = vx' + v'w'x$
  - initial  $v w = 0 0$
  - output  $z = v'w'$

# Reverse Engineering

---

---

- From the drawing, we have:
  - next  $v = vx + wx'$
  - next  $w = vx' + v'w'x$
  - initial  $v w = 0 0$
  - output  $z = v'w'$
- Construct a diagram with states =  $v w$ , starting with initial state  $0 0$ :

$0 0$ with input $0 \rightarrow 0 0$	$0 0$ with input $1 \rightarrow$
$0 1$ with input $0 \rightarrow$	$0 1$ with input $1 \rightarrow$
$1 0$ with input $0 \rightarrow$	$1 0$ with input $1 \rightarrow$

# Reverse Engineering

---

---

- From the drawing, we have:
  - next  $v = vx + wx'$
  - next  $w = vx' + v'w'x$
  - initial  $v w = 0 0$
  - output  $z = v'w'$
- Construct a diagram with states =  $v w$ , starting with initial state  $0 0$ :

$0 0$  with input  $0 \rightarrow 0 0$

$0 1$  with input  $0 \rightarrow 1 0$

$1 0$  with input  $0 \rightarrow 0 1$

$0 0$  with input  $1 \rightarrow 0 1$

$0 1$  with input  $1 \rightarrow 0 0$


$1 0$  with input  $1 \rightarrow 1 0$

# Reverse Engineering

---

---

- The resulting diagram:

 

which is what we started with.

- In general, reverse engineering will start from the logic.

---

# Physical Computers

(as distinguished from  
"virtual" computers, such as  
Turing machines)

# Computer Components

---

---

- Finite-state machines
- Combinational logic
- Busses

# Register

---

---


- A register is a finite-state machine that remembers values as bit vectors.
- A register may perform other functions as well:
  - Clearing
  - Incrementing, decrementing
  - Shifting

# Simplest register


---

---

Remembers one bit = Flip-Flop

 

# Two-Bit Register

 


# Inputs to a Register

---

---

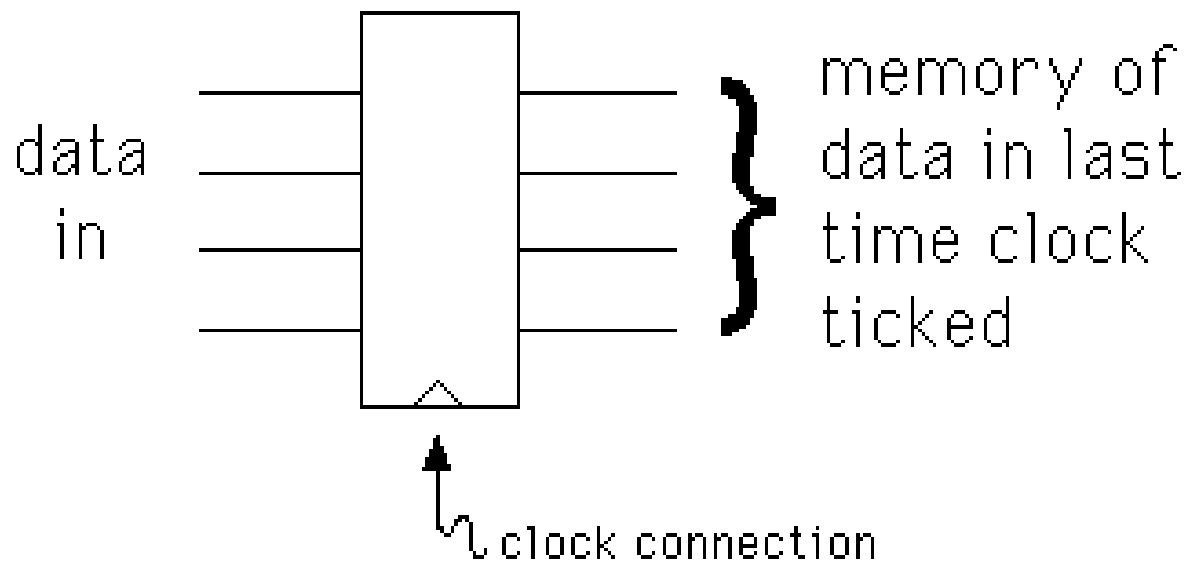
- Data (e.g. value to be remembered)
- "Strobe": function to be performed
- Simplest register has no strobe inputs



# Register with Strobe Input

---


---

 

# Register with Two Strobe Inputs

---

---

 


# 1-bit register with load & clear

---

---

 - {clear, load} is 1-hot (never both 1 simultaneously)



# Strobe Possibilities

---


---

- load
- clear
- increment
- decrement
- complement
- left-shift
- right-shift

# Register Transfer


---

---

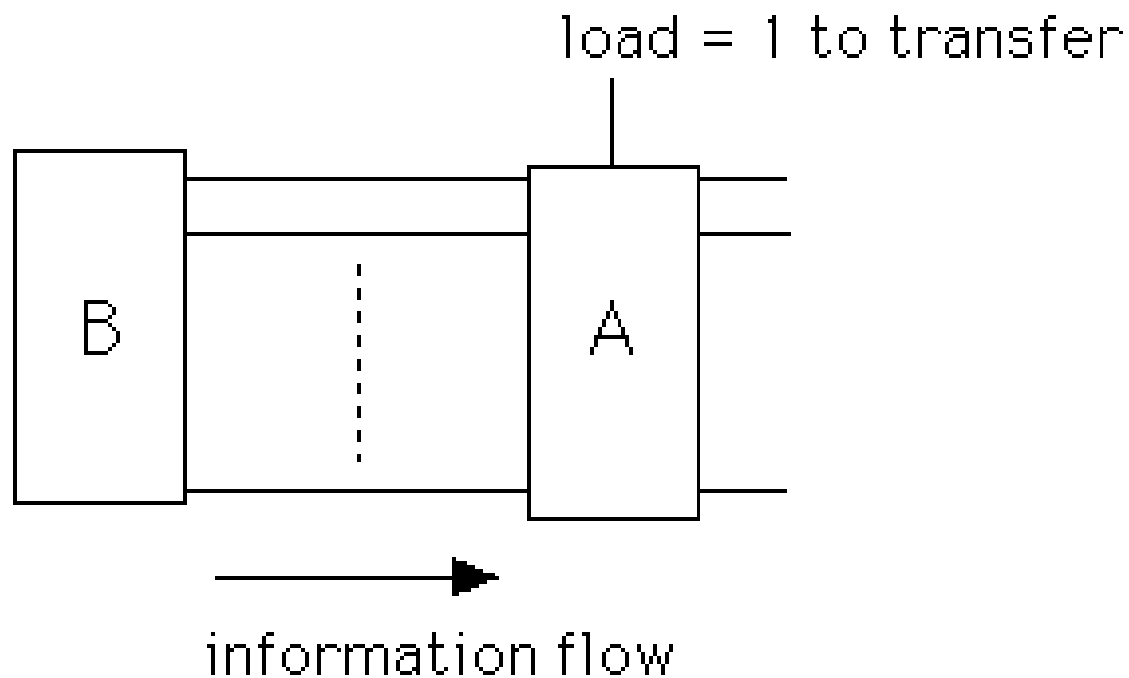

Equivalent Java: `A = B;`


# Selective Register Transfer

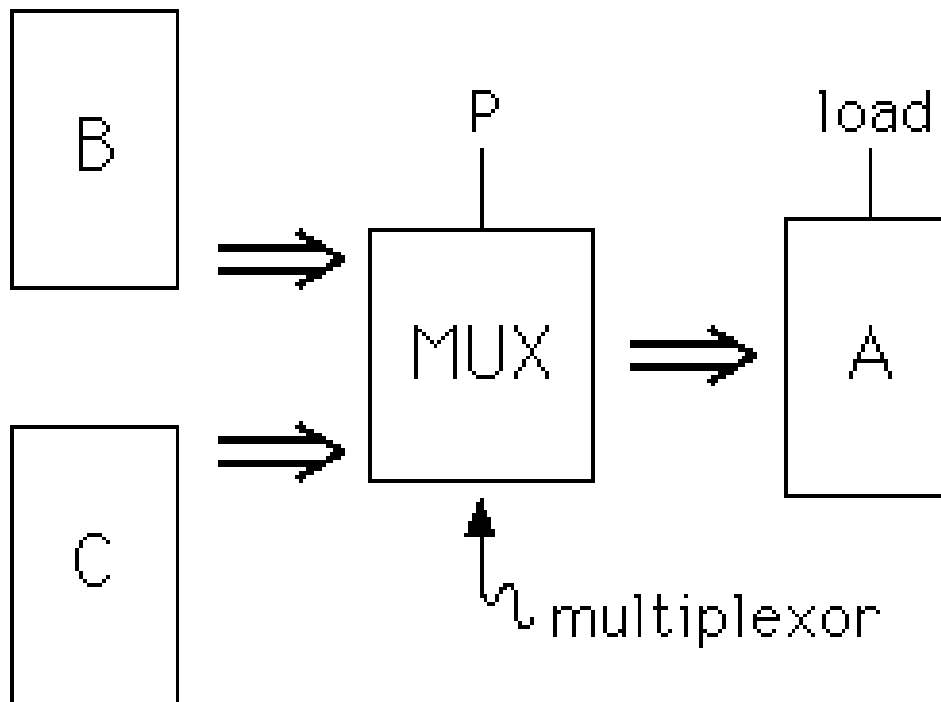


See also:  
Boole/Shannon  
Expansion

Equivalent Java: `A = P ? B : C;`

# 4-way selection

 

# Selection Using a Bus

 

For this to make sense, we need another register output value separate from 0,1.

# Implementing Bus Connection

---


---

- We can't simply use AND-gates; the output of an AND will *always* be 0 or 1.
- Connecting together wires with 0 and 1 simultaneously would be fatal.
- For the bus, use a third possible output value:
  - "high impedance", "high Z", or
  - NC (no connection)


# 3-State Buffer

---

---

 


output = control ? data : NC;

 

No Connection

# Selection using Bus

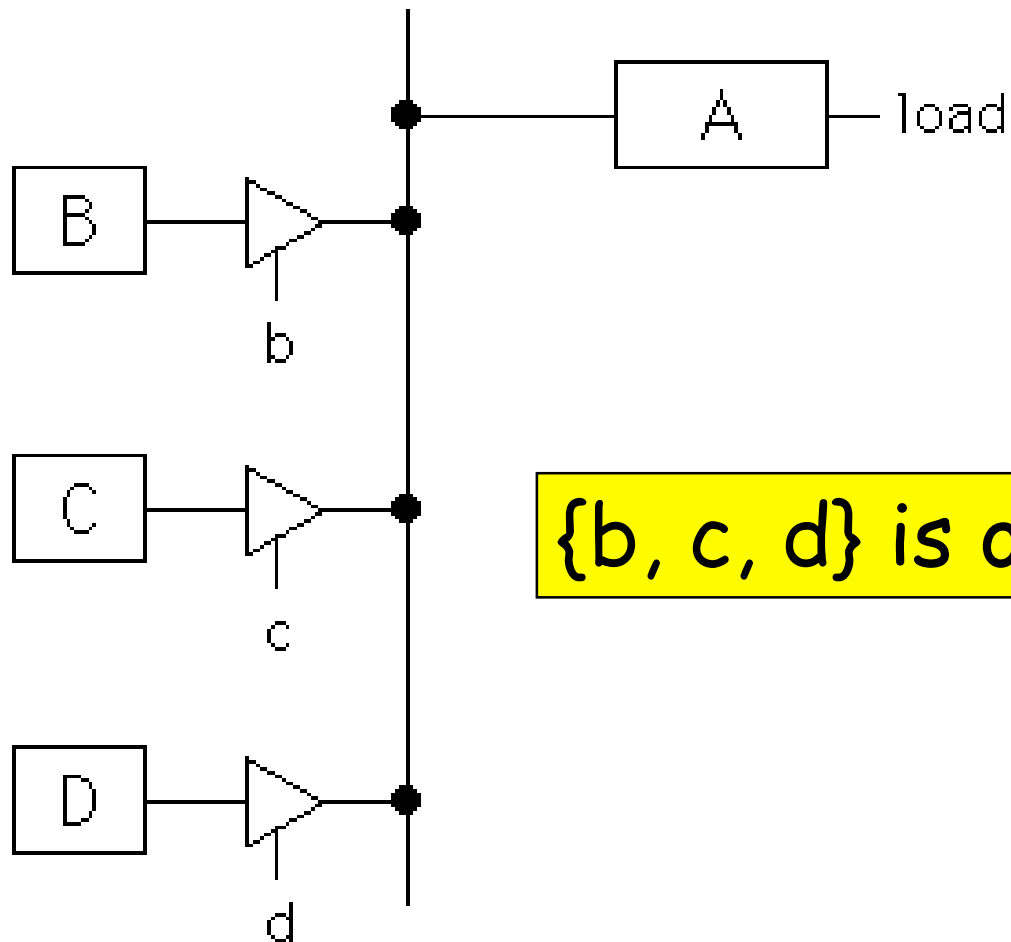

**{b, c, d} is one-hot**


# Bus vs. Multiplexor

---

---

- The bus-type connection allows selection from a large number of inputs without requiring a multiplexor tree or other complex logic.
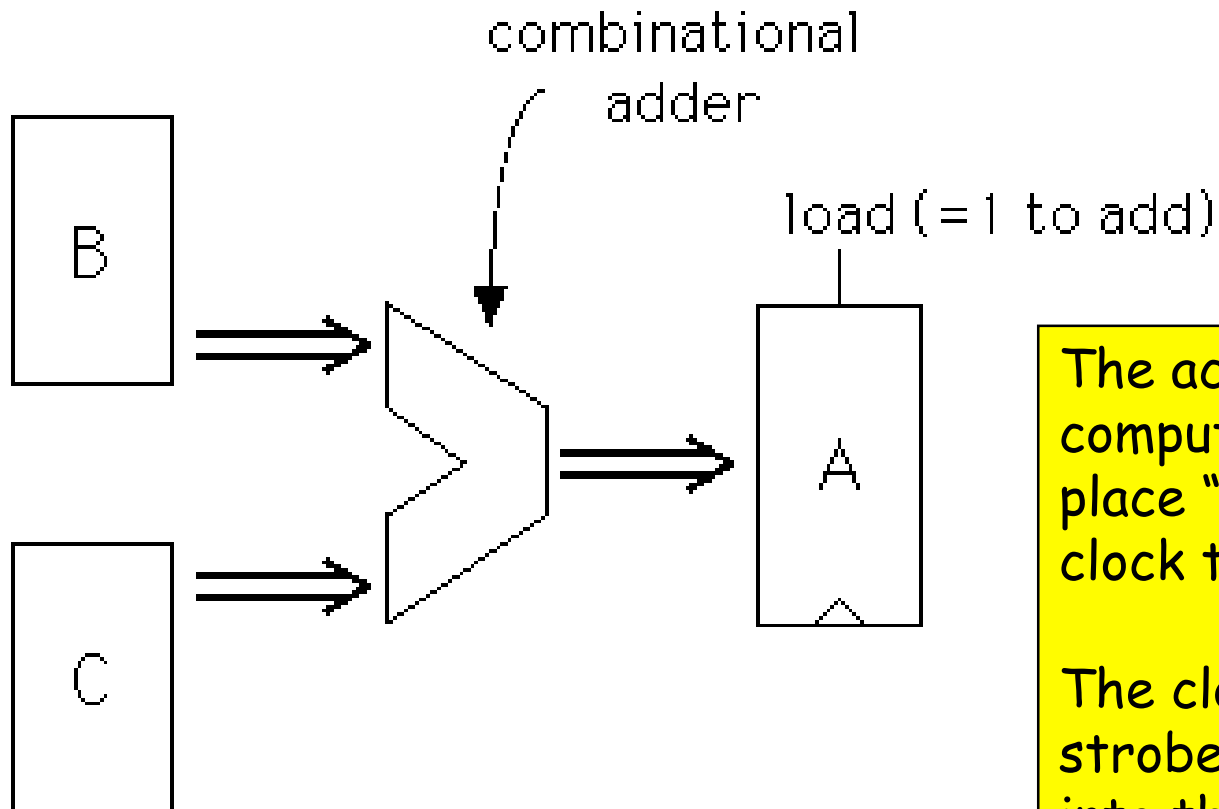
# Computing using Combinational Functions



Java: `A = B + C;`

The actual computation takes place "between" clock ticks.

The clock simply strobes the result into the register.