
Logic Circuits

Robert Keller
November 2012

Gates

- Gates realize logic functions, e.g. electronically.
- Gates can be combined using what is essentially functional programming.
- We give symbolic versions of common logic functions.


and

form 1 table:

x	y	and(x, y)
0	0	0
0	1	0
1	0	0
1	1	1



arguments


results

  


and with >2 inputs

- Because *and* is associative and commutative, the inputs can be regarded as a set with no particular order.



3 inputs

 


7 inputs

or

form 1 table:


x	y	or(x, y)
0	0	0
0	1	1
1	0	1
1	1	1

gate symbol

 


or with >2 inputs

 - Because *or* is associative and commutative, the inputs can be regarded as a set with no particular order.



3 inputs

 


7 inputs

not (inverter)

form 1 table:

x	not(x)
0	1
1	0

gate symbol

 

and, or, implies


- 0 and x is
- 1 and x is

- 0 or x is
- 1 or x is

- 0 implies x is
- 1 implies x is


half-adder (HA) circuit

x	y	carry	sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 

1-bit multiplexer

 - The gate equivalent of if-then-else
- $z = \text{select} ? x : y$




select	x	y	z
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

1-bit demultiplexer

- The gate equivalent of if-then-else
- $y = \text{select} ? z : 0$
 $x = !\text{select} ? z : 0$

z	select	x	y
0	0	0	0
0	1	0	0
1	0	1	0
1	1	0	1

 


implies circuit

form 1 table:

x	y	implies(x, y)
0	0	1
0	1	1
1	0	0
1	1	1

$z = \text{implies}(x, y)$

 

Gate Repertoire

- By "repertoire" we mean a set of gate types, such as (2-input *and*, 2-input *or*, *inverter*).

Universal Repertoire

- A repertoire of *n*-input *and* and *or* gates, and *not*, is **adequate** to realize any switching function.

Proof that {and, or, not} are adequate

- Suppose f is an n -ary switching function.
- Basis: $n = 1$:
 - There are four 1-input functions.
 - $f_{00}(x) = 0 = \text{and}(x, \text{not}(x))$
 - $f_{01}(x) = x$
 - $f_{10}(x) = \text{not}(x)$
 - $f_{11}(x) = 1 = \text{or}(x, \text{not}(x))$
- (The subscripts of these functions are the result column of the truth table.)

x	$f_{00}(x)$
0	0
1	0

x	$f_{01}(x)$
0	0
1	1

x	$f_{10}(x)$
0	1
1	0

x	$f_{11}(x)$
0	1
1	1

Proof Continued: Induction Step

- Suppose that we can realize any n -ary function with {and, or, not}.
- Let f be an arbitrary $(n+1)$ -ary function.
- Then $f(x_0, x_1, \dots, x_n) =$
 $\text{or}(\text{and}(x_0, f(1, x_1, \dots, x_n)),$
 $\text{and}(\text{not}(x_0), f(0, x_1, \dots, x_n)))$
- But $f(0, x_1, \dots, x_n)$ and $f(1, x_1, \dots, x_n)$ are realizable, as they are n -ary functions.

Proof of the equality

- If $x_0 = 1$, the equality is:

- $f(1, x_1, \dots, x_n) =$
 $\text{or}(\text{and}(1, f(1, x_1, \dots, x_n)),$
 $\text{and}(\text{not}(1), f(0, x_1, \dots, x_n)))$

- But the RHS is
 $\text{or}(\text{and}(1, f(1, x_1, \dots, x_n)), \text{and}(0, ______)))$

$$= \text{or}(f(1, x_1, \dots, x_n), 0)$$

$$= f(1, x_1, \dots, x_n)$$

so the equality checks for the case $x_0 = 1$.

Proof of the equality

- If $x_0 = 0$, the equality is:

- $f(0, x_1, \dots, x_n) =$
 $\text{or}(\text{and}(0, f(1, x_1, \dots, x_n)),$
 $\text{and}(\text{not}(0), f(0, x_1, \dots, x_n)))$


- But the RHS is
 $\text{or}(\text{and}(0, ______), \text{and}(1, f(0, x_1, \dots, x_n))))$

$$= \text{or}(0, f(0, x_1, \dots, x_n))$$

$$= f(0, x_1, \dots, x_n)$$

so the equality checks for the case $x_0 = 0$.

Diagrammatic Proof

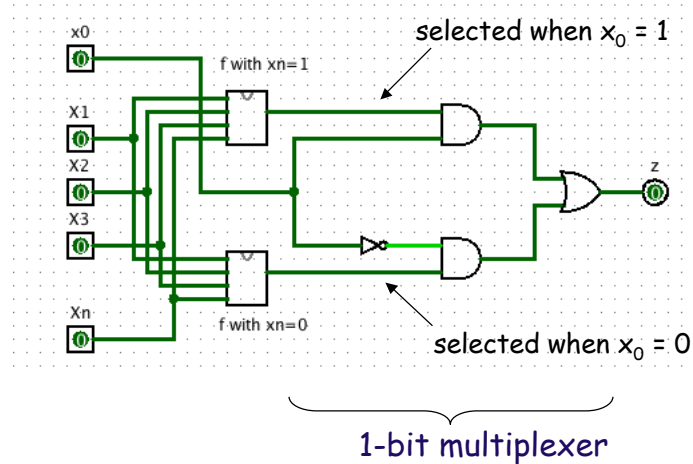

Proof as Synthesis

- The preceding proof determines one synthesis method for an arbitrary switching function:
 - If the function is of 1-ary, it is one of the four basis functions.
 - If the function is $n+1$ -ary, then decompose it into a composition of n -ary functions, *and*, *or*, and *not*.

Synthesis Example

- Synthesis the function f represented by this truth-table:

w	x	y	z
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

Synthesis Example

- Decompose on w

x	y	z
0	0	0
0	1	1
1	0	1
1	1	1

$w=0$

w	x	y	z
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

$w=1$


x	y	z
0	0	1
0	1	1
1	0	1
1	1	0

Synthesis Example

- Decompose each on x

$\begin{array}{c c} y & z \\ \hline 0 & 0 \\ 1 & 1 \end{array}$	x=0	$\begin{array}{c c c} x & y & z \\ \hline 0 & 0 & 0 \\ 0 & 1 & 1 \\ 1 & 0 & 1 \\ 1 & 1 & 1 \end{array}$	w=0	$\begin{array}{c c c c} w & x & y & z \\ \hline 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 1 \\ 0 & 1 & 0 & 1 \\ 0 & 1 & 1 & 1 \\ 1 & 0 & 0 & 1 \\ 1 & 0 & 1 & 1 \\ 1 & 1 & 0 & 1 \\ 1 & 1 & 1 & 0 \end{array}$
$\begin{array}{c c} y & z \\ \hline 0 & 1 \\ 1 & 1 \end{array}$	x=1			
$\begin{array}{c c} y & z \\ \hline 0 & 1 \\ 1 & 1 \end{array}$	x=0	$\begin{array}{c c c} x & y & z \\ \hline 0 & 0 & 1 \\ 0 & 1 & 1 \\ 1 & 0 & 1 \\ 1 & 1 & 0 \end{array}$	w=1	
$\begin{array}{c c} y & z \\ \hline 0 & 1 \\ 1 & 0 \end{array}$	x=1			

Synthesis Example

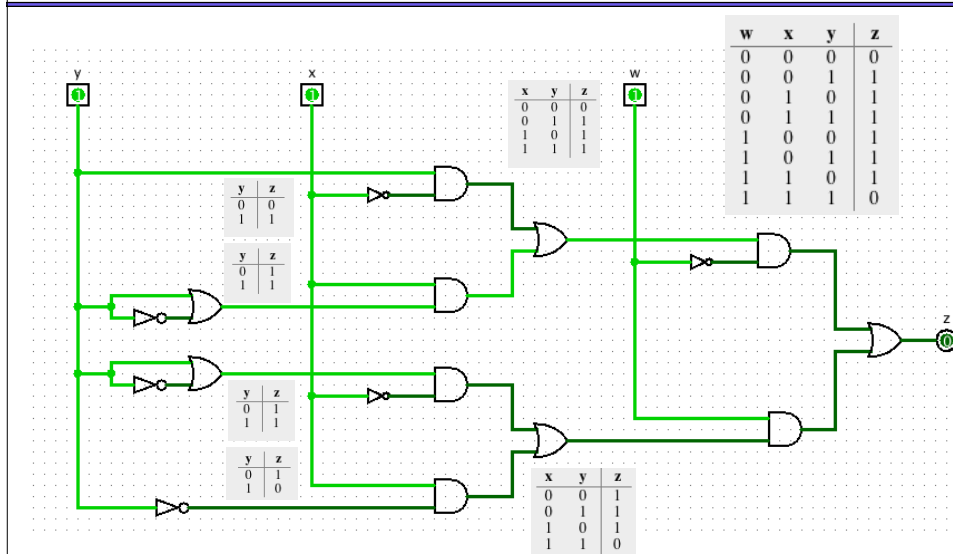

Another Synthesis Method

- A problem with the previous method is that it tends to produce circuits with long paths (= delay).
- The next method reduces this problem.

Minterm Synthesis

- For a given set of variables, a minterm is a product (and) of those variables and their negations.
- Example: 3 variables: x, y, z
 - Some minterms: $xyz', x'yz', \dots$
- Each minterm represents a function that is "on" (1) for exactly one combination of variables
 - e.g. xyz' is on for 110, $x'yz'$ is on for 010.

Minterm Representation

- Any function can be represented as the sum (or) of its minterms.
- These correspond to the rows of the truth table for which the function is 1.

Minterm Example

w	x	y	z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

Minterm representation is

$$w'xy' + w'xy + wx'y + wxy'$$

corresponding to rows


010 011 101 110

numbering


$$\Sigma(2, 3, 5, 6)$$

Minterm Synthesis

- Use "rails" for clarity

 


Minterm Synthesis

 


$$w'xy' + w'xy + wx'y + wxy'$$


Illustrating Combinations

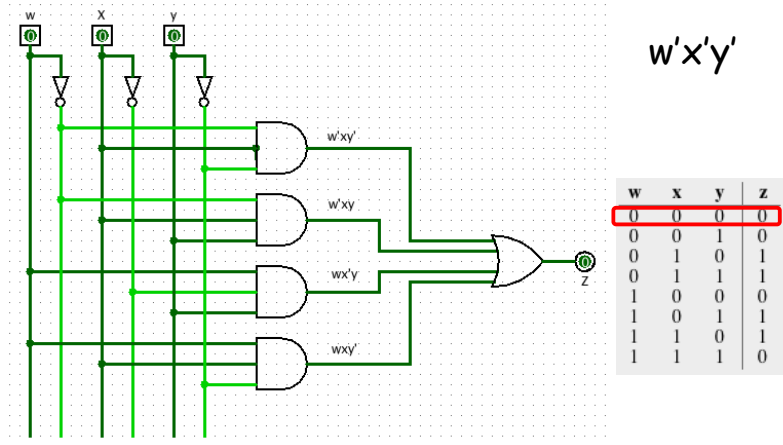


Illustrating Combinations

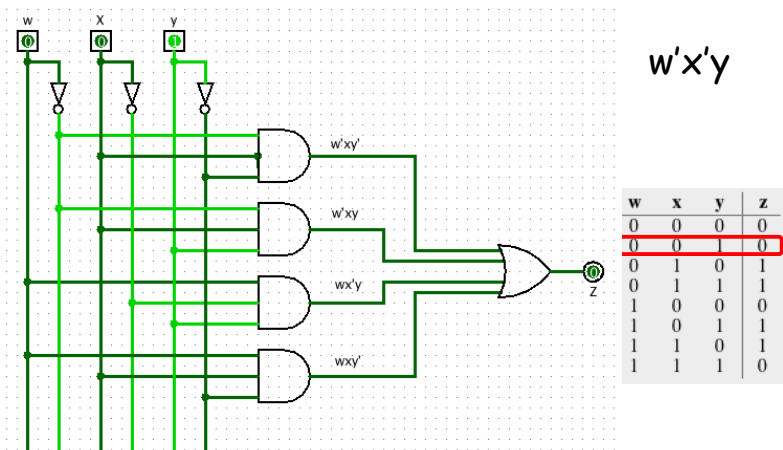


Illustrating Combinations

 

Illustrating Combinations

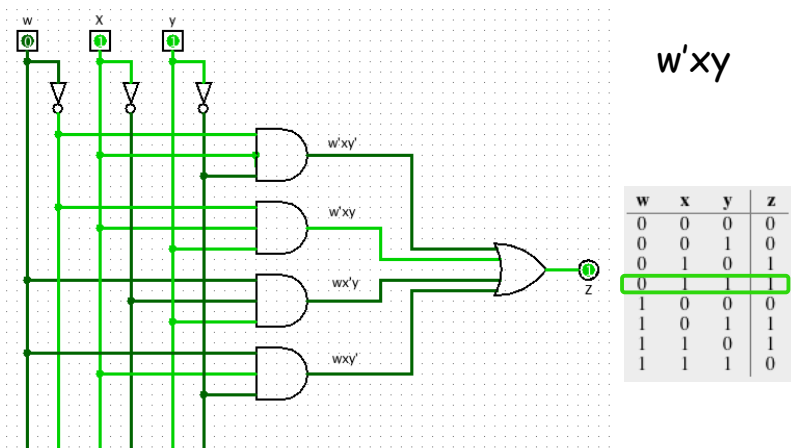


Illustrating Combinations

 

$wx'y$

w	x	y	z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0


Illustrating Combinations

 


$wx'y$

w	x	y	z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

Illustrating Combinations

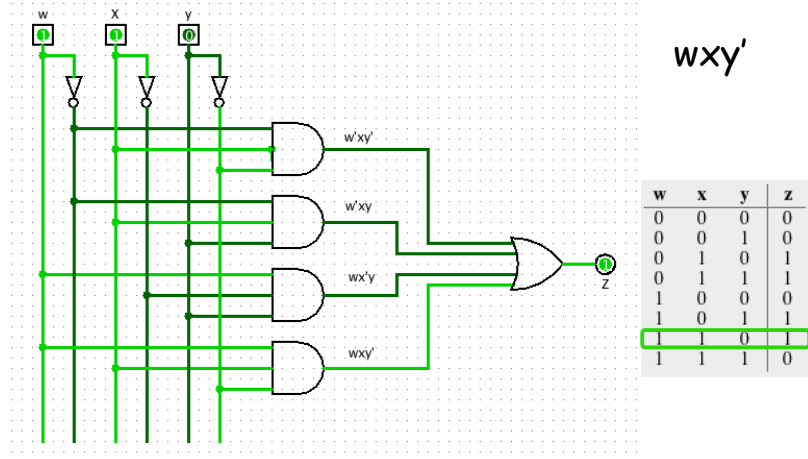

Illustrating Combinations

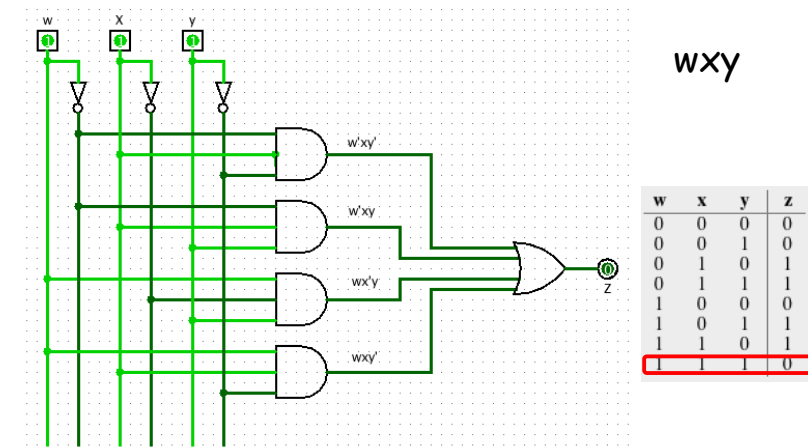

A Universal Repertoire of One Gate Type


- nand = "not and"

nand

form 1 table:


x	y	nand(x, y)
0	0	1
0	1	1
1	0	1
1	1	0

gate symbol

 

bubble

logically equivalent to:

 

Universality of Nand

- Consider any minterm realization, e.g.
 $m_1 + m_2 + m_3$
- To realize this with a final nand, use a version of deMorgan's law:

$$\begin{aligned} m_1 + m_2 + m_3 &= (m_1' m_2' m_3')' \\ &= \text{nand}(m_1', m_2', m_3') \end{aligned}$$


But each minterm m_i is an **and** of variables or their negations. So each m_i' is a **nand** of the same variables and their negations.

not from nand




Nand Minterm Example

and/or

 


nand

 

Another universal set: {nor}

- *nor* is the negation of *or*
- Show that any minterm form can be re-expressed using only *nor*.

nor gate symbol

 

Number of Functions

- For n variables, how many minterms are there?
- How many distinct n -ary functions are there?

Building Blocks


- For functions of large arity, it is sometime impractical to synthesize by previous methods: Tables may be too large.
- In such cases, it is common to use standard building blocks to construct circuits.

xor (exclusive or) building block

form 1 table:

x	y	xor(x, y)
0	0	0
0	1	1
1	0	1
1	1	0



minterm realization

 

xor with >2 inputs

- Because *xor* is associative and commutative, the inputs can be regarded as a set with no particular order.

- xor symbols:

  

Full Adder (FA)

- The full adder is a building block sometimes used to construct adders of arbitrary length.
- Unlike the Half-Adder, an FA has:
 - 3 inputs: x, y, carryIn
 - 2 outputs: sum, carryOut


Full Adder (FA)

carryIn	x	y	carryOut	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Each output can be synthesized as a separate function.


sum is a 3-input xor

CarryOut is a 2/3 majority

 

n-stage Ripple-Carry Adder

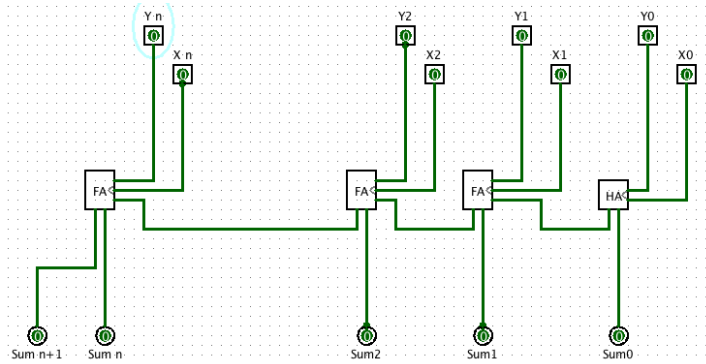
- This adder is easy to make, but slow for large n .



Gate-Depth

- The longest path in # of gates through the circuit determines the delay. This is called the "gate depth".
- An n -bit ripple carry adder has gate depth $O(n)$.

Carry-Select Adder Construction

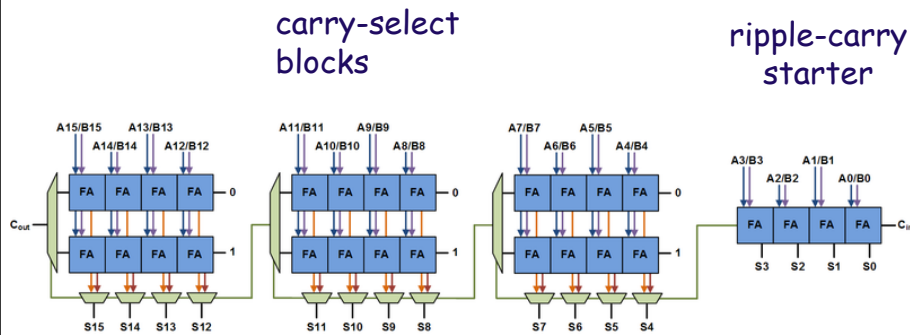

In general, \sqrt{n} blocks of size \sqrt{n} can be used.

Note that this is a Divide & Conquer approach.

http://en.wikipedia.org/wiki/Carry-select_adder

Even Faster Addition


- A lower-bound for n -bit addition is $\Omega(\log n)$. (Ω , rather than O , is used for lower bounds).
- The Kogge-Stone adder achieves this bound.
- This is an example of a "digital" (radix-based) approach.

http://en.wikipedia.org/wiki/Kogge%E2%80%93Stone_adder


Multiplier Problem

- In the current assignment, you are asked to construct a multiplier.
- Consider using a "digital" method, wherein the multiplier's bits are used to decide whether or not to include the multiplicand at various points in the product computation.
- Essentially use the algorithm learned in school, but in binary.
- One approach is to use a "controlled" version of the ripple-carry adder as a building block.

A Partial Multiplier Tester

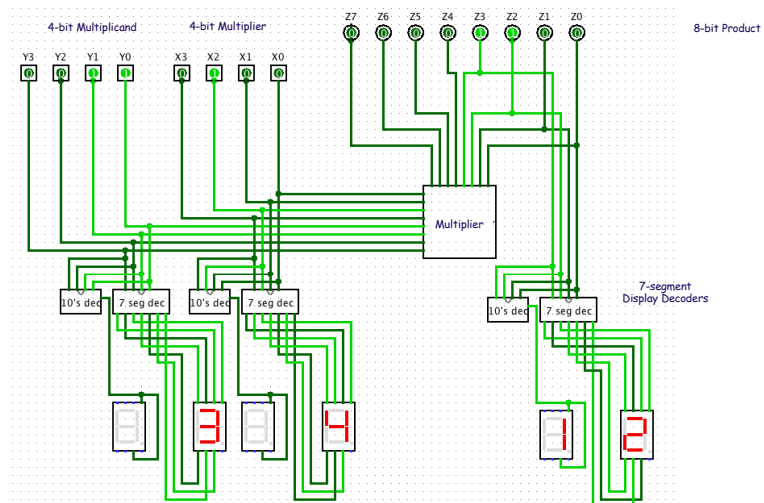

 Note: Decimal read-out for product is currently limited to 0 to 15.



Programmable Logic Arrays (PLAs)


Elements with Memory

- So far we have discussed "combinational" elements. The output, after all signals have fully propagated, is a function of the input, without regard to history.
- More capabilities are available through elements with memory. These allow computations to be **sequential**, rather than just combinational.

Flip-Flop: A basic memory unit

- The flip-flop remembers the value (0 or 1) it was last assigned.
- Assignment normally is done at the tick of a *clock*.
- Circuits constructed this way are called **clocked sequential circuits**, or **synchronous circuits**.

D Flip-Flop with Clock

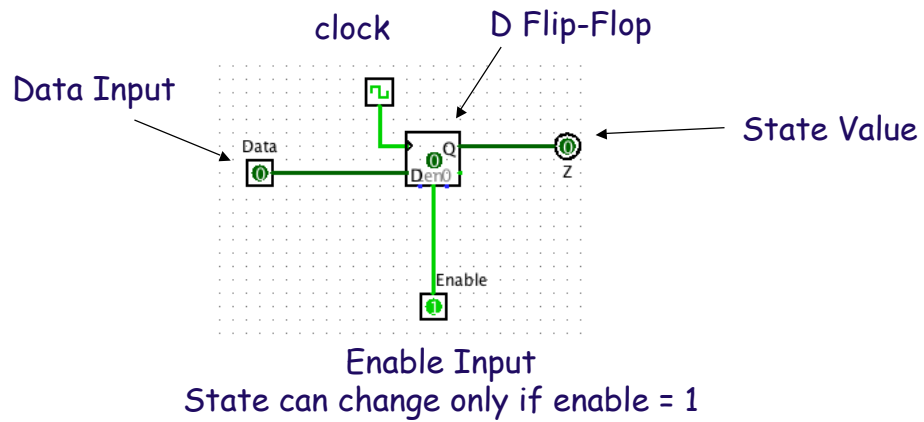


D Flip-Flop Behavior

Clock(460,390)	Enable	Data	D Flip-Flop(520,420)	Z
			0	
			0	
1	1	0	0	0
0	1	0	0	0
1	1	0	0	0
0	1	0	0	0
0	1	1	0	0
1	1	1	1	1
0	1	1	1	1
1	1	0	1	1
0	1	0	1	1
1	1	0	0	0
1	0	0	0	0
0	0	0	0	0
1	0	0	0	0
1	0	1	0	0
0	0	1	0	0
1	0	1	0	0

Annotations in the table:

- Two horizontal arrows labeled "Clock ticks" point to the clock input column at rows 7 and 11.
- Two horizontal arrows labeled "Data remembered" point to the data input column at rows 7 and 11.
- A vertical bracket labeled "Disabled" spans the rows where Enable = 0 (rows 13-16).

 Sequential Circuit remembers whether Data was ever 1.




Clock(460,390)	D Flip-Flop(520,420)	Data	Enable	Was Data ever 1?
1	0	0	1	0
0	0	0	1	0
1	0	0	1	0
1	0	1	1	0
0	0	1	1	0
1	1	1	1	1
0	1	0	1	1
1	1	0	1	1
0	1	0	1	1
1	1	0	1	1
0	1	0	1	1

Data remembered forever

State Diagram

Input = Value of Data at Tick

 


State = Value of Q

Sequential Adder

- Using a D Flip-Flop, the circuit can remember the carry from one tick to the next.
- Use two D Flip-Flops for input, one for output, one for carry.

Sequential Adder

 
adds X and Y least-significant bit first to get Z



←
 00111000110 X right to left
 00111011100 Y right to left
 01110100010 Z right to left
 01111011100 Carry right to left

Clock(460,390)	Carry	X	Y	Z
0	0	0	0	0
1	0	0	0	0
0	0	0	0	0
0	0	1	0	0
1	0	1	0	1
1	0	0	0	1
0	0	0	0	1
0	0	1	1	1
1	1	1	1	0
0	1	1	1	0
0	1	0	1	0
1	1	0	1	0
0	1	0	1	0
1	1	0	1	0
1	1	0	1	0
0	1	0	0	0
1	1	0	0	1
0	0	0	0	1
0	0	1	0	1
0	0	1	1	1
1	1	1	1	0
0	1	1	1	0
1	1	1	1	1
1	1	1	1	1
0	1	1	1	1
0	1	0	1	1
0	1	0	0	1
1	0	0	0	1
1	0	0	0	0
0	0	0	0	0

State Diagram for Adder

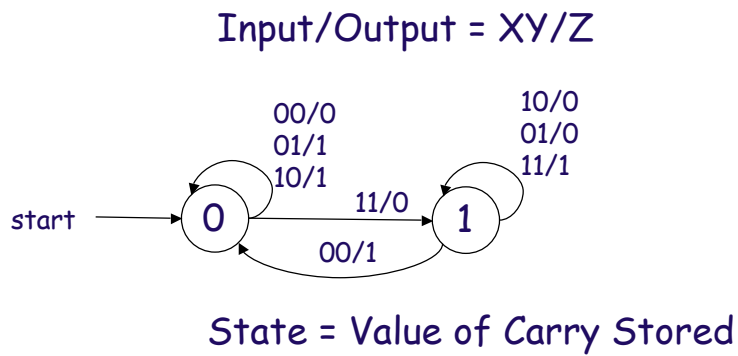


Flip-Flop Construction

- Flip-Flops can be constructed from basic gates.
- Broad-categories, of increasing sophistication, are:
 - Latch
 - Gated Latch, or Level-Triggered Flip-Flop
 - Edge-triggered Flip-Flop

Latches

 - A latch is the basic memory structure for a flip-flop.
- Here is one possible latch, called set-reset (SR), constructed from **nor** gates:




Shown is the **reset** state:
 $Q = 0, Q' = 1.$

Latch Operation


- Only one of S, R should be 1 at any given time.
- When S is raised, the latch goes to the **set** state ($Q = 1, Q' = 0$).
- When S is lowered, the set state is maintained.
- When R is raised, the latch goes to the **reset** state ($Q = 0, Q' = 1$).
- When R is lowered, the set state is maintained.

Latch Operation

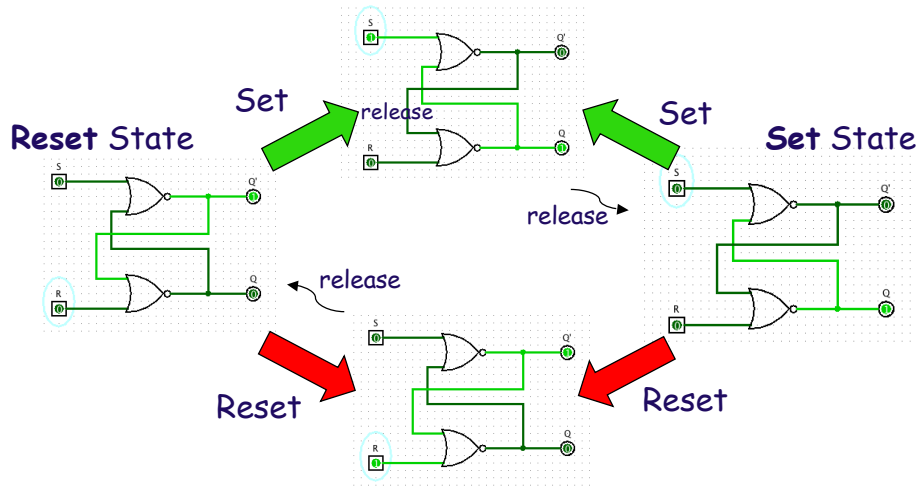

Gated Latch

 
- This enables or disables the latch set and reset.
- Enable line is also called "Strobe".
- D is for "Data"




Registers

- A flip-flop is a 1-bit register.
- Flip-flops can be combined in parallel to produce multiple-bit registers.
- Contents of one register can be transferred to another on clock tick

Straight Register Transfer

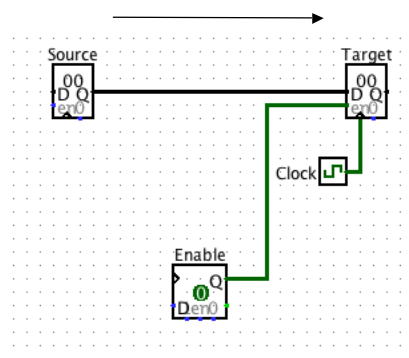


Register Transfer with Combinational Functions

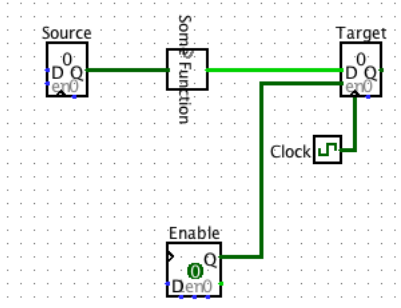


Extra In-Register Functions

 - Shift (Left or Right)
- Increment or Decrement
- Zero
- Complement



[http://en.wikipedia.org/wiki/Flip-flop_\(electronics\)](http://en.wikipedia.org/wiki/Flip-flop_(electronics))

Sequential Multiplier

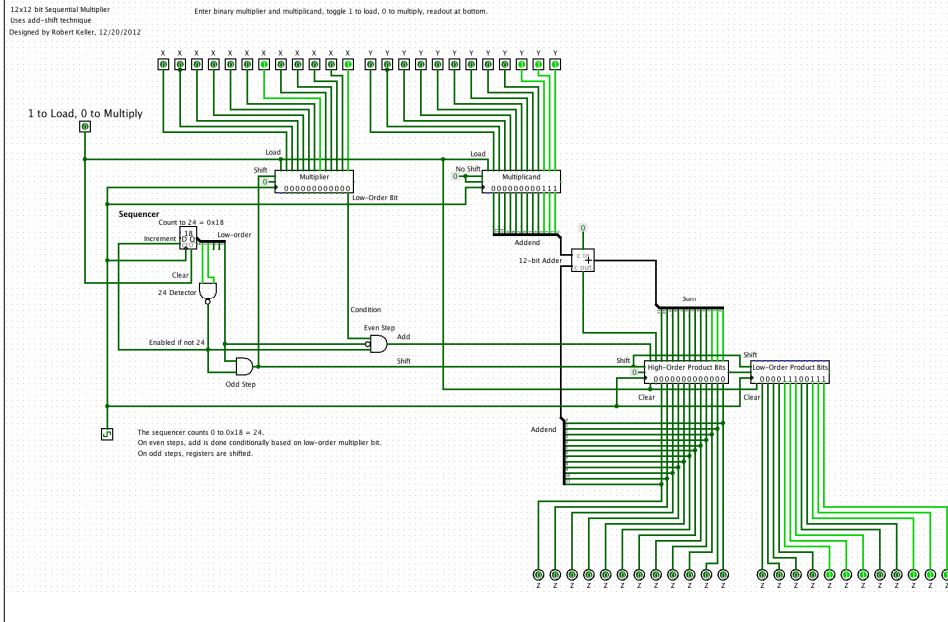


Implementing General Finite-State Machines

- Finite-State machines have many uses in computers, including registers and sequencers.
- Here we deal with the general problem of implementing an FSM starting with a state-transition diagram.


Memory Considerations

- The state of the machine has to be stored in some kind of memory, usually flip-flops.
- The flip-flop values represent an **encoding** of the current state.

State-Machine Example

 


Target FSM Architecture

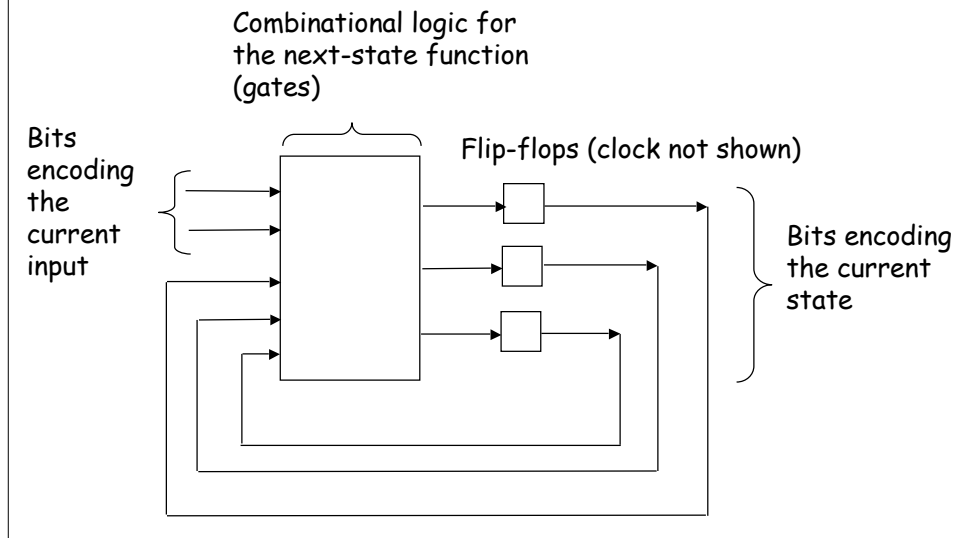

Input and State Encodings

 - Encodings may be pre-specified, or at the discretion of the designer.
- Example: Suppose the input is pre-specified to be {0, 1}, while the state encodings are discretionary.



Encoding State Set

- State set is {0, 1, 2}.
- What are the possible ways to encode it in binary?
- What is the fewest number of bits?


Binary Encoding

- $0 \rightarrow 00$ (\rightarrow = "is encoded as")
- $1 \rightarrow 01$
- $2 \rightarrow 10$

Gray-Code Encoding

- 0 → 00
- 1 → 01
- 2 → 11

General Gray-Code Pattern: Reflection

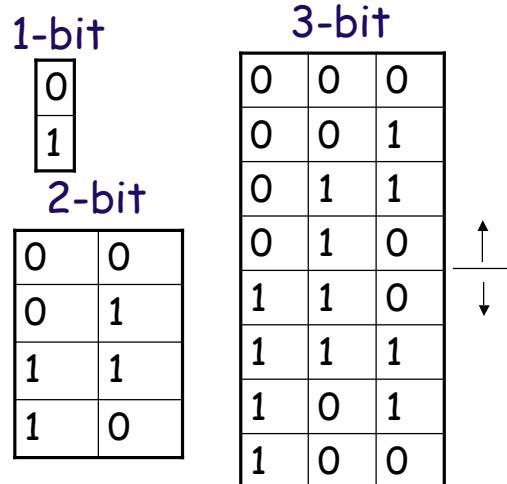

One-Hot Encoding

- 0 → 100
- 1 → 010
- 2 → 001


"Thermometer" Encoding

- 0 → 100
- 1 → 110
- 2 → 111


Simplest Logic

- One-Hot Encoding often yields simplest design.
- However, it is expensive if the number of states is large (n flip-flops for n states, vs. $\text{ceil}(\log(n))$ possible).

One-Hot Version

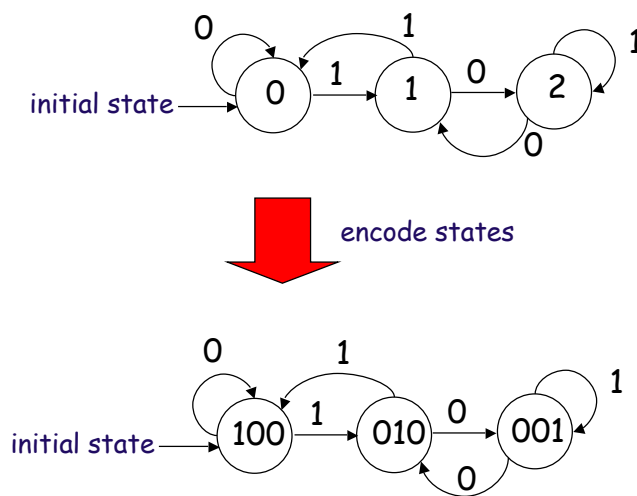


 For One-Hot, logic functions can be read off from the state diagram




- Let the input variable be x .
- Let the state variables be $y_1y_2y_3$ (initially 100).
- Then in combinational logic:
 - next $y_1 = y_1x' + y_2x$
 - next $y_2 = y_1x + y_3x'$
 - next $y_3 = y_2x' + y_3x$
- Note that in a one-hot design, the negations of flip-flop values are not needed.


First Equation

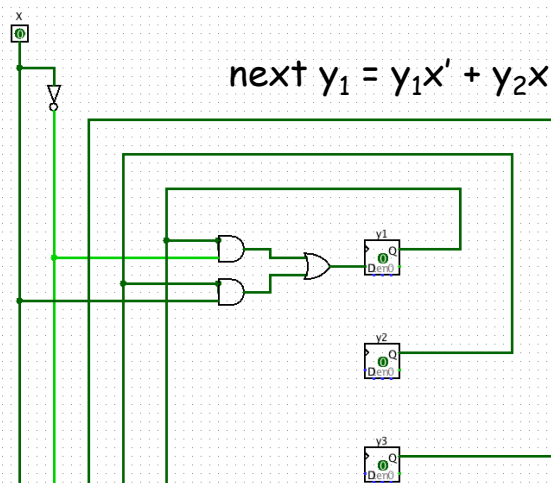

Final Design

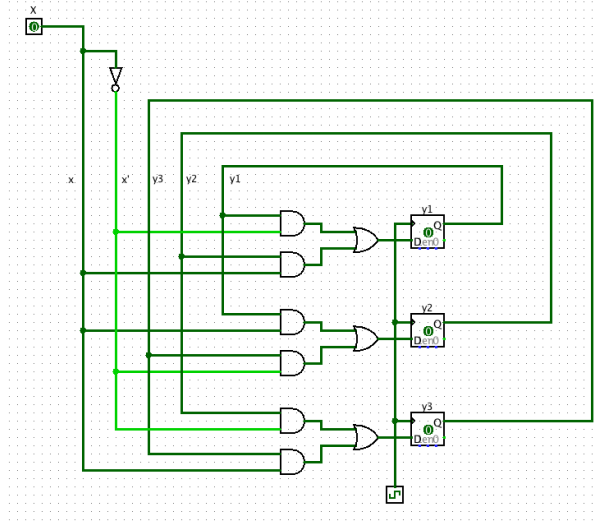

Check Operation

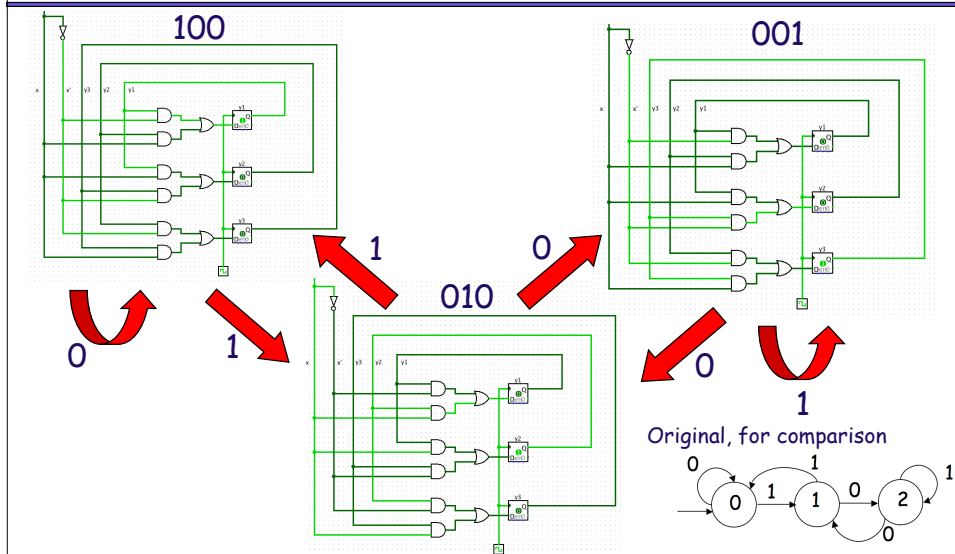


Using a Different State Encoding

- To demonstrate, let's use the Gray-code encoding:
 - 0 → 00
 - 1 → 01
 - 2 → 11

Transition Table

 - Here is the state-transition function in tabular form:



Next State		Input	
		0	1
Current State	0	0	1
	1	2	0
	2	1	2

Edit the States

- Carefully replace each state with its corresponding encoding:

0 → 00, 1 → 01, 2 → 11

Next State		Input	
		0	1
Current State	00	00	01
	01	11	00
	11	01	11

Split the Table into Separate Tables for Each Flip-Flop

Next State		Input	
		0	1
Current State	00	00	01
	01	11	00
	11	01	11

Next y_1		Input		Next y_2		Input	
		0	1			0	1
Current State	00	0	0	00	0	1	
	01	1	0	01	1	0	
	11	0	1	11	1	1	

Read Off Equations from Each Table


Next y_1		Input		Next y_2		Input	
		0	1			0	1
Current State	00	0	0	Current State	00	0	1
	01	1	0		01	1	0
	11	0	1		11	1	1

$$\text{next } y_1 = y_1' y_2' x' + y_1 y_2 x$$


$$\text{next } y_2 = y_1' y_2' x + y_1' y_2 x' + y_1 y_2$$

Note that we need to use negations of flip-flop values, unlike with one-hot encoding. Also, we combined the last two minterms for the second function.

Design for Gray-Code Encoding

 

Check for Gray-Code Version Operation

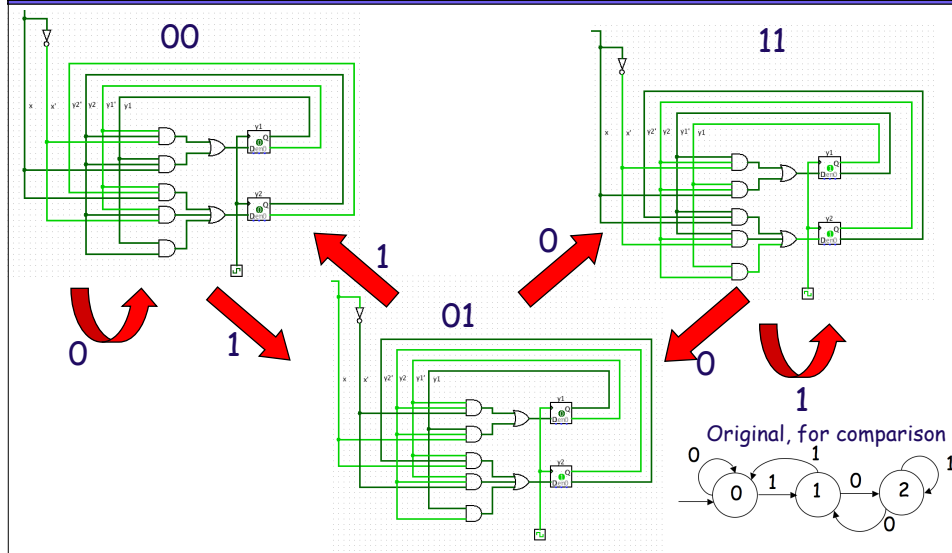

Adding Output

- The preceding discussion only addresses the state-transition aspect of finite-state machines.
- To do useful work, our machine may need output as well.

Output Models


- There are two general models for output:
 - Attach output to transitions (called the **Mealy model**, after George H. Mealy)
 - Attach output to states (called the **Moore model**, after E.F. Moore)
 - A special case of just two possible output values is called an **acceptor**.

Acceptor

- Each state of an acceptor is either
 - Accepting, or
 - Rejecting
- The convention is that accepting states are doubly circled.
- There can be multiple accepting states.


Acceptor Example

 This acceptor accepts sequence that are multiples of 3 in binary, msb-first, e.g. 0, 11, 110, 1001, 1100, ...



Acceptor Example 2

 This acceptor accepts sequence that are *not* multiples of 3 in binary, msb-first, e.g. 1, 10, 100, 101, ...




Note on Acceptance

- Acceptance and Rejection apply to the amount of the input sequence seen so far. They are generally not final conditions.
- It is possible to go from accept to reject and back, by providing more input.


Acceptance \rightarrow Output

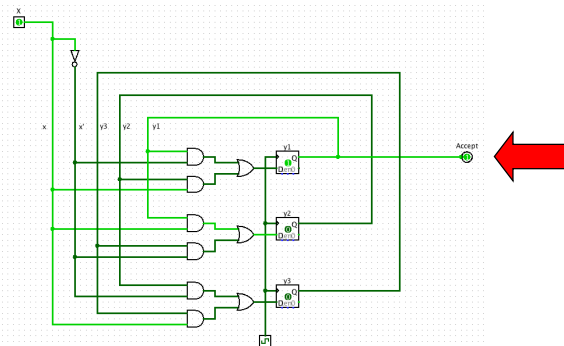- We can assign an output of 1 to acceptance, 0 to rejection using combinational logic. For multiple-of-3, one-hot:



Acceptance \rightarrow Output

 
- 1 to acceptance, 0 to rejection using combinational logic. For multiple-of-3, Gray code:



Mealy Model

- The output is attached to transitions, but a transition comes from a state and is based on an input.
- Therefore the output is a combination of the current state and the input.
- This output can be "captured" by flip-flops. This was indicated back on the sequential binary adder example.

Mealy Model Example

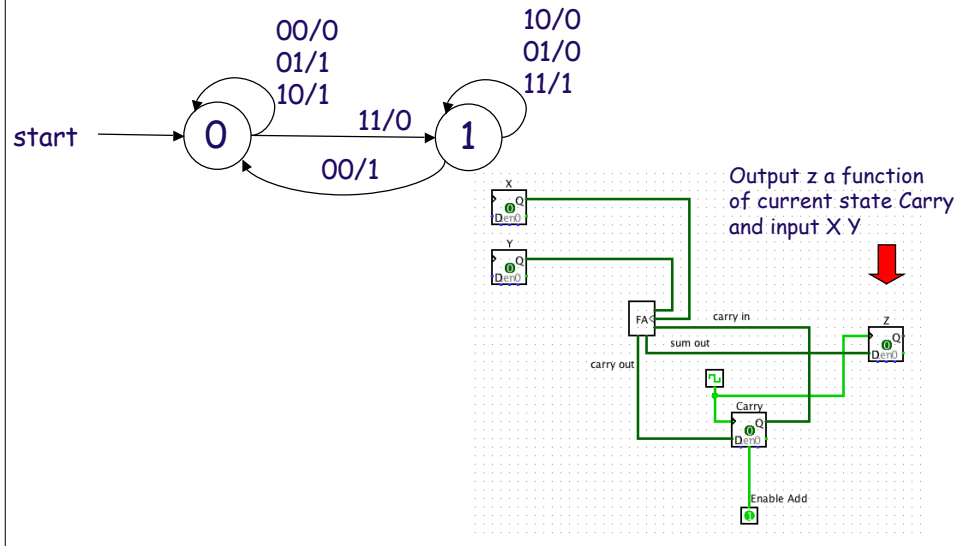

Subsequent Discussions

- Finite-State Machines in the abstract
- Regular (type 3) languages: languages accepted by finite-state acceptors
- Regular expressions