

## The CS 5 Times

### Dormitory Destroyed

Claremont (PP): A Harvey Mudd College dormitory was left in shambles Tuesday after an unexpected low-frequency resonance caused it to self-destruct.

"I didn't mean any harm," reported a shaken student. "I was doing my CS lab, and I thought it would be cool to share my sounds with the other Westies, so I hooked my computer up to the dorm speakers. Who knew that 42 Hertz was a special frequency?"

Rescuers worked frantically to recover the student's hard drive, which reportedly contained notes for an upcoming physics exam. At press time, the drive remained buried under tons of rubble, and hope for a positive outcome was fading. "I'd give anything for a copy of the Lorentz velocity transformation equations," wailed the distraught student.

Upon hearing of this offer, North dorm residents



"West" dormitory after unfortunate incident.


Read Sections 4.3.5-4.4!




## A 1-Bit Memory




This stuff is truly unforgettable!

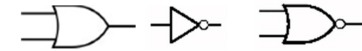


$$\text{OR} + \text{NOT} = \text{NOR}$$

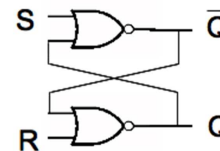


## A 1-Bit Memory

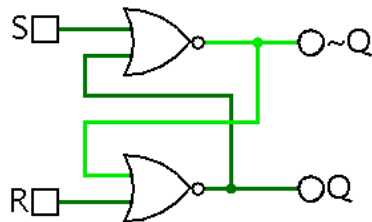


## Setting a 1-Bit Memory

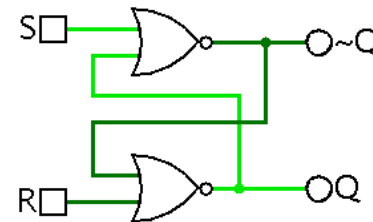

## Initializing a 1-Bit Memory

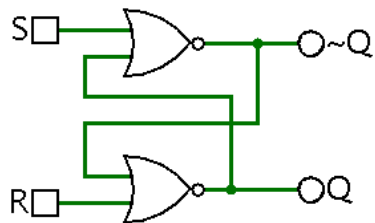


## From S-R Latches to D-Latches

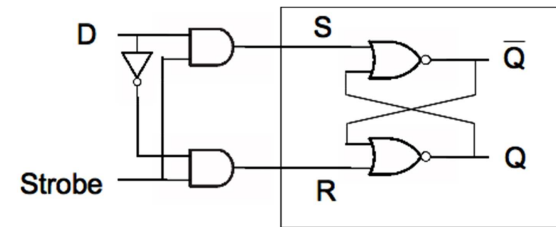


Worksheet!


## A Random Access Memory (RAM)

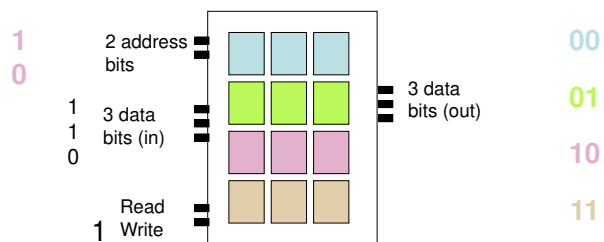


## A Random Access Memory (RAM)

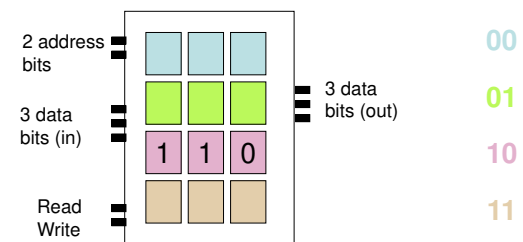


## A Random Access Memory (RAM)

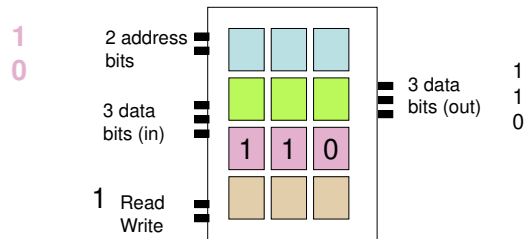


## A Random Access Memory (RAM)

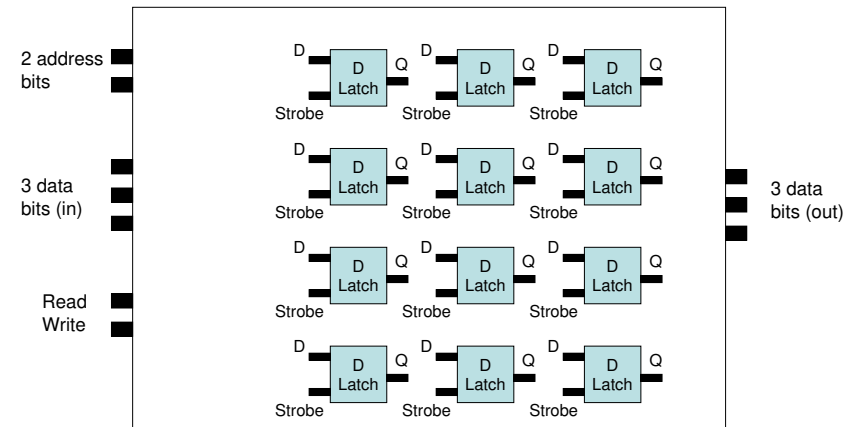


## A Random Access Memory (RAM)

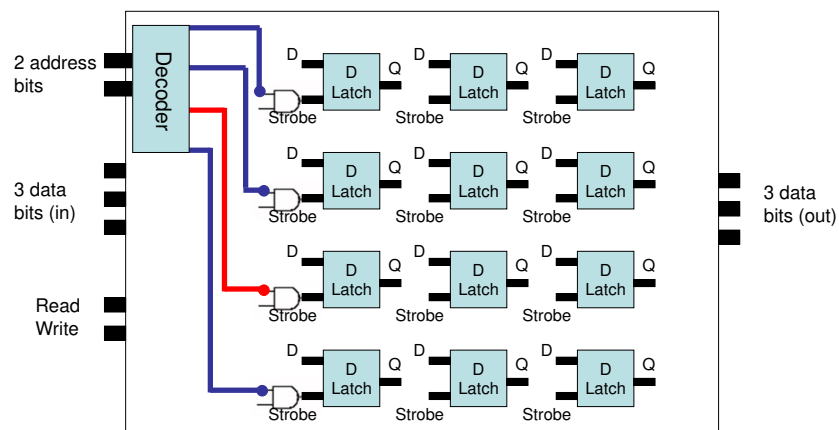


## A Random Access Memory (RAM)

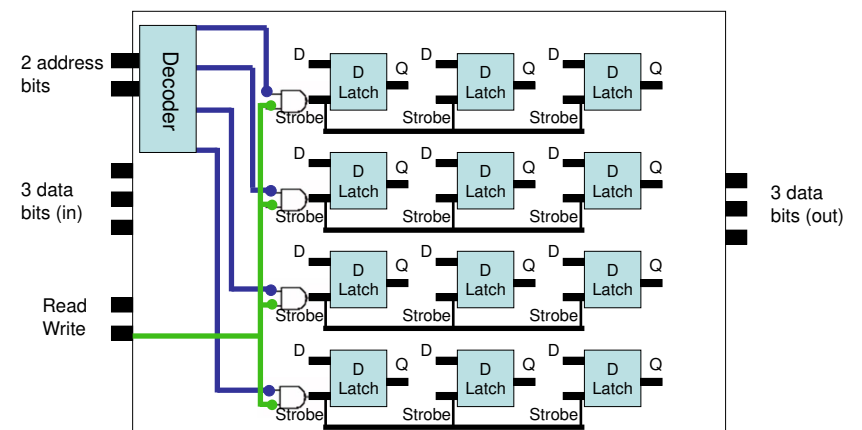


## A Random Access Memory (RAM)

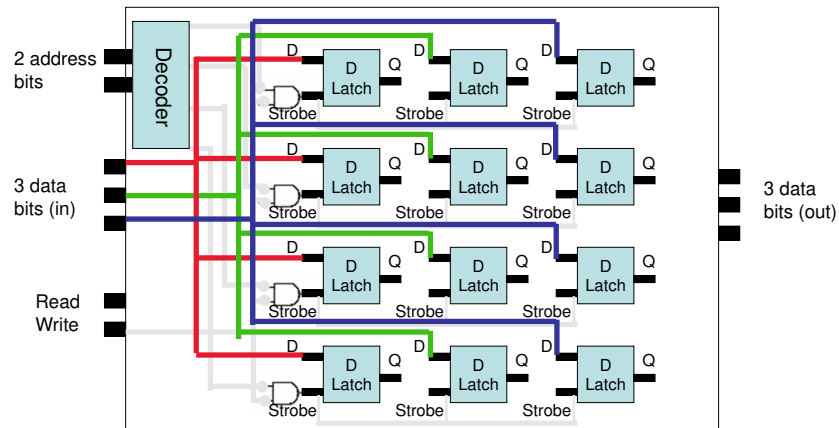


## Small Memory, “Big” Memory...

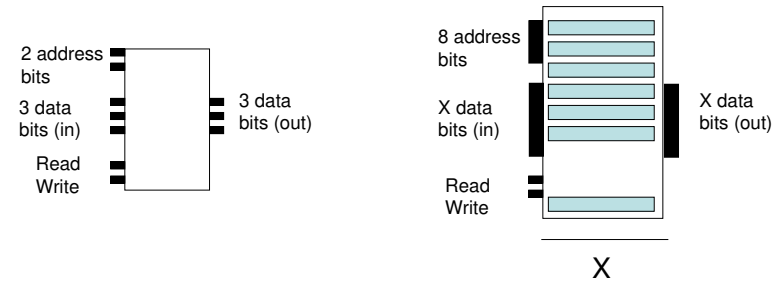


## A “Calculator”

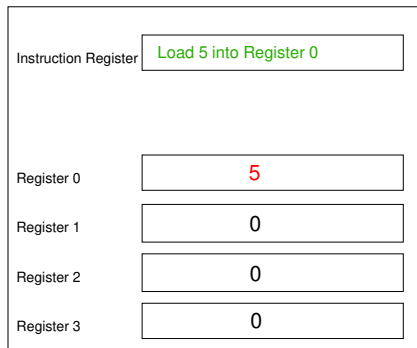


## A “Calculator”

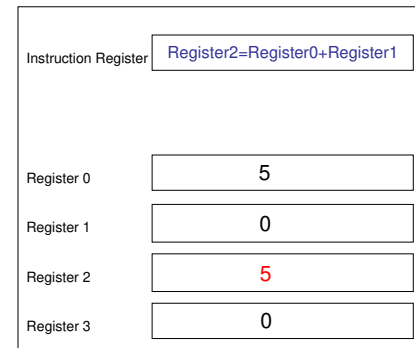


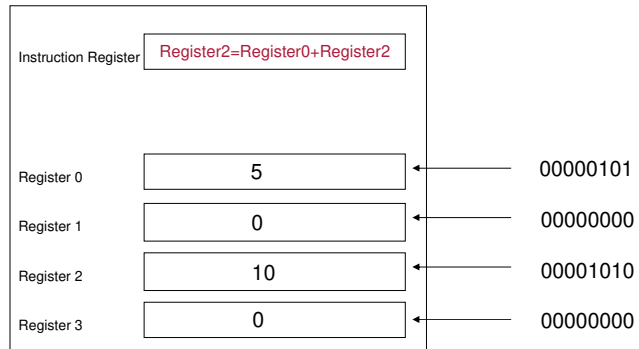01	Subtract	
10	Subtract	

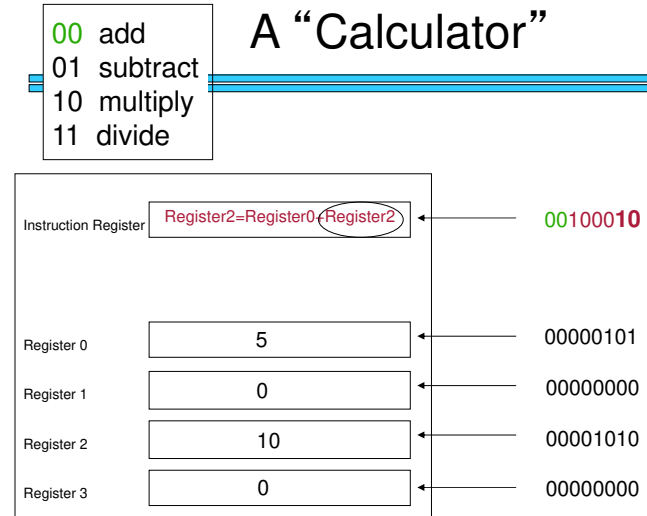


01	subtract	
02	add	

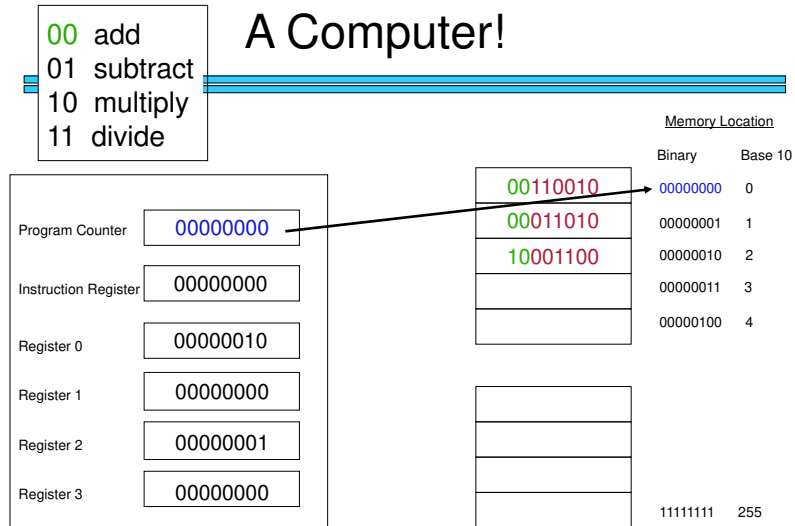

Central Processing Unit (CPU)

## Memory

01	subtract	
02		

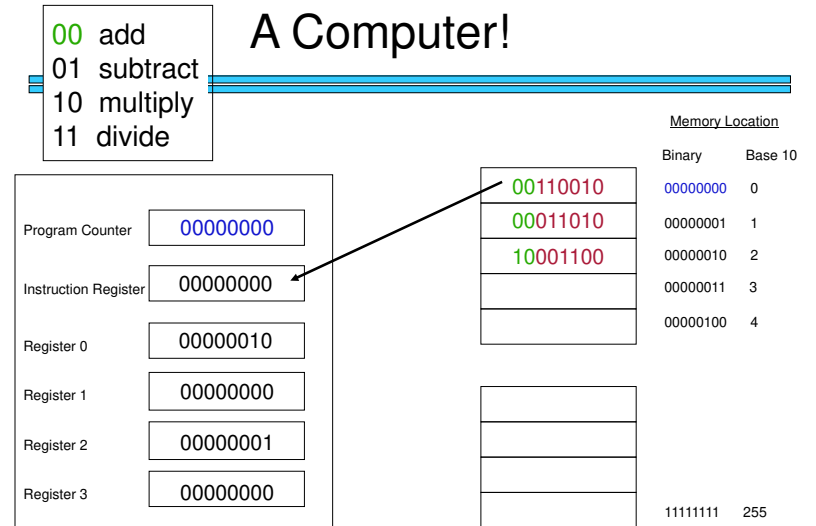


Central Processing Unit (CPU)

## Memory


- 00 add
- 01 subtract
- 10 multiply
- 11 divide

## A Computer!

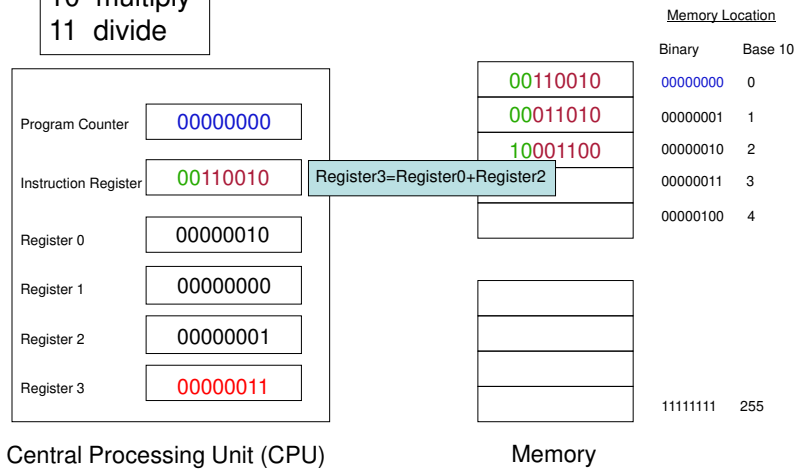


- 00 add
- 01 subtract
- 10 multiply
- 11 divide

## A Computer!

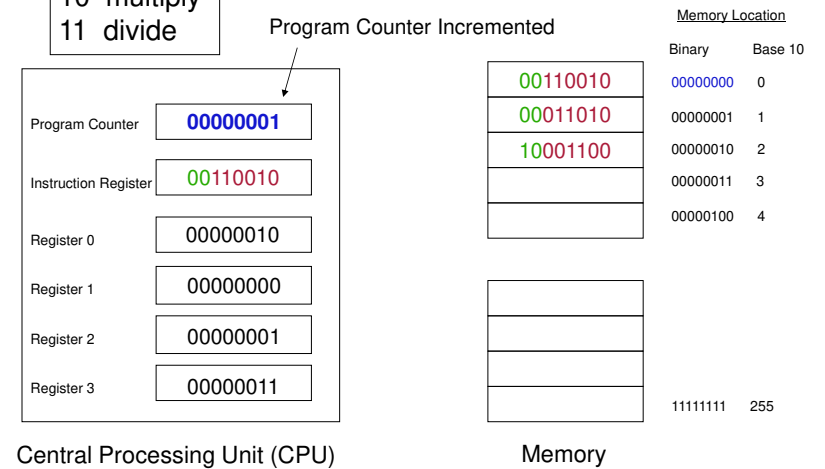


- 00 add
- 01 subtract
- 10 multiply
- 11 divide

## A Computer!

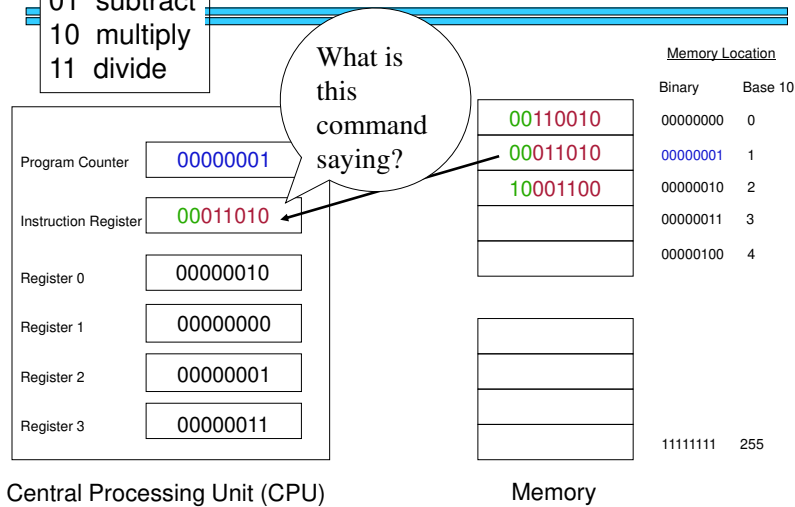


- 00 add
- 01 subtract
- 10 multiply
- 11 divide

## A Computer!

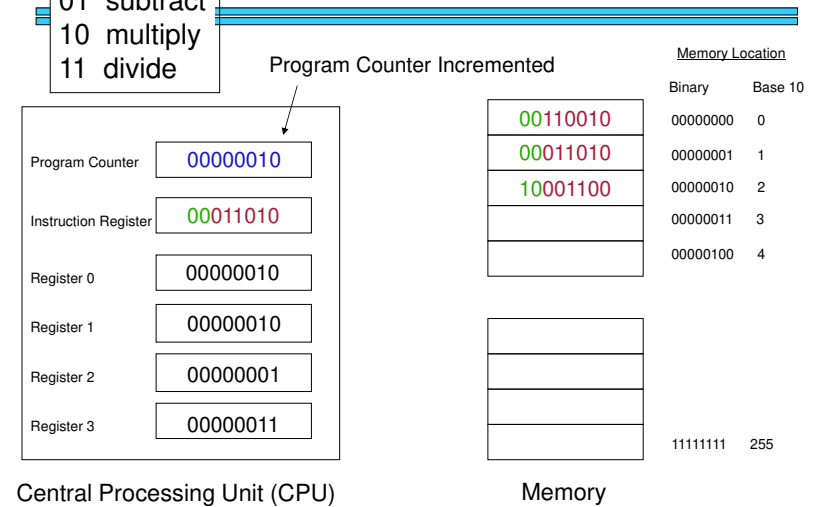


00 add  
01 subtract  
10 multiply  
11 divide

## A Computer!

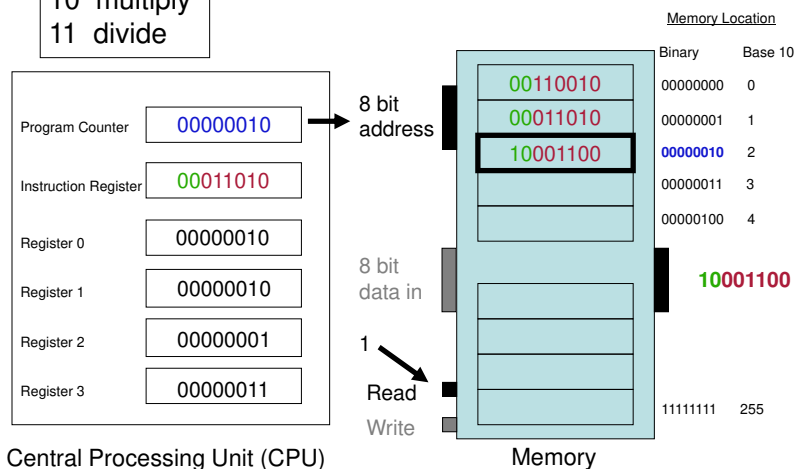

00 add  
01 subtract  
10 multiply  
11 divide



## A Computer!

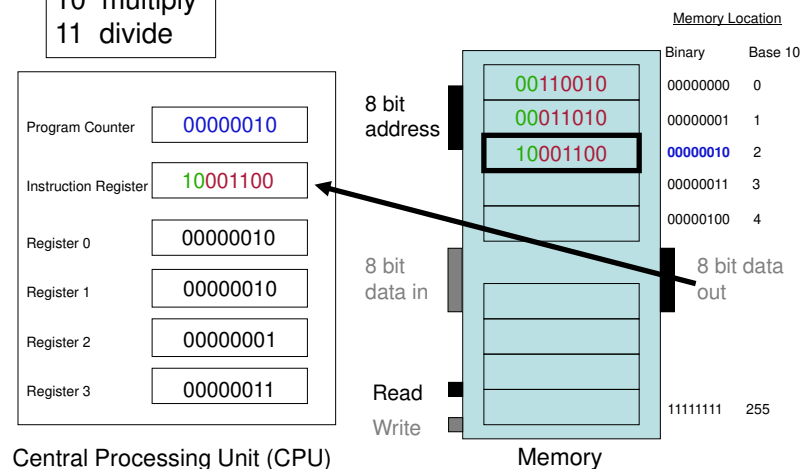

## The von Neumann "Architecture"



John von Neumann

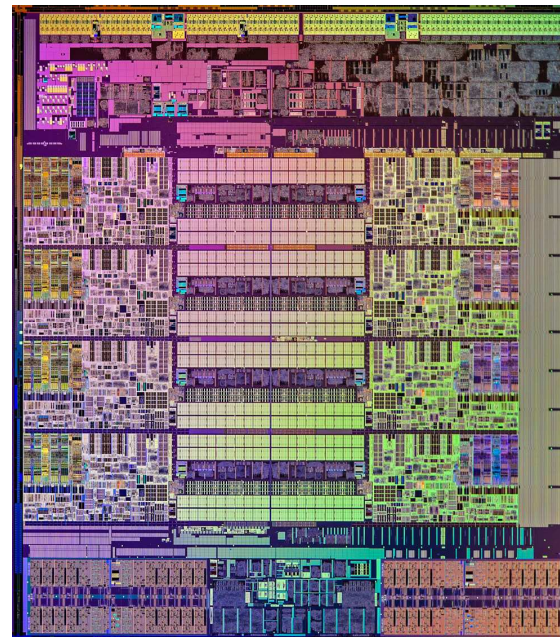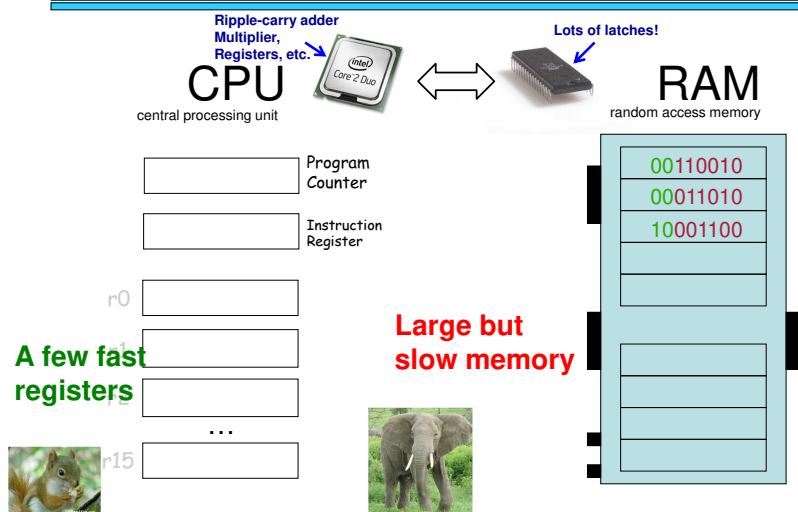

2014  
Intel Haswell-E  
Up to 4 GHz clock  
64-bit processor (8 of 'em!)  
1.4 billion transistors  
22 nm feature size



It doesn't  
look all that  
fast to me!



## A Short Aside...

CPU



16 Registers ("Bytes")

1 cycle


Actual  
time:

$<10^{-9}$  sec

If "cycle"

= 1 sec    1 sec

Main Memory  
(RAM)

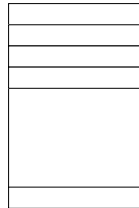

$10^9$  "Bytes" of  
memory

200 cycles

$<10^{-7}$  sec

Disk Drive



$10^{12}$  "Bytes" of  
memory

? cycles

$<10^{-2}$  sec