
 


Composing circuits


4-bit Ripple-Carry Adder

 

Now let's make lots of them!!



hw6pr2: A 4-bit multiplier

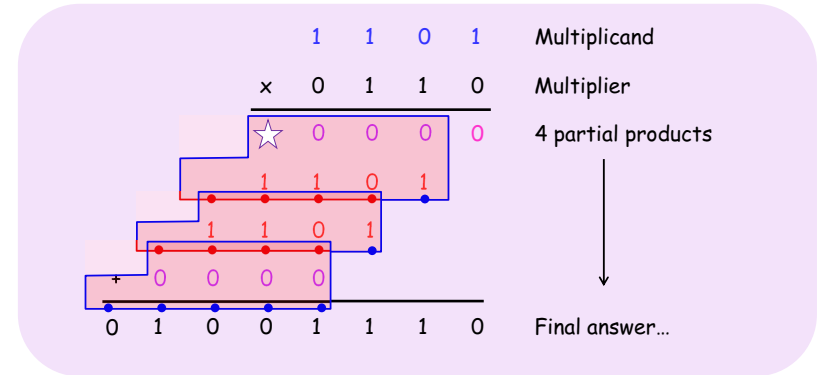


(A1) The AND gate is **single-bit** multiplication. (A2) ☆ == 0

(A1) Use a 4x1-bit helper circuit to find the four *partial products*...

(A3) You need three (3) ripple-carry adders to finish: *see above*...



Division? hw6pr3

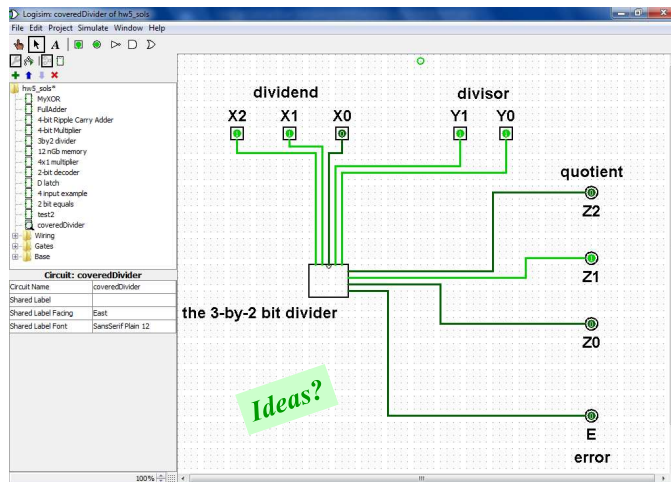

principled design Minterm Division

(0) All computation can be expressed as bits...

(1) **Any** function of bits can be made a truth table →

(2) Consider the output, *one bit at a time*...

(3) *The circuit will output 0 by default!*

(4) Are there *subcircuit patterns* to notice?

(5) Else, use an AND gate to **select** each input for which the output should be 1 (a minterm!)

To implement the red 1, how many inputs will its AND gate have?

How many negated?

What division is it?

(6) OR the outputs from step (5) together.

(7) optimize your circuit later -- *or never*

INPUTS				OUTPUT				
Y2	Y1	Y0	X1	X0	Z2	Z1	Z0	E
dividend				divisor		quotient		
anything				0	0	anything	1	error bit
0	0	0	0	1	0	0	0	0
0	0	1	0	1	0	0	1	0
0	1	0	0	1	0	1	0	0
0	1	1	0	1	0	1	1	0
1	0	0	0	1	1	0	0	0
1	0	1	0	1	1	0	1	0
1	1	0	0	1	1	1	0	0
1	1	1	0	1	1	1	1	0
<hr/>								
0	0	0	1	0	0	0	0	0
0	0	1	1	0	0	0	0	0
0	1	0	1	0	0	0	1	0
0	1	1	1	0	0	0	1	0
1	0	0	1	0	0	1	0	0
1	0	1	1	0	0	1	0	0
1	1	0	1	0	0	1	1	0
1	1	1	1	0	0	1	1	0
<hr/>								
0	0	0	1	1	0	0	0	0
0	0	1	1	1	0	0	0	0
0	1	0	1	1	0	0	0	0
0	1	1	1	1	0	0	1	0
1	0	0	1	1	0	0	1	0
1	0	1	1	1	0	0	1	0
1	0	1	1	1	0	0	1	0
1	1	0	1	1	0	1	0	0
1	1	1	1	1	0	1	0	0

Time-optimized circuits: *Carry lookahead adders*

The following circuit is called a **carry lookahead adder**.

By adding more hardware, we reduced the number of levels in the circuit and sped things up.

We can "cascade" carry lookahead adders, just like ripple carry adders. We'd have to do carry lookahead *between* the adders too.

How much faster is this?

For a 4-bit adder, not much. There are 4 gates in the longest path of a carry lookahead adder, versus 9 gates for a ripple carry adder.


But if we do the cascading properly, a 16-bit carry lookahead adder could have only 8 gates in the longest path, as opposed to 33 for a ripple carry adder.

Newer CPUs these days use 64-bit adders. **That's 12 vs. 129 gates or 10x speedup!**


The delay of a carry lookahead adder grows *logarithmically* with the size of the adder, while a ripple carry adder's delay grows *linearly*.

The thing to remember about this is the **trade-off between complexity and performance**. Ripple carry adders are simpler, but slower. Carry lookahead adders are faster but more complex.

Building a NOT gate

 


Building a NOT gate from transistors...

 


Transistors are current **switches**:


switch-off-type (pmos)

 

switch-on-type (nmos)

 

Half a computer: the CPU

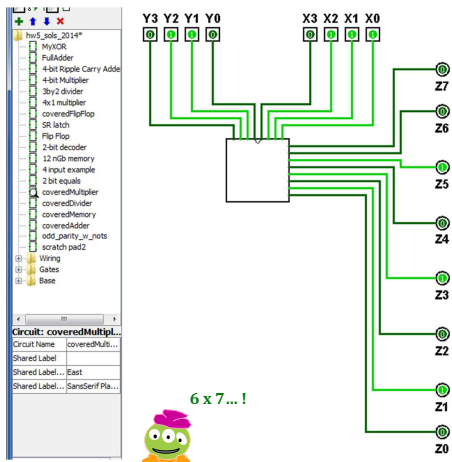


transistors

↓
gates

↓
arithmetic

For systems, a face-lift is to add an edge that **creates a cycle**, not just an additional node.

- also Alan Perlis

 

NOR's Truth Table

NOR		
X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	0

Let's engineer this into 1 bit of memory!


For systems, a face-lift is to add an edge that *creates a cycle*, not just an additional node.

- also Alan Perlis



Thought experiment

 - The circuit starts with **R** being **0** and **S** being **0**
- The *internal wires* may be undefined, to start (this is ok) ...




NOR's Truth Table

X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	0

- What happens if **R** is set to **1**? (and **S** stays **0**)
- What happens if **R** is set back to **0**? (and **S** stays **0**)
- What if, then, **S** is set to **1**? (and **R** stays **0**)
- What happens if, then, **S** is set back to **0**? (and **R** stays **0**)
- Why does "**S**" stand for "**Set**" and **R** for "**Reset**"?

The flip-flop

Demo!

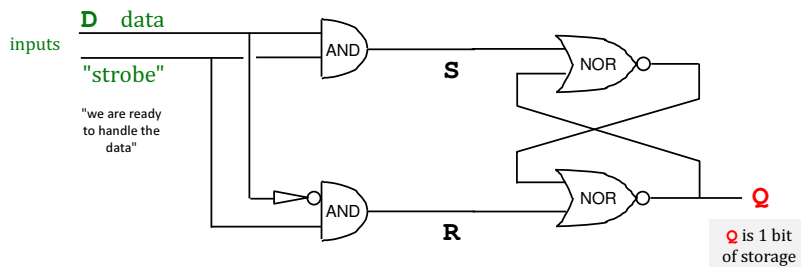


the flip-flop's diagram

1 bit of memory!

Random Access Memory


Demo!

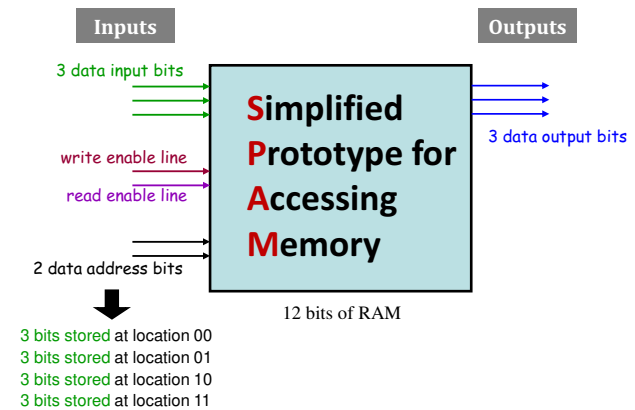Extra this week: *Design 12nGbits of RAM*




Extra Credit

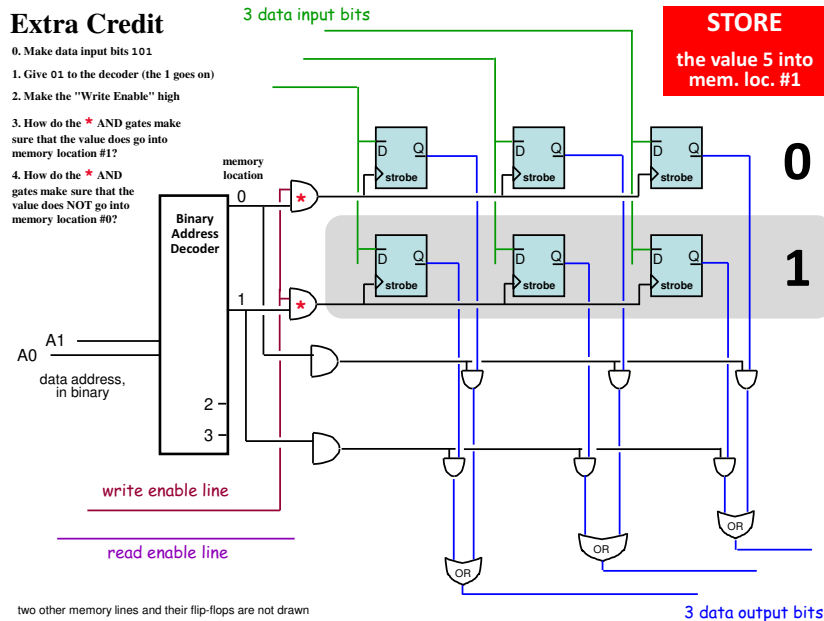0. Make data input bits 101
1. Give 01 to the decoder (the 1 goes on)
2. Make the "Write Enable" high
3. How do the * AND gates make sure that the value does go into memory location #1?
4. How do the * AND gates make sure that the value does NOT go into memory location #0?



0. Suppose 101 is in Location #1
1. Give 01 to the decoder (the 1 goes on)
2. Make the "Read Enable" high
3. Which gates will ensure bits from memory location #1 are read out?
4. Which gates will ensure bits from memory location #0 are not read out?

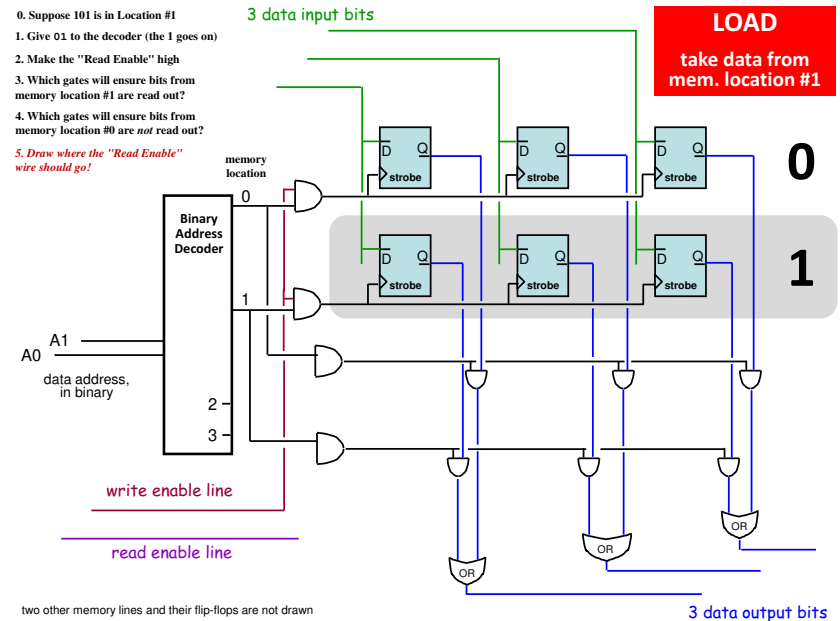5. Draw where the "Read Enable" wire should go!



Quiz

Name(s) _____

X	Y	Z
0	0	
0	1	
1	0	
1	1	

(1) Find the circuit's truth table


Transistors are current **switches**:

switch-off-type (pmos)


0v "connects" this wire 3v "cuts" this wire

switch-on-type (nmos)

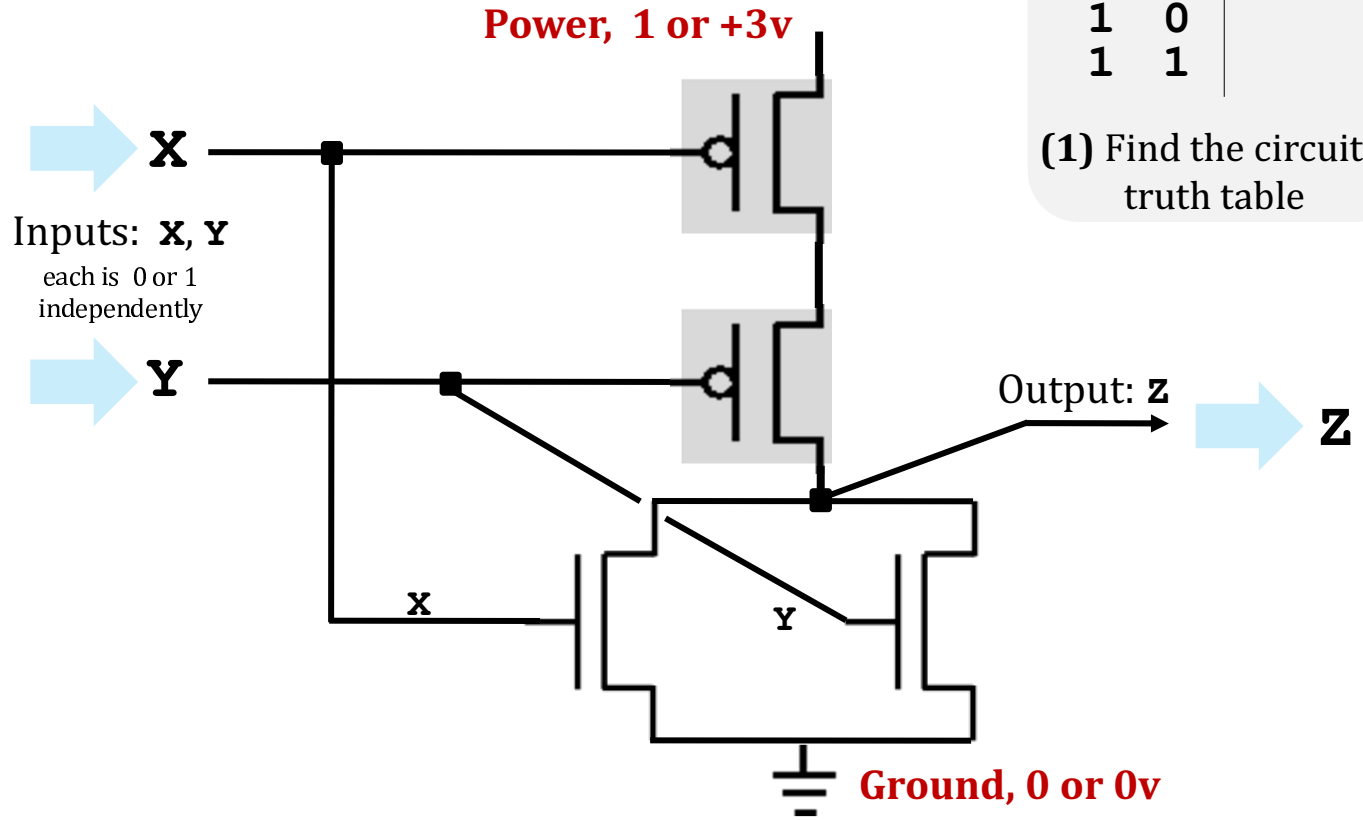0v "cuts" this wire 3v "connects" this wire



 (3) Extra! How could you alter the transistor-level design to make an AND?



(2) the above circuit is one of these gates – *which one?*

